


ECE 2C HW #6 Solution

1/12

By Li Sun.

Problem 1:

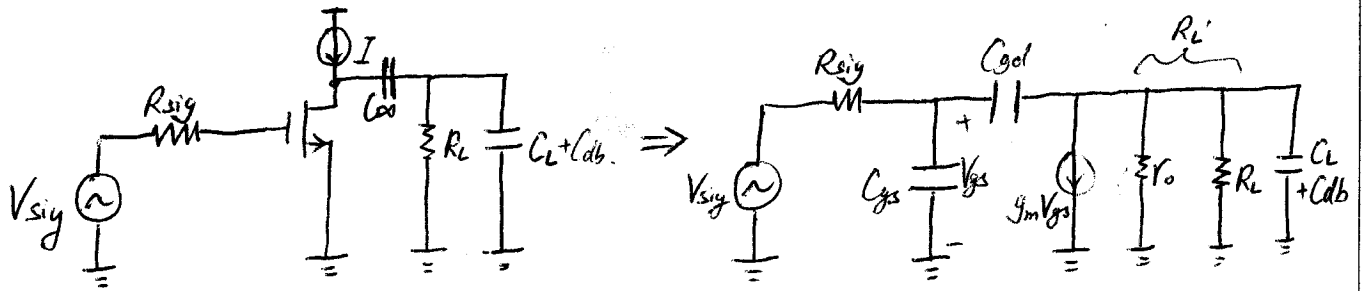(a) The circuit schematic and equivalent circuit is as:



where $C_L + C_{db} = 1 \text{ pF}$, $R_{sig} = R_L = 20 \text{ k}\Omega = r_o$, $g_m = 5 \text{ mA/V}$, $C_{gs} = 2 \text{ pF} = 10 \cdot C_{gd}$.

Obviously, $A_m = -g_m (R_L \parallel r_o) = -5 \times 10 = -50$

As for the f_H , we need to calculate Z_H first.

$$Z_H = C_{gs} \cdot R_{gs}^o + C_{gd} \cdot R_{gd}^o + (C_L + C_{db}) \cdot R_L^{i'o}$$


where $R_{gs}^o = R_{sig}$, $R_L^{i'o} = R_L \parallel r_o$, $R_{gd}^o = (1 + g_m R_L') R_{sig} + R_L'$

$$\begin{aligned} \therefore Z_H &= 2 \text{ pF} \times 20 \text{ k}\Omega + 1 \text{ pF} \times 10 \text{ k}\Omega + 0.2 \text{ pF} \times (51 \times 20 \text{ k}\Omega + 10 \text{ k}\Omega) \\ &= 40 + 10 + 206 \text{ ns} = 256 \text{ ns} \end{aligned}$$

therefore, $f_H = \frac{1}{2\pi Z_H} = 621.7 \text{ kHz}$.

$$\therefore \text{BW}_{LP} = f_t = 50 \times 621.7 \text{ kHz} = 31.1 \text{ MHz}$$

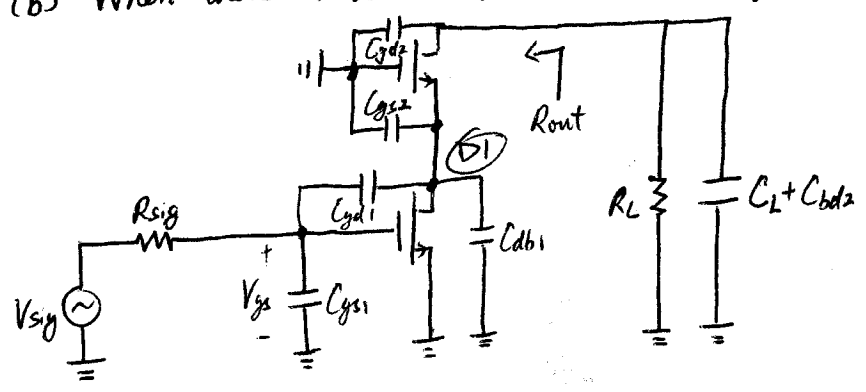(b) When there is a CG transistor, the equivalent circuit will be:



Here, we can find 4 terms in time constant, corresponding to

C_{gs1} , C_{gd1} , $C_{db1} + C_{gs2}$, and $C_{gd2} + C_L + C_{gd2}$, respectively.

First, we need to calculate R_{D1} , which is the resistance looking into node $\triangleright 1$.

This R_{D1} is also the corresponding open-time constant resistance of $C_{db1} + C_{gs2}$.

$$R_{D1}^0 = R_{D1} = r_{o1} \parallel \left[\frac{1}{g_{m2} + g_{mb2}} + \frac{R_L}{A_{v02}} \right]$$

where $g_{mb2} = \chi g_{m2}$, we can get $g_m' = g_m + g_{mb} = 1.2 \cdot g_m = 6 \text{ mS}$

Also, $A_{v02} = 1 + g_m' \cdot r_{o2} = 1 + 1.2 \times 5 \text{ mS} \times 20 \text{ k}\Omega = 121$

$$\therefore R_{D1}^0 = R_{D1} = 20 \text{ k}\Omega \parallel 0.332 \text{ k}\Omega \approx 0.32654 \text{ k}\Omega$$

Now we can write $Z_{H-cascade} = C_{gs1} \cdot R_{gs1}^0 + C_{gd1} \cdot R_{gd1}^0 + (C_{db1} + C_{gs2}) \cdot R_{D1}^0 + (C_{gd2} + C_L + C_{gd2}) \cdot (R_L \parallel R_{out})$

$$\text{And } \begin{cases} R_{gs1}^0 = R_{sig} \\ R_{gd1}^0 = R_{D1} + (1 + g_m' \cdot R_{D1}) \cdot R_{sig} \\ R_{out} = r_{o2} + A_{v02} \cdot r_{o1} \approx A_0 \cdot r_{o1} \\ A_0 = g_m' \cdot r_{o1} \approx A_{v02} = 121 \end{cases} \Rightarrow \begin{cases} R_{gs1}^0 = 20 \text{ k}\Omega \\ R_{gd1}^0 = 39.511 \text{ k}\Omega \\ R_{D1}^0 = 0.32654 \text{ k}\Omega \\ R_L \parallel R_{out} \approx 121 \times 20 \text{ k}\Omega \end{cases}$$

Therefore, $Z_{in_cascade} = 2\text{pF} \times 20\text{k}\Omega + 0.2\text{pF} \times 53\text{k}\Omega + 2.2\text{pF} \times 0.32654\text{k}\Omega + 1.2\text{pF} \times 20\text{k}\Omega$


$$= 40\text{ns} + 10.6\text{ns} + 0.7184\text{ns} + 24\text{ns}$$

$$= 75.32\text{ns}$$

$$\therefore f_{H_cascade} = \frac{1}{2\pi Z_{in_cascade}} = 2.113\text{MHz}$$

Because $A_{v_cascade} = A_{v1} A_{v2} \dots \frac{R_{L2}}{R_{L1} + A_{v1} C_{L1}} = A_{v1} A_{v2} \dots \frac{R_{L2}}{R_{L1} + A_{v1} C_{L1}} = -98.4\%N$

we have $f_T = |A_{v_cascade}| \times f_{H_cascade} = 207.924\text{MHz}$

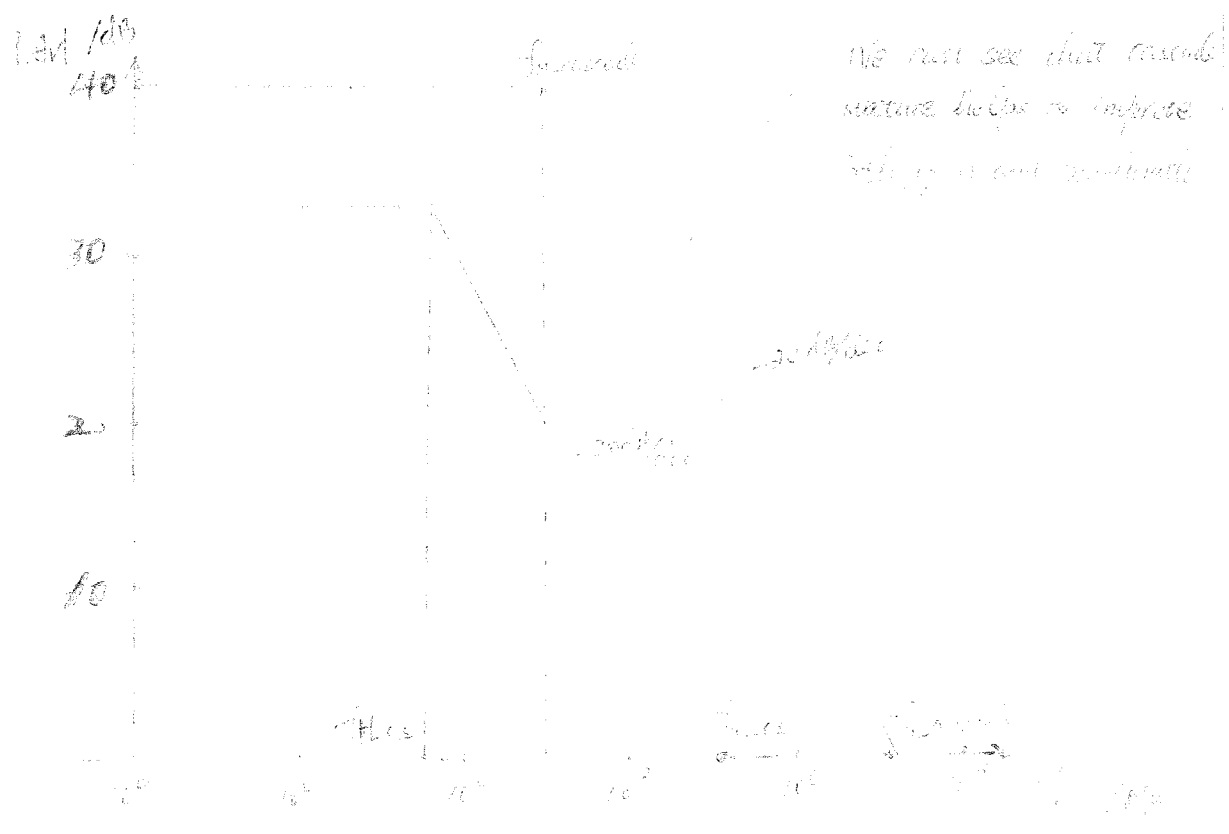


As for the $2I$ current source, because the equivalent resistance seen by this source is $R_{eq} = r_{o1} \parallel \left[\frac{1}{g_{m2} + g_{mb2}} + \frac{R_L}{A_{v02}} \right]$

where R_L is the output resistance of I current source

Therefore, $R_{eq} \approx r_{o1} \parallel r_{o2} \approx r_{o1}/2$


As long as the output resistance of $2I$ current source $R_{out-2I} \gg R_{eq}$, we can assume this source is ideal.

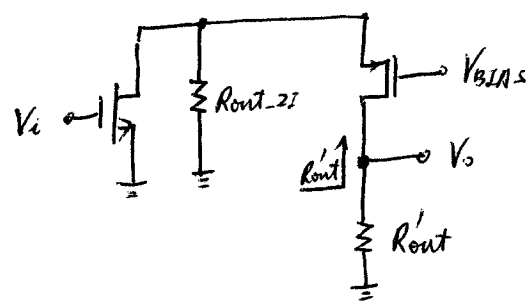When taking into account of the output resistance of $2I$ source, we have:



Now, we still can calculate A'_{v0} first.
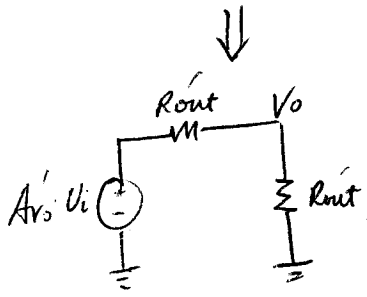
$$A'_{v0} = A'_{v01} \cdot A'_{v02} = -g_{m1} (r_{o1} \parallel R_{out-2I}) \cdot [1 + g_{m2} r_{o2}]$$



Therefore, $\frac{V_o}{V_i} = \frac{A'_{v0}}{2} = -\frac{g_{m1}}{2} (r_{o1} \parallel R_{out-2I}) (1 + g_{m2} r_{o2})$



Hence, if the total gain reduced by 1%, means that $r_{o1} \parallel R_{out-2I} = 0.99 \cdot r_{o1}$

$$\Rightarrow R_{out-2I} = 99 \cdot r_{o1} = 4.95 \text{ M}\Omega$$

Problem 3:

$\beta_0 = 100, V_A = 100V, C_u = 0.2 pF$

$C_e = 0.8 pF, f_T = 400 MHz$

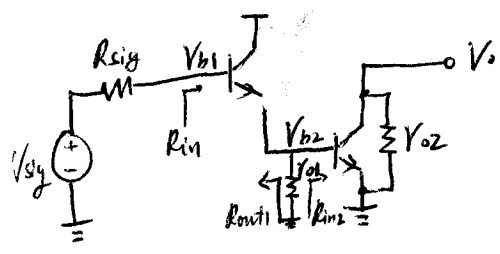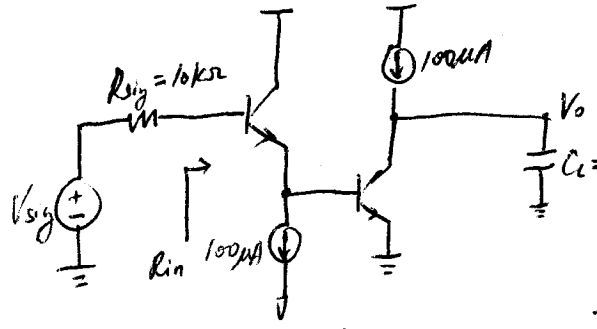

(a) we can get that $g_m = \frac{100 \mu A}{25 mV} = 4 mS$

$R_{in2} = r_{e2} = \beta/g_m = 25 k\Omega$

$r_o = V_A/I = 1 M\Omega$

$R_{out1} = (r_{e1} + \frac{R_{sig}}{\beta+1}) \parallel r_o = (250 + \frac{10k}{101}) \parallel 1M \approx 349 \Omega$

$R_{in} = (\beta+1)(r_{e1} + R_{in2}) = 101 \times 25.25 k = 2.55 M\Omega$

$\therefore \frac{V_o}{V_{sig}} = \frac{V_o}{V_{b2}} \cdot \frac{V_{b2}}{V_{b1}} \cdot \frac{V_{b1}}{V_{sig}}$


Here $r_{o1} = 1 M\Omega \gg R_{in2} = 25 k\Omega$ we just neglect r_{o1} .

$\frac{V_o}{V_{b2}} = -g_m \cdot r_{o2}, \frac{V_{b2}}{V_{b1}} = \frac{R_{in2}}{R_{in2} + R_{out1}} = \frac{25000}{25000 + 349} \approx 0.98623$

$\frac{V_{b1}}{V_{sig}} = \frac{R_{in}}{R_{in} + R_{sig}} = \frac{2550 k\Omega}{2550 k\Omega + 10 k\Omega} \approx 0.9961$

Therefore, $\frac{V_o}{V_{sig}} = 0.9961 \times 0.98623 \times (-4 mS \times 1 M\Omega) = -3929.53$

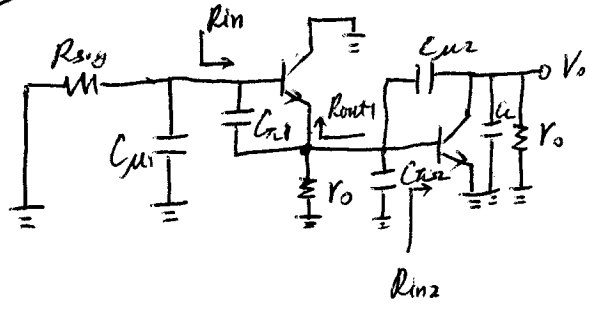(b) Because $C_u + C_{e1} = \frac{g_m}{2\pi f_T} = 1.59 pF \therefore C_{T0} = 1.39 pF$



We have 4 capacitors. therefore

$Z_H = C_{u1} \cdot R_{in} + C_{e1} \cdot R_{in} + C_{u2} \cdot R_{in2} + C_{e2} \cdot R_{in2} + C_L \cdot r_o$

Obviously, $R_{in}^0 = R_{sig} \parallel R_{in} = 10k\Omega \parallel 2.55M\Omega \approx 10k\Omega$

7/12

$$R_{\pi 1}^0 = \frac{R_{sig} + R_L'}{1 + \frac{R_{sig}}{r_{\pi}} + \frac{R_L'}{r_e}} \quad \text{where } R_L' = r_o \parallel R_{in2} \approx 25k\Omega$$

$$= \frac{10k + 25k}{1 + \frac{10k}{25k} + \frac{25k}{250}} \approx 345.16 \Omega$$

$$R_{out}^0 = R_{out1} \parallel r_o \parallel R_{in2} \approx 349\Omega \parallel 1M\Omega \parallel 25k\Omega = 344.2 \Omega$$

$$R_{in2}^0 = r_o + (1 + g_m r_o) \cdot (R_{out1} \parallel r_o \parallel R_{in2})$$

$$= 1M\Omega + (1 + 4ms^{-1}M\Omega) \times 344.2 \Omega \approx 2.377 M\Omega$$

Therefore, $Z_H = 0.2pF \times 10k\Omega + 1.39pF \times 345.16\Omega + 1.39pF \times 344.2\Omega + 0.2pF \times 2.377M\Omega + 1pF \times 1M\Omega$

$$\approx 478.36 \text{ ns}$$

$$\therefore f_H = \frac{1}{2\pi Z_H} = \frac{107.66}{2\pi} \text{ kHz}$$

Obviously, C_1 is dominant because r_o is huge compared to others.

C_{in2} is second important capacitor.

(c) If current increases to 10 times, g_m will be $10g_m$ r_o will be $r_o/10$

$$\therefore \frac{V_o}{V_{sig}} = -10g_m \frac{r_o}{r_o} \times \frac{25k/10}{25k/10 + 25 + \frac{10k}{101}} \times \frac{101 \times (25 + \frac{25k}{10})}{101 \times (25 + \frac{25k}{10}) + 10k} = -3667.2$$

which is not very different than before.

But as for frequency response, because now $C_{T1} + C_p = \frac{10.9 \text{ n}}{2\pi f_T} = 15.9 \text{ pF}$ 8/12

we have $C_{T1} = 15.7 \text{ pF}$

$$\left\{ \begin{aligned} R_{\mu 1}^0 &= R_{sig} \parallel R_{in}' = 10 \text{ k}\Omega \parallel 255.025 \text{ k}\Omega \approx 9.6 \text{ k}\Omega \\ R_{T1}^0 &= \frac{R_{sig} + R_o' \parallel R_{in}'}{1 + \frac{R_{sig}}{r_{\pi}} + \frac{R_o' \parallel R_{in}'}{r_e}} = \frac{10 \text{ k} + 100 \text{ k} \parallel 2500}{1 + \frac{10 \text{ k}}{2500} + \frac{100 \text{ k} \parallel 2500}{25}} = \frac{12439}{1 + 4 + 4} = 121.285 \Omega \\ R_{\mu 2}^0 &= R_{out1} \parallel R_o' \parallel R_{in2} = 124 \Omega \parallel 100 \text{ k} \parallel 2500 \approx 118.15 \Omega \\ R_{\mu 2}^0 &= R_o' + (1 + g_m' r_o')(R_{\mu 2}^0) = 100 \text{ k}\Omega + 4001 \times 118.15 \Omega = 572.72 \text{ k}\Omega \end{aligned} \right.$$


$$\therefore Z_H' = 0.2 \text{ pF} \times 9.6 \text{ k}\Omega + 15.7 \text{ pF} \times 121.285 \Omega + 15.7 \text{ pF} \times 118.15 \Omega + 0.2 \text{ pF} \times 572.72 \text{ k}\Omega + 1 \text{ pF} \times 100 \text{ k}\Omega$$

$$\approx 220.22 \text{ nS}$$

$$\therefore f_H' = \frac{1}{2\pi Z_H'} = 722.7 \text{ kHz}$$

Now we find that both C_L and $C_{\mu 2}$ are dominant, and the f_H is increased by about 7 times.


Problem 4.

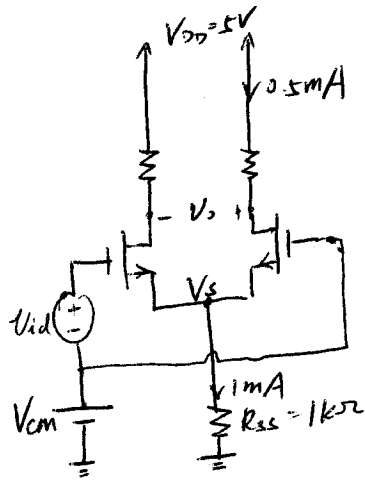

(a) Obviously, $0.5\text{mA} = \frac{1}{2} \times 2.5\text{mA/V} \times (V_{cm} - V_s - |V_{th}|)^2$

where $V_s = 1\text{mA} \times 1\text{k}\Omega = 1\text{V}$

$\Rightarrow V_{cm} = 2.332\text{V}$

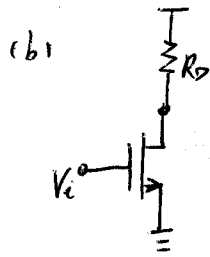


we have that $A_d = g_m R_D = 8\text{ V/V}$

where $g_m = \frac{2I_D}{(V_{cm} - V_s - |V_{th}|)} = 1.58\text{ mS}$

$\therefore R_D = 5.06\text{ k}\Omega$

(c) Because the current of each transistor is 0.5mA . Hence $V_D = 2.47\text{V}$

And because $V_D > V_{cm} - |V_{th}|$, Q_1 and Q_2 indeed are saturated.

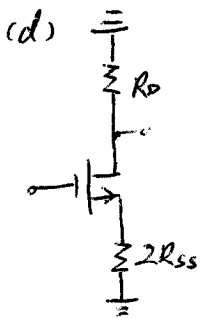

Because we cannot neglect $1/g_m$.

We know $\frac{\Delta V_{D1}}{\Delta V_{cm}} = - \frac{g_m}{1 + g_m 2R_{ss}} \times R_D = \frac{-5.06\text{ k}}{2\text{ k} + 0.633\text{ k}} = -1.92$

(e) If Q_1 and Q_2 get into triode region,

we know that $V_G - V_{th} = V_D$

$2.332\text{V} + \Delta V_{cm} - 0.7\text{V} = 2.47\text{V} + \Delta V_D$

Based on (d), $\Delta V_D = -1.92 \Delta V_{cm}$, hence,


$2.92 \Delta V_{cm} = 0.838\text{V}$

$\Rightarrow \Delta V_{cm} = 0.287\text{V}$

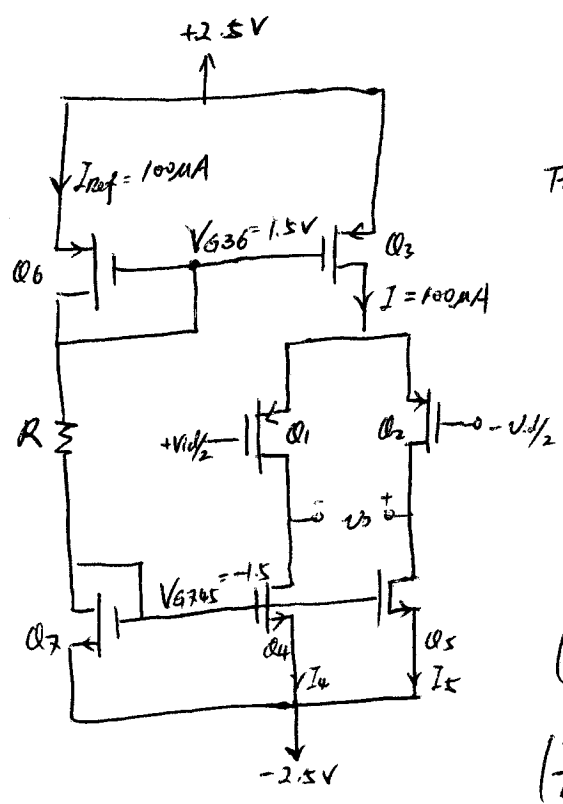Problem 3.

Obviously, $I_3 = I_6 = I = I_{ref} = 100 \mu A$

$$I_1 = I_2 = I_4 = I_5 = \frac{I}{2} = 50 \mu A$$



Therefore, $\left(\frac{W}{L}\right)_3 = \left(\frac{W}{L}\right)_6$

$$\left(\frac{W}{L}\right)_4 = \left(\frac{W}{L}\right)_5 = \frac{1}{2} \left(\frac{W}{L}\right)_7$$

$$I = 100 \mu A = \frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L}\right)_{3,6} (2.5 - 1.5 - 0.7)^2$$

$$\frac{I}{2} = 50 \mu A = \frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L}\right)_{4,5} (1.5 + 2.5 - 0.7)^2$$

$$\left(\frac{W}{L}\right)_3 = \left(\frac{W}{L}\right)_6 = 74.07, \quad \left(\frac{W}{L}\right)_4 = \left(\frac{W}{L}\right)_5 = 12.346$$

$$\left(\frac{W}{L}\right)_7 = 2 \left(\frac{W}{L}\right)_{4,5} = 24.69$$

If we want $A_d = 80 V/V$ - $g_{m1} (r_{on} || r_{op})$ must be 80.

where $g_{m1} = \sqrt{2 \cdot \frac{I}{2} \mu_n C_{ox} \left(\frac{W}{L}\right)_1}$ and $r_{on} = r_{op} = \frac{V_A}{I/2} = \frac{20V}{50 \mu A} = 400 k\Omega$

$$\therefore \sqrt{3000 \mu A/V^2 \left(\frac{W}{L}\right)_1} \cdot 200 k\Omega = 80$$


$$\Rightarrow \left(\frac{W}{L}\right)_1 = \left(\frac{W}{L}\right)_2 = 53.33$$

As for R, we know $R = \frac{V}{I} = \frac{V_{G36} - V_{G745}}{I_{ref}} = \frac{3V}{100 \mu A} = 30 k\Omega$

For $V_{GS1,2}$, we know $50 \mu A = \frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L}\right)_{1,2} (V_{GS1,2} - 0.7)^2$

$$\Rightarrow V_{GS1,2} = 0.95 V$$

Problem 6.

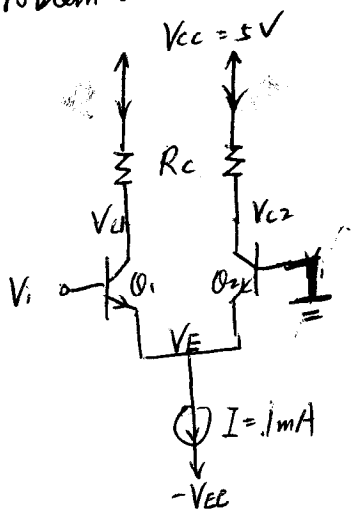


First we need to know what region the transistors are. Because $V_i = 1V$, we can assume Q_1 works in saturation. Hence, $V_E = 1 - 0.7 = 0.3V$, which means Q_2 will be off.

$\therefore V_{C2} = V_{CC} = 5V \quad I_{E1} = I = 1mA$

$\therefore I_{C1} = \alpha I_{E1} = \frac{\beta}{\beta+1} I_{E1} = 0.99mA$

$\therefore V_{C1} = V_{CC} - I_{C1} \cdot R_C = 2.03V$

Problem 7.

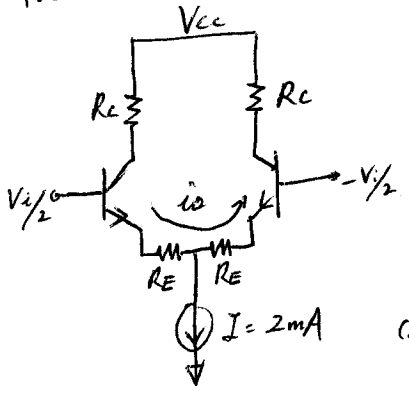

(a) $i_e = \frac{v_{id}}{2r_e + 2R_E} = \frac{0.1V}{50\Omega + 200\Omega} = 400\mu A$

$v_{be} = (v_{id} - 2R_E \cdot i_e) / 2 = (0.1V - 200\Omega \times 400\mu A) / 2 = 0.01V$

(b) $I_{E1} = \frac{I}{2} + i_e = 1.4mA, \quad I_{E2} = \frac{I}{2} - i_e = 0.6mA$


(c) ~~...~~

$v_c = \pm \frac{R_C}{r_e + R_E} \times \frac{v_{id}}{2} = \pm \frac{5k\Omega}{25\Omega + 100\Omega} \times 0.05V = \pm 2V$

(d) $A_{vd} = \frac{R_C}{r_e + R_E} = 40 \text{ V/V}$

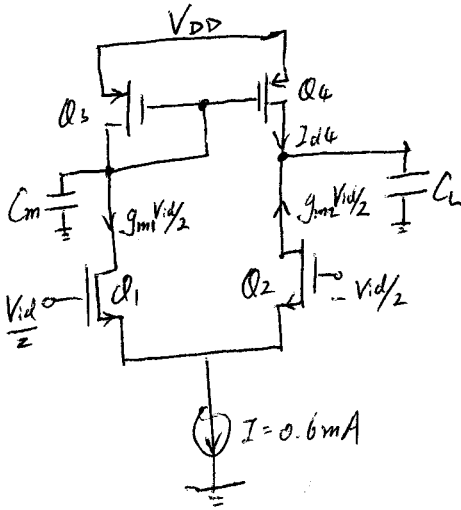Problem 8:

we know $C_m = 0.1 \text{ pF}$, $C_L = 0.2 \text{ pF}$.



$$\begin{cases} g_{m1} = g_{m2} = \frac{2I/2}{V_{ov1,2}} = \frac{0.6 \text{ mA}}{0.3 \text{ V}} = 2 \text{ mS} \\ g_{m3} = g_{m4} = \frac{2I/2}{V_{ov3,4}} = \frac{0.6 \text{ mA}}{0.5 \text{ V}} = 1.2 \text{ mS} \end{cases}$$

$$r_{o1} = r_{o2} = r_{o3} = r_{o4} = r_o = \frac{V_A}{I/2} = \frac{9 \text{ V}}{0.3 \text{ mA}} = 30 \text{ k}\Omega$$

$$V_{g3} = V_{g4} = -g_{m1} V_{id/2} \cdot \left[\frac{1}{g_{m3}} \parallel r_o \parallel r_o \parallel \frac{1}{sC_m} \right]$$

$$= -g_{m1} V_{id/2} \times \frac{1}{sC_m + 1.267 \text{ mS}}$$

$$I_{d4} = -g_{m4} \cdot V_{g3} = \frac{g_{m4} g_{m1} V_{id/2}}{sC_m + 1.267 \text{ mS}}$$

$$\Rightarrow I_o = I_{d4} + I_{d2} = \frac{g_{m4} g_{m1} V_{id/2}}{sC_m + 1.267 \text{ mS}} + g_{m2} V_{id/2} \quad \text{and} \quad V_o = I_o \frac{1}{\frac{1}{R_o} + sC_L}$$

$$\Rightarrow V_o = \frac{V_{id}}{2} \times \left[g_{m2} + \frac{g_{m4} g_{m1}}{sC_m + 1.267 \text{ mS}} \left(\frac{R_o}{1 + sC_L R_o} \right) \right]$$

$$\Rightarrow A_v = \frac{V_o}{V_{id}} = \frac{g_{m1}}{2} \left[1 + \frac{g_{m4}}{sC_m + 1.267 \text{ mS}} \left(\frac{15 \text{ k}\Omega}{1 + sC_L R_o} \right) \right]$$

$$= g_{m1} \times 15 \text{ k}\Omega \times \frac{0.97356}{1 + sC_m/1.267 \text{ mS}} \times \frac{1 + sC_m/2.467 \text{ mS}}{1 + sC_L R_o}$$

Therefore $A_{v0} = g_{m1} \times 15 \text{ k}\Omega \times 0.97356 = 29.2068$

$$f_{p1} = \frac{1}{2\pi C_L R_o} = \frac{1}{2\pi \times 0.2 \text{ pF} \times 15 \text{ k}\Omega} = 53.052 \text{ MHz}$$

$$f_{p2} = \frac{1}{2\pi C_m/1.267 \text{ mS}} = \frac{1}{2\pi \times 0.1 \text{ pF}/1.267 \text{ mS}} = 2.016 \text{ GHz}$$

$$f_z = \frac{1}{2\pi C_m/2.467 \text{ mS}} = 3.926 \text{ GHz}$$