

Reading Assignment: S&S: 4.6-4.9, 5.6-5.7


### Homework #3

**Due: 10/20/2009 at 5PM**

Note: for some problems you may find it helpful to refer to Table 4.4 (p.319) and Table 5.6 (p.484) in S&S. Show DC and AC equivalent circuits for your calculations where appropriate. The common-gate circuit is similar to one that you will build in lab 1. For this exercise, the MOSFET has a  $V_t = 2\text{V}$ , a  $K_n = 200 \text{ mA/V}^2$  and a  $|V_A| = \infty$ .
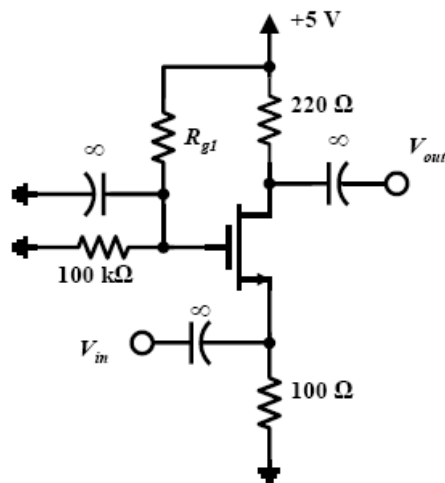
#### Part I: Hand Calculation

- Find the gate resistance  $R_{g1}$  that will give  $I_d = 10\text{mA}$ , and calculate the resulting quiescent (DC) value of  $V_{ds}$ . Is the device in saturation?
- Calculate the transconductance,  $g_m$ .
- Draw the ac small-signal equivalent circuit for this amplifier.
- Calculate the small-signal voltage gain, input resistance, and output resistance for this amplifier.
- What will be the gain if a  $1\text{-k}\Omega$  load resistor is connected to the output terminal at  $V_{out}$ ?
- Use the method of open-circuit time constant (MOTC) to calculate the lower corner frequency and the upper corner frequency. Then sketch the bode plots. You only need to consider  $C_{gs} = 12.3 \text{ pF}$  and  $C_{gd} = 33.4 \text{ pF}$  in our high-frequency ac small-signal model.



#### Part II: Computer-aid Simulation

Based on 2N7000 SPICE model provided, change the parameters to satisfy  $V_t = 2\text{V}$ ,  $K_n = 200\text{mA/V}^2$ , and  $I_d = 10\text{mA}$ , we can build this amplifier and perform the AC simulation in Multisim.

- If we want  $K_n = 200\text{mA/V}^2$ , for the  $\mu_n$  and  $C_{ox}$  given in SPICE model, what is  $W/L$ ?
- Simulate the small-signal voltage gain, input resistance, and output resistance for this amplifier.
- What would be the new gain if a  $1\text{k}\Omega$  load resistor is connected to the output terminal?
- Obtain the Bode Plot from Simulation to determine the  $-3\text{-dB}$  bandwidth? How does it compare to what you calculated?