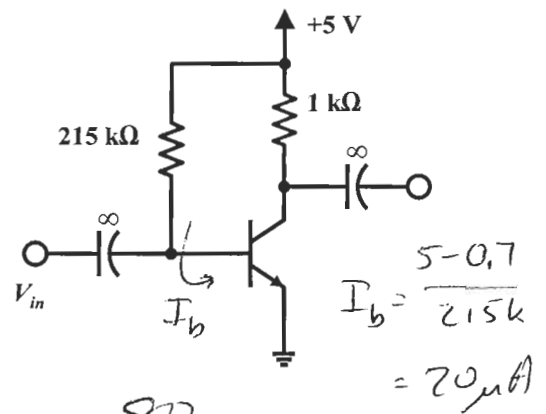


Problem 5

(20 points)

In this common-emitter amplifier the BJT has $\beta = 100$, $|V_A| = \infty$, $C_\pi = 1\text{pF}$, $C_\mu = 0.1\text{pF}$, and $V_{be} = 0.7\text{V}$ when biased in the forward conduction region. Assume room temperature such that $kT/q \approx 25\text{mV}$.


a) Find the DC collector current I_c , DC collector voltage V_c , and transconductance g_m



$$I_c = \underline{2} \text{ mA} \quad V_c = \underline{3} \text{ V} \quad g_m = \underline{80} \text{ mS}$$

$5 - I_c R_c$ $I_c / 25\text{mV}$

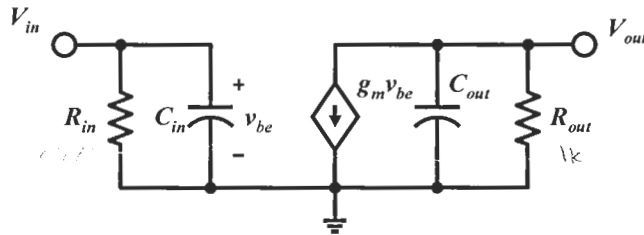b) Using the **Miller approximation**, the equivalent circuit for the high-frequency response of this amplifier can be reduced to the circuit shown at right. Find the parameters below.



Mid-band gain $A_v = \underline{-80}$

$$R_{in} = \underline{1250} \Omega$$

$$R_{out} = \underline{1k} \Omega$$

$$C_{in} = \underline{9.1} \text{ pF}$$

$$C_{out} = \underline{0.1} \text{ pF}$$

$$r_{\pi} = \beta / g_m = 1250$$

$$R_{in} = 215k \parallel r_{\pi} \approx r_{\pi}$$

$$A_v = -g_m R_{out} = -80$$

$$C_{in} = C_{\pi} + C_{\mu}(1 - A_v)$$

$$= 1 + 0.1(81) = 9.1$$

$C_{out} \approx C_{\mu}$

c) Find the dominant pole in the high-frequency response (express your answer in Hz or some engineering multiple such as MHz, GHz, etc., **not** rad/s)

$$\omega_{p1} = \frac{1}{R_{in} C_{in}} \quad \omega_{p2} = \frac{1}{R_{out} C_{out}} \gg \omega_{p1}$$


$$= 88 \times 10^6 \text{ rad/s}$$

$$\Rightarrow \omega_{p1} \text{ is dominant (lowest frequency)}$$

$$= \boxed{14 \text{ MHz}}$$

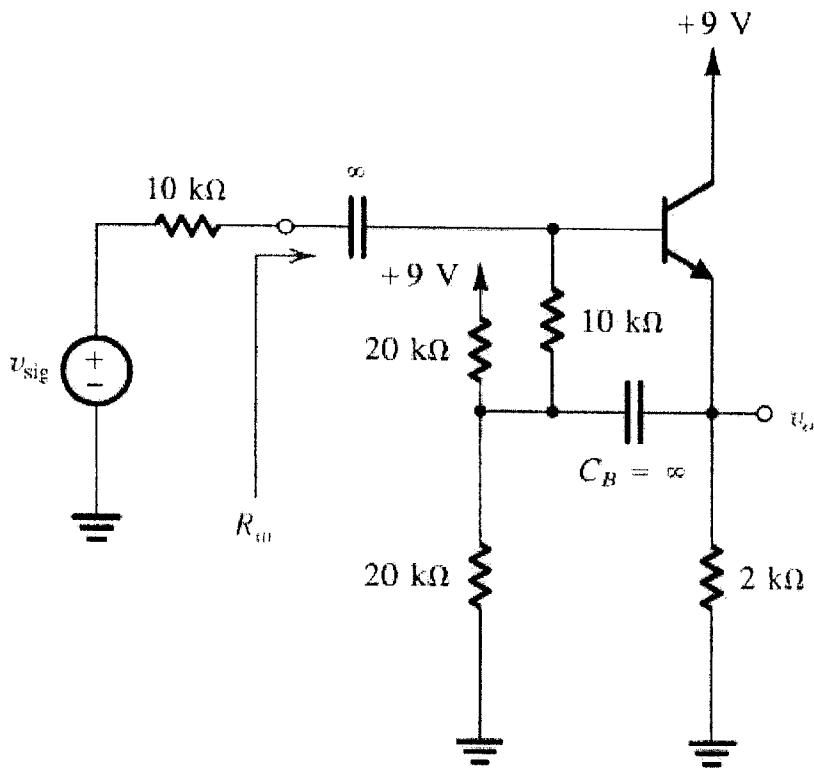Problem 3 [Total 40 pt.]

(3-a) [10 pt.] Find the dc emitter current and the NPN's small-signal equivalent circuit parameters: g_m , r_e , and r_π for $\beta=100$.




(a) DC Analysis

$$I_E = \frac{4.5 - 0.7}{2 + \frac{10+10}{101}} = \underline{\underline{1.73 \text{ mA}}}$$


$$I_C = 0.99 \times 1.73 = \underline{\underline{1.71 \text{ mA}}}$$
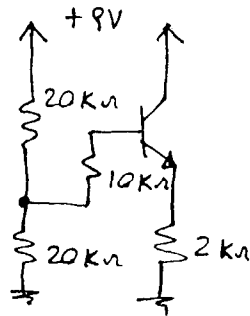
$$g_m = \frac{I_C}{V_T} = 68.5 \text{ mA/V}$$




$$r_e = \frac{V_T}{I_E} = \underline{\underline{14.5 \mu}}$$
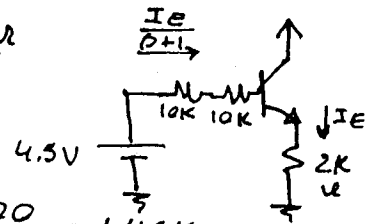
$$r_\pi = \frac{\beta}{g_m} = \frac{100}{68.5} = \underline{\underline{1.46 \text{ k}\Omega}}$$



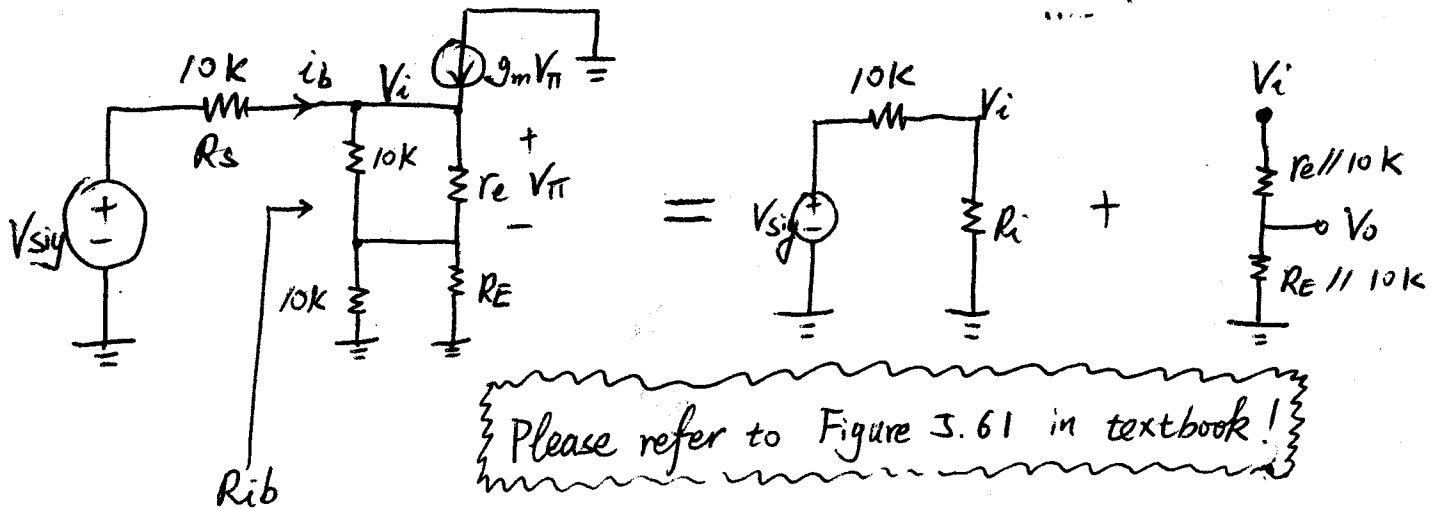(3-b) [15 pt.] Using BJT small signal model (neglect r_o), analyze the circuit to determine the input resistance R_{in} and the voltage gain v_o/v_{sig} .




For R_{ib} , we know that $R_{ib} = (\beta+1)(r_e \parallel 10k + R_E \parallel 10k)$
 $\approx 101 \times (14.5 \Omega + 1666.67 \Omega) = 169.798 \text{ k}\Omega$

Here $R_{in} = R_{ib}$. Also $\frac{V_o}{V_{sig}} = \frac{V_o}{V_i} \times \frac{V_i}{V_{sig}}$

where $\frac{V_o}{V_i} = \frac{R_E \parallel 10k}{R_E \parallel 10k + r_e \parallel 10k} = \frac{1666.67 \Omega}{1681.17 \Omega}$, $\frac{V_i}{V_{sig}} = \frac{R_{ib}}{R_{ib} + 10k} = \frac{169.798 \text{ k}\Omega}{179.798 \text{ k}\Omega}$

$\therefore \frac{V_o}{V_{sig}} = \frac{1666.67}{1681.17} \times \frac{169.798}{179.798} = 0.936 \text{ V/V}$

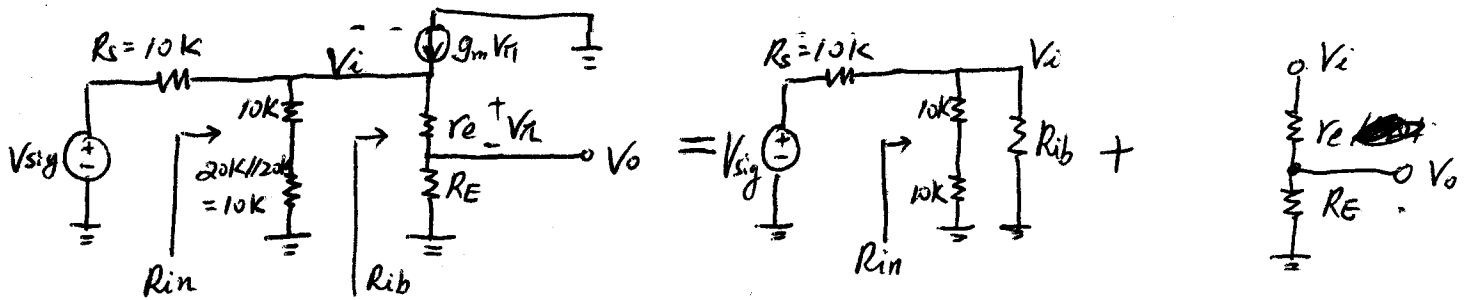(3-c) [15 pt.] Repeat (3-b) for the case when capacitor C_B is open-circuited?



Obviously, $R_{ib} = (\beta+1)(r_e + R_E) = 101 \times (2014.5 \Omega) = 203.46 \text{ k}\Omega$

Here $R_{in} = R_{ib} \parallel (10k + 10k) = 18.21 \text{ k}\Omega$

Also, $\frac{V_o}{V_{sig}} = \frac{V_o}{V_i} \times \frac{V_i}{V_{sig}} = \frac{R_E}{R_E + r_e} \times \frac{R_{in}}{R_s + R_{in}} = \frac{2000}{2014.5} \times \frac{18.21}{28.21} = 0.641 \text{ V/V}$