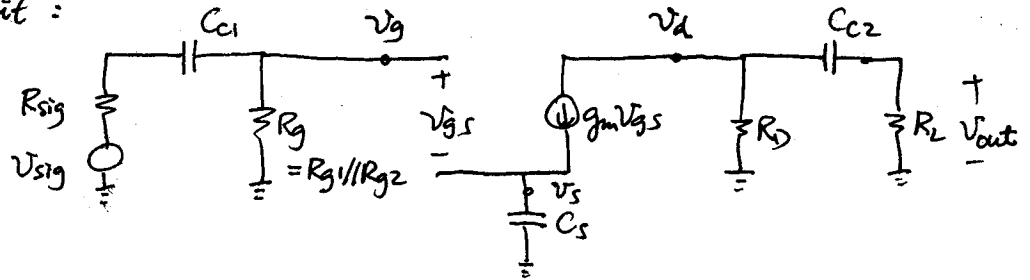


Low-freq response of a CS amplifier. (Fig. 4.51 in text)

Eq. Circuit:



Eq. 4.139:

$$A_{V-LF} = \frac{V_{out}}{V_{sig}} = \overbrace{-g_m(R_D // R_L) \frac{R_g}{R_g + R_{sig}}}_{A_{V-midband}} \cdot \left( \frac{s}{s + \omega_{p1}} \right) \left( \frac{s}{s + \omega_{p2}} \right) \left( \frac{s}{s + \omega_{p3}} \right)$$

$$\text{where } \omega_{p1} = \frac{1}{(R_g + R_{sig})C_{c1}}, \quad \omega_{p2} = \frac{g_m}{C_s}, \quad \omega_{p3} = \frac{1}{(R_D + R_L)C_{c2}}$$

Rewrite 4.139 as

$$A_{V-LF} = A_{V-midband} \left( \frac{1}{1 + \frac{\omega_{p1}}{s}} \right) \left( \frac{1}{1 + \frac{\omega_{p2}}{s}} \right) \left( \frac{1}{1 + \frac{\omega_{p3}}{s}} \right)$$

$$= A_{V-midband} \left( \frac{1}{1 + \frac{\omega_{p1}}{s} + \frac{\omega_{p2}}{s} + \frac{\omega_{p3}}{s} + \frac{\omega_{p1}\omega_{p2}}{s^2} + \frac{\omega_{p2}\omega_{p3}}{s^2} + \frac{\omega_{p1}\omega_{p3}}{s^2} + \frac{\omega_{p1}\omega_{p2}\omega_{p3}}{s^3}} \right)$$

$$= A_{V-midband} \left( \frac{1}{1 + \frac{\omega_{p1} + \omega_{p2} + \omega_{p3}}{s} + \frac{\omega_{p1}\omega_{p2} + \omega_{p2}\omega_{p3} + \omega_{p1}\omega_{p3}}{s^2} + \frac{\omega_{p1}\omega_{p2}\omega_{p3}}{s^3}} \right)$$

sub  $s = j\omega$ , and for  $\omega > \omega_{p1}, \omega_{p2}, \omega_{p3}$ , we can ignore the  $s^{-2}$  and  $s^{-3}$  terms:


$$\therefore A_{V-LF} \approx A_{V-midband} \frac{1}{1 + \frac{\omega_{p1} + \omega_{p2} + \omega_{p3}}{s}} = A_{V-midband} \frac{s}{s + (\omega_{p1} + \omega_{p2} + \omega_{p3})}$$

therefore, the lower corner frequency is  $\omega_{LF} \approx \omega_{p1} + \omega_{p2} + \omega_{p3}$

e.g.  $\omega_{p3} = 1000 \text{ krad/s}$ ,  $\omega_{p2} = 10 \text{ krad/s}$ ,  $\omega_{p1} = 0.1 \text{ krad/s}$

i.e.  $\omega_{p3} \gg \omega_{p2} \gg \omega_{p1}$ ,  $\omega_{LF} \approx \omega_{p3}$  the dominate corner frequency.

sketch of the LF Bode plot :

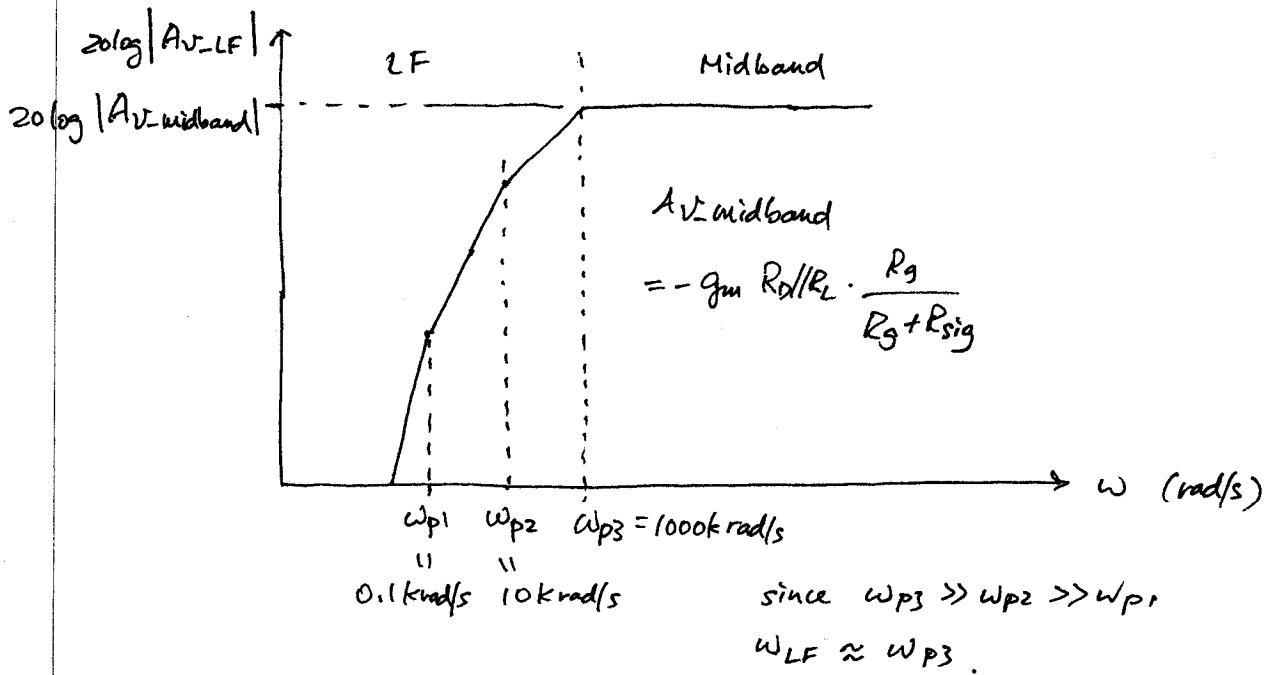


From the above derivation, we can generalize a quick estimation technique for computing  $\omega_{LF}$

$$\omega_{LF} = \sum_{i=1}^n \left( \frac{1}{\tau_i} \right) \quad \text{where } \tau_i \text{ is the time constant associated with the } i\text{th ac-coupling or bypass capacitor.}$$

To find  $\tau_i$ , we need to find <sup>the</sup> effective resistance ( $R_i$ ) seen by  $C_i$ .  $\tau_i = R_i C_i$ . When solving for  $R_i$ , all other capacitors are short circuited. This technique is sometimes referred to the Short Circuit Time Constant (SCTC) method for solving the low-frequency corner freq ( $\omega_{LF}$ ).

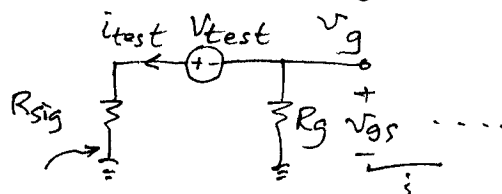(A) For the above example,  $\tau_1 = (R_g + R_{sig}) C_{c1}$ , b/c the effective  $R$  seen by  $C_{c1}$  is  $R_g + R_{sig}$  :




$$R_{cc1} = \frac{V_{test}}{I_{test}} = R_{sig} + R_g$$

$$\tau_1 = R_{cc1} C_{c1} = (R_g + R_{sig}) C_{c1}$$

$V_{sig}$ , the independent source is replaced by a short circuit.

22-141 50 SHEETS  
 22-142 100 SHEETS  
 22-144 200 SHEETS

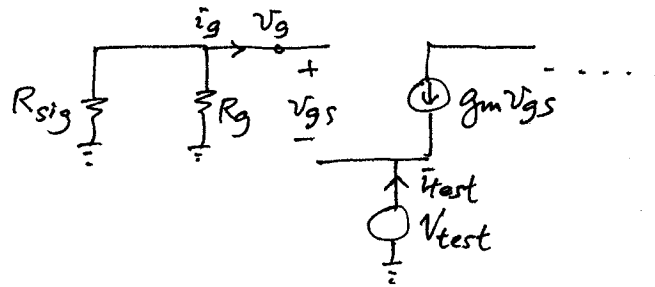(B)  $\tau_2$  is associated with  $C_s$ , to find  $R_{C_s}$ , again we remove  $v_{sig}$  and short circuit all other capacitors in the eq. circuit (i.e.  $C_{c1}$  and  $C_{c2}$ ), then apply a test voltage source to replace  $C_s$  and solve for  $V_{test}/i_{test}$



Perform KCL at the source node,  $i_{test} = -g_m v_{gs}$

Also, since  $i_g = 0$ ,  $v_g = 0$ .


Therefore  $v_{gs} = v_g - v_s = -v_s$ , which is  $= -V_{test}$ .

$$\Rightarrow v_{gs} = -V_{test}$$

$$\text{Now we can find } \frac{V_{test}}{i_{test}} = \frac{-v_{gs}}{-g_m v_{gs}} = \frac{1}{g_m} \quad (\text{as expected})$$

$$\therefore \tau_2 = \frac{1}{g_m} \cdot C_s$$

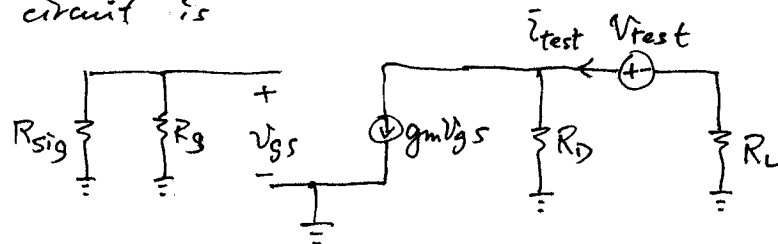(C) The 3rd time constant,  $\tau_3$ , is associated with  $C_{c2}$ :  
 the eq. circuit is



since both  $v_g$  and  $v_s$  are both 0V,  $g_m v_{gs} = 0$ ,


$$\text{so } R_{C_{c2}} = R_D + R_L = V_{test}/i_{test}.$$

$$\therefore \tau_3 = R_{C_{c2}} \cdot C_{c2} = (R_D + R_L) C_{c2}$$

To recap, once we know the time constants, we estimate

$$\omega_{LF} = \sum_{i=1}^n \frac{1}{\tau_i} = \frac{1}{\tau_1} + \frac{1}{\tau_2} + \frac{1}{\tau_3} = \omega_{p1} + \omega_{p2} + \omega_{p3}.$$

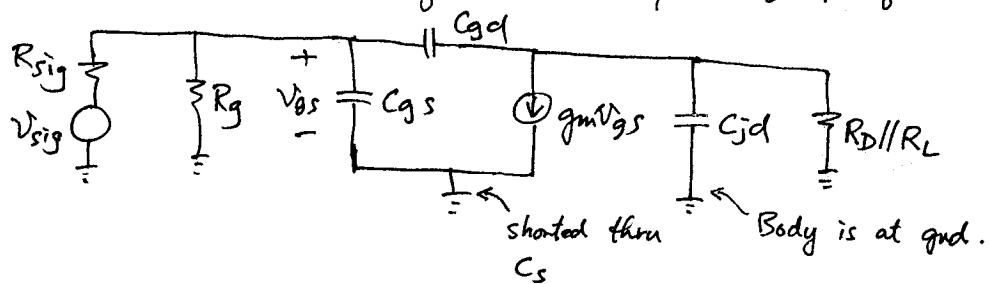Now, we can solve for the HF response of the CS amp. Let's include the effects of  $C_{gs}$ ,  $C_{gd}$  and  $C_{jd}$  in the small-signal model. Therefore, the eq. circuit for high-freq analysis is



$C_{c1}$ ,  $C_{c2}$  and  $C_s$  are all replaced by short circuit.

Because at high freq,  $\frac{1}{sC_{c1}} \rightarrow \frac{1}{j\omega C_{c1}} \rightarrow 0$  for large  $\omega$ .

$$\frac{1}{j\omega C_{c2}} \rightarrow 0 \quad ''$$

$$\frac{1}{j\omega C_s} \rightarrow 0 \quad ''$$

Just like we did in the midband analysis.

The technique to use is called open-circuit time constant (OCTC) method.