

“Open-Circuit” parameters

$$V_1 = Z_{11}I_1 + Z_{12}I_2$$


$$V_2 = Z_{21}I_1 + Z_{22}I_2$$

Reciprocal networks: $Z_{12} = Z_{21}$


Symmetrical networks: $Z_{11} = Z_{22}$

Lossless networks: $\text{Re}\{Z_{mn}\} = 0$

Thevenin equivalent circuit

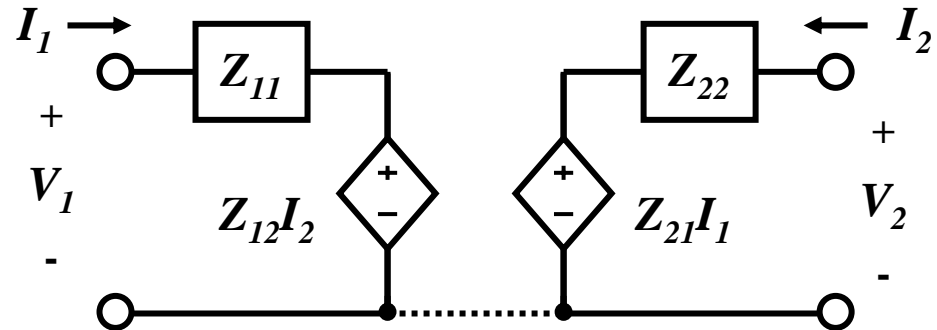

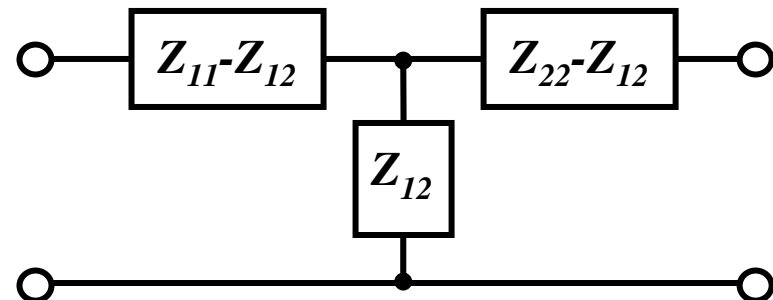equivalent circuit for reciprocal networks



“Short-Circuit” parameters

$$I_1 = Y_{11}V_1 + Y_{12}V_2$$


$$I_2 = Y_{21}V_1 + Y_{22}V_2$$

Reciprocal networks: $Y_{12} = Y_{21}$


Symmetrical networks: $Y_{11} = Y_{22}$

Lossless networks: $\text{Re}\{Y_{mn}\} = 0$

Norton equivalent circuit

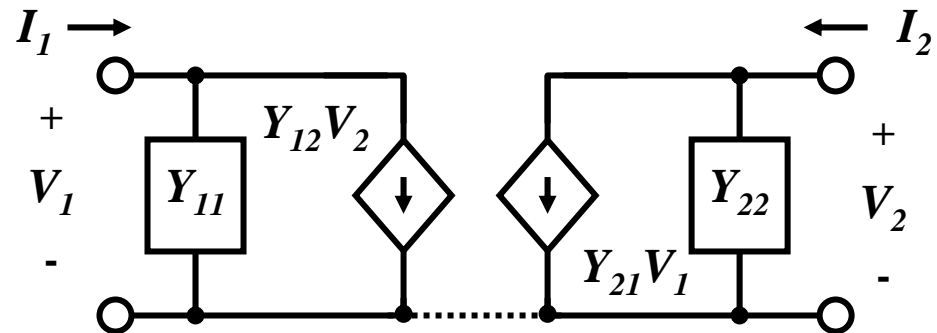

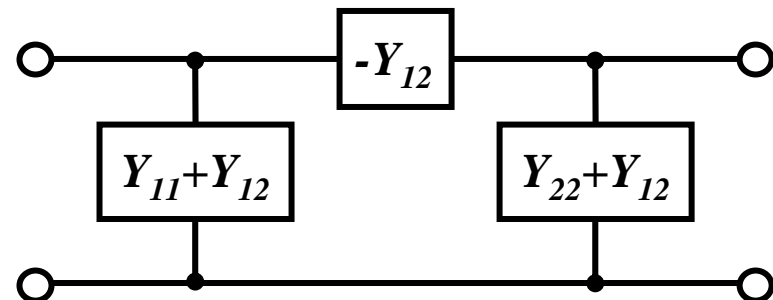equivalent circuit for reciprocal networks




“Hybrid” parameters

$$V_1 = h_{11}I_1 + h_{12}V_2$$

$$I_2 = h_{21}I_1 + h_{22}V_2$$

Equivalent circuit

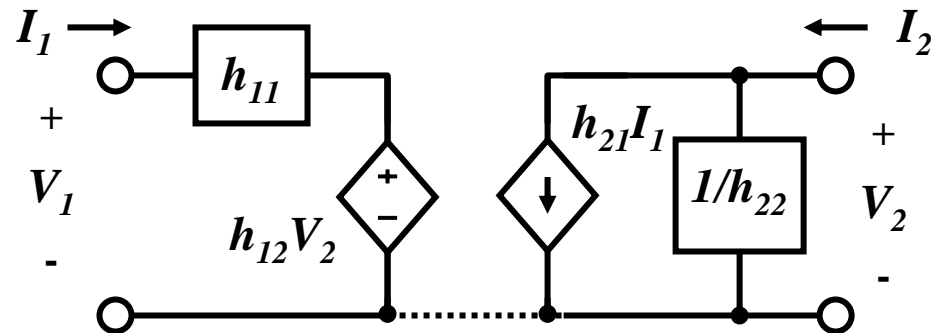

Conversions between parameters



	<i>Z</i>	<i>Y</i>	<i>h</i>	<i>ABCD</i>
<i>Z</i>	$\begin{array}{cc} z_{11} & z_{12} \\ z_{21} & z_{22} \end{array}$	$\begin{array}{cc} \frac{y_{22}}{\Delta y} & \frac{-y_{12}}{\Delta y} \\ \frac{-y_{21}}{\Delta y} & \frac{y_{11}}{\Delta y} \end{array}$	$\begin{array}{cc} \frac{\Delta h}{h_{22}} & \frac{h_{12}}{h_{22}} \\ \frac{-h_{21}}{h_{22}} & \frac{1}{h_{22}} \end{array}$	$\begin{array}{cc} \frac{A}{C} & \frac{AD-BC}{C} \\ \frac{1}{C} & \frac{D}{C} \end{array}$
<i>Y</i>	$\begin{array}{cc} \frac{z_{22}}{\Delta z} & \frac{-z_{12}}{\Delta z} \\ \frac{-z_{21}}{\Delta z} & \frac{z_{11}}{\Delta z} \end{array}$	$\begin{array}{cc} y_{11} & y_{12} \\ y_{21} & y_{22} \end{array}$	$\begin{array}{cc} \frac{1}{h_{11}} & \frac{-h_{12}}{h_{11}} \\ \frac{h_{21}}{h_{11}} & \frac{\Delta h}{h_{11}} \end{array}$	$\begin{array}{cc} \frac{D}{B} & \frac{BC-AD}{B} \\ \frac{-1}{B} & \frac{A}{B} \end{array}$
<i>h</i>	$\begin{array}{cc} \frac{\Delta z}{z_{22}} & \frac{z_{12}}{z_{22}} \\ \frac{-z_{21}}{z_{22}} & \frac{1}{z_{22}} \end{array}$	$\begin{array}{cc} \frac{1}{y_{11}} & \frac{-y_{12}}{y_{11}} \\ \frac{y_{21}}{y_{11}} & \frac{\Delta y}{y_{11}} \end{array}$	$\begin{array}{cc} h_{11} & h_{12} \\ h_{21} & h_{22} \end{array}$	$\begin{array}{cc} \frac{B}{D} & \frac{AD-BC}{D} \\ \frac{-1}{D} & \frac{C}{D} \end{array}$
<i>ABCD</i>	$\begin{array}{cc} \frac{z_{11}}{z_{21}} & \frac{\Delta z}{z_{21}} \\ \frac{1}{z_{21}} & \frac{z_{22}}{z_{21}} \end{array}$	$\begin{array}{cc} \frac{-y_{22}}{y_{21}} & \frac{-1}{y_{21}} \\ \frac{-\Delta y}{y_{21}} & \frac{-y_{11}}{y_{21}} \end{array}$	$\begin{array}{cc} \frac{-\Delta h}{h_{21}} & \frac{-h_{11}}{h_{21}} \\ \frac{-h_{22}}{h_{21}} & \frac{-1}{h_{21}} \end{array}$	$\begin{array}{cc} A & B \\ C & D \end{array}$

$$\Delta z = z_{11}z_{22} - z_{12}z_{21} \quad \Delta y = y_{11}y_{22} - y_{12}y_{21} \quad \Delta h = h_{11}h_{22} - h_{12}h_{21}$$