
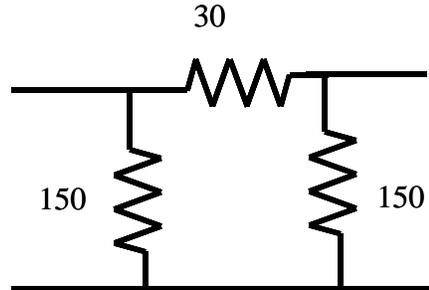


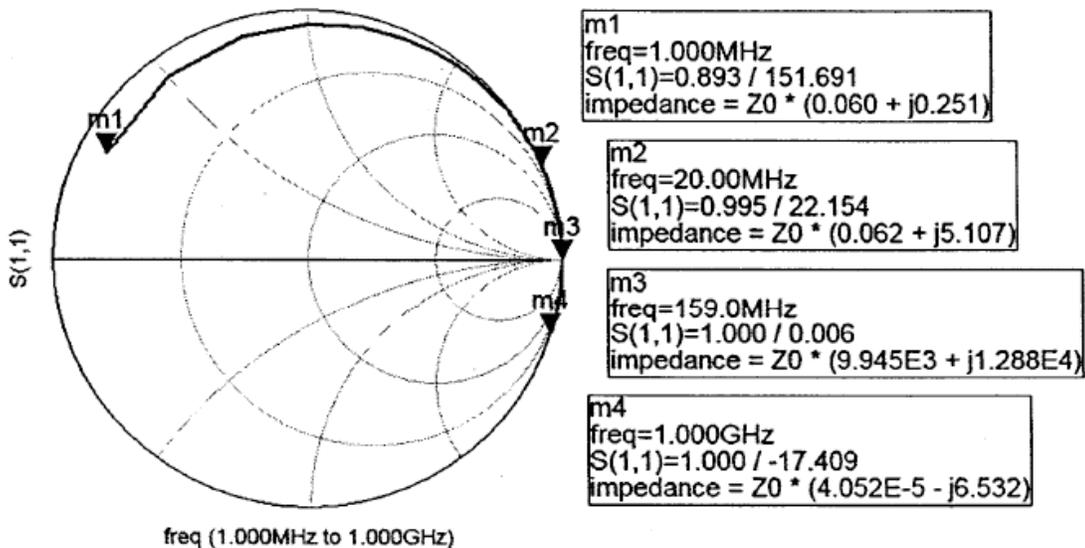
1. a. Calculate the 4 S parameters for the network below assuming a 50 ohm system characteristic impedance.
- b. Determine the transducer gain in dB in this system.



2. A component was measured on the network analyzer over the frequency range of 1 MHz to 1 GHz. S11 is plotted on the 50 ohm Smith Chart. Identify the component and construct and determine values for the equivalent circuit representing that component.



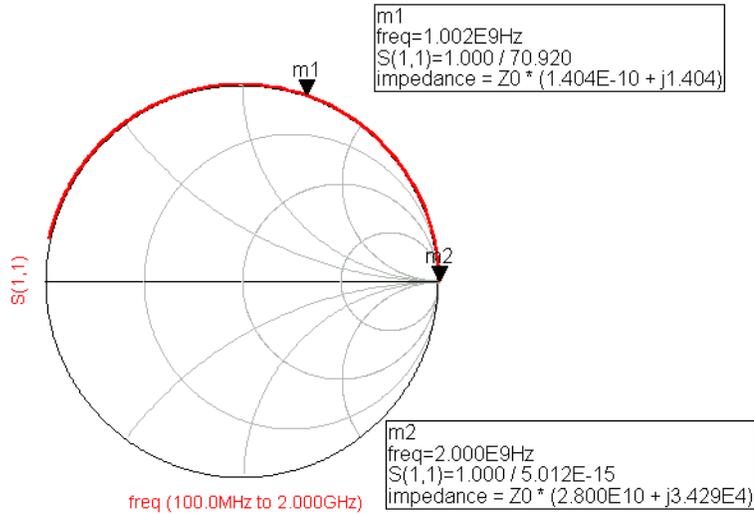
3. A shorted transmission line stub was measured on the network analyzer up to 2 GHz. From the data provided, determine the Z_0 , phase velocity and effective dielectric constant of the transmission line. The physical length is 2 cm.



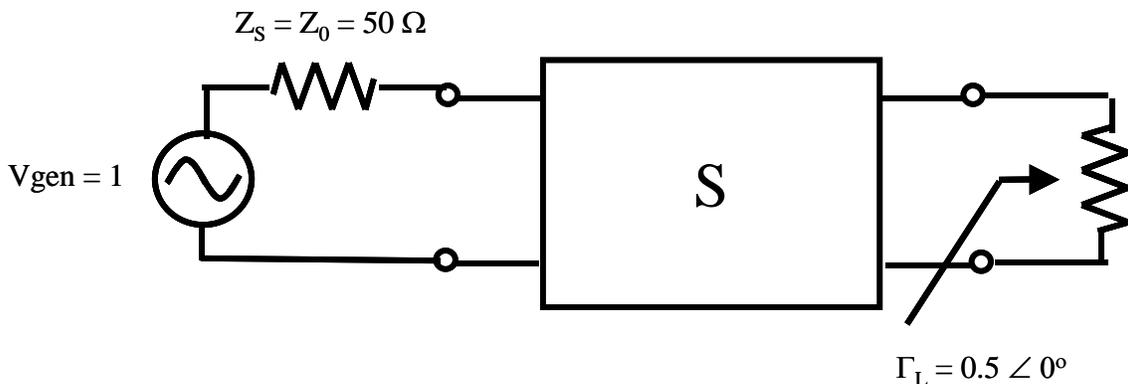4. The two port below has the following S parameters:
 $S_{11} = 0 \angle 0$ $S_{12} = 0.1 \angle 0$ $S_{21} = 3 \angle 0$ $S_{22} = 0.6 \angle 180$

$Z_0 = 50$ ohms.

- Determine the power delivered to the load, P_L , and the power reflected from the input of the network, $P_{\text{reflected}}$.
- Calculate the VSWR seen by the generator.



- Use the Smith chart (download a pdf from the course website under Smith Charts and Prototyping Guides: ZY Smith Chart) to design 4 different lumped element L networks to match a load with impedance $Z_L = 20 + j60$ to a 100 ohm source.
- Reading the Smith chart, find Γ_L .
- Determine component values for the 4 matching networks if the design frequency is 15.9 MHz.
- Read the ADS Tutorial: Basics. Download the example files in ADS Tutorial #1.
- Verify 2 of your 4 designs using ADS.