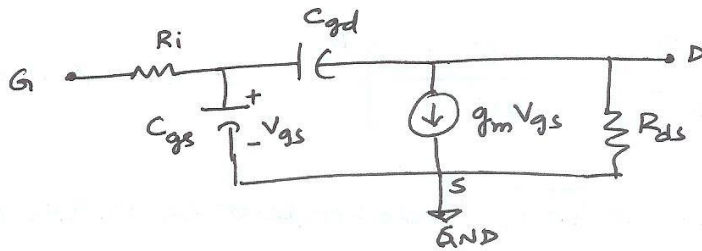


Problem - 1

1(a)



To compute MAG, match both input and o/p ports.


$$Z_{gen} = Z_{in}^* ; Z_L = Z_{out}^*$$

$$P_{in} = I_{in}^2 R_i$$

$$P_{out} = I_{out}^2 R_{ds}$$

$$\text{clearly, } Z_{gen} = R_i - \frac{1}{j\omega C_{gs}}$$

$$Z_{out} = R_{ds}$$

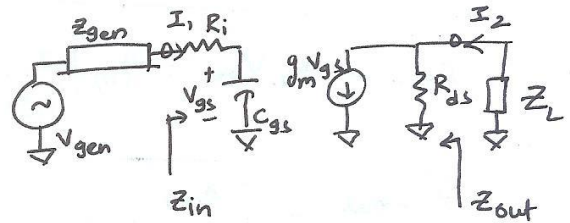

with  $C_{gd} = 0$

$$P_{out} = I_{out}^2 R_{ds} ; I_{out} = \frac{g_m V_{gs}}{2} ; V_{gs} = I_{in} \left( \frac{1}{j\omega C_{gs}} \right)$$

$$= \left[ \frac{g_m V_{gs}}{2} \right]^2 R_{ds}$$

$$\frac{P_{out}}{P_{in}} = \left[ \frac{g_m I_{in}}{2 j\omega C_{gs}} \right]^2 R_{ds} \cdot \frac{1}{I_{in}^2 R_i} = \frac{-g_m^2 R_{ds}}{4 \omega^2 C_{gs}^2 R_i}$$

$$MAG = \left| \frac{P_{out}}{P_{in}} \right| \Big|_{\substack{Z_{gen} = Z_{in}^* \\ Z_L = Z_{out}^*}} = \frac{g_m^2 R_{ds}}{4 \omega^2 C_{gs}^2 R_i}$$

$$\boxed{MAG = \frac{g_m^2 R_{ds}}{4 \omega^2 C_{gs}^2 R_i}}$$

$$MAG = 1 @ f = f_{max} \Rightarrow f_{max} = \left[ \frac{g_m^2 R_{ds}}{16 \pi^2 C_{gs}^2 R_i} \right]^{1/2}$$

$$\Rightarrow \boxed{f_{max} = \frac{g_m}{4 \pi C_{gs}} \left[ \frac{R_{ds}}{R_i} \right]^{1/2}}$$

$$\text{MAG } f_{\max} = \frac{(1.5 \text{ mS}/\mu\text{m}) \cdot W_g}{4\pi(1.0 \text{ fF}/\mu\text{m}) \cdot W_g} \left[ \frac{1}{(1/g_m) \cdot (0.1 \text{ mS}/\mu\text{m} \cdot W_g)} \right]^{1/2} \quad (2)$$


$$= \frac{1.5 \times 10^{-3}}{4\pi \times 10^{-15}} \left[ \frac{1.5}{0.1} \right]^{1/2} = 462.3 \text{ GHz}$$

$$\boxed{f_{\max} = 462.3 \text{ GHz}} \quad (\text{independent of width of gate!})$$

Short circuit current gain

$$I_{\text{out}} = g_m V_{gs} = g_m \left[ \frac{I_{\text{in}}}{j\omega C_{gs}} \right]$$
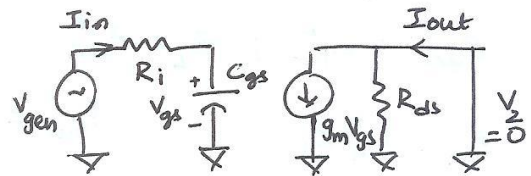
$$\Rightarrow \boxed{\frac{I_{\text{out}}}{I_{\text{in}}} = \left[ \frac{g_m}{j\omega C_{gs}} \right]}$$



SC curr gain = 1 @  $f = f_T$

$$\left| \frac{I_{\text{out}}}{I_{\text{in}}} \right|_{V_2=0} = \frac{g_m}{\omega_T C_{gs}} = 1$$

$$\Rightarrow f_T = \frac{g_m}{2\pi C_{gs}}$$

$$= \frac{1.5 \text{ mS}/\mu\text{m} \cdot W_g}{2\pi \cdot 1.0 \text{ fF}/\mu\text{m} \cdot W_g}$$

$$\boxed{f_T = 238.73 \text{ GHz}}$$

1(b)

$$\textcircled{a} \frac{f_{\max}}{10} = 46.23 \text{ GHz}$$

$$Z_{\text{gen}} = Z_{\text{in}}^*$$

$$Z_{\text{out}}^* = Z_L = R_{\text{ds}}$$

$$Z_{\text{in}}^* = R_i - \frac{1}{j\omega C_{\text{gs}}}$$

$$W_g = 100 \mu\text{m} \quad \textcircled{3}$$

$$R_i = 1/g_m = 6.67 \Omega$$

$$g_m = 1.5 \text{ mS}/\mu\text{m} \cdot W_g = 150 \text{ mS}$$

$$C_{\text{gs}} = 1.0 \text{ fF}/\mu\text{m} \cdot W_g = 100 \text{ fF}$$


$$G_{\text{ds}} = \frac{1}{R_{\text{ds}}} = 0.1 \text{ mS}/\mu\text{m} \cdot W_g$$
$$= 10 \text{ mS} \Rightarrow R_{\text{ds}} = 100 \Omega$$

$$j\omega C_{\text{gs}} = j0.0628 \text{ S}$$

$$Z_{\text{gen}} = 6.67 \Omega - \frac{1}{j0.063 \text{ S}} = (6.67 + j15.873) \Omega$$


$$Z_{\text{out}} = 100 \Omega$$

1(c)

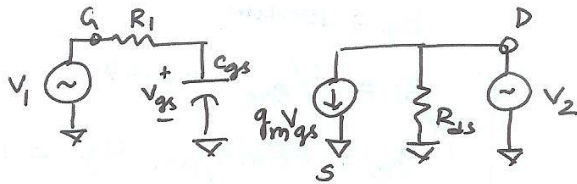

To calculate  $Y_{11}, Y_{21}$   
Set  $V_2 = 0$

$$Y_{11} = \frac{I_1}{V_1} \Big|_{V_2=0} \quad Y_{21} = \frac{I_2}{V_1} \Big|_{V_2=0}$$

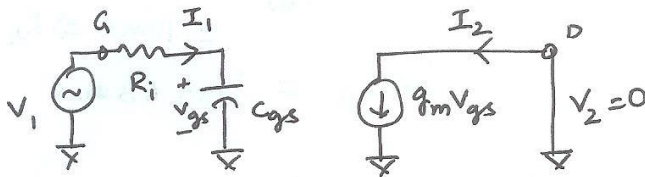

$R_{ds}$  is shorted too!


$$\frac{I_1}{V_1} = \frac{V_1}{R_i + (1/j\omega C_{gs})} \Rightarrow Y_{11} = \frac{1}{R_i + (1/j\omega C_{gs})} = \frac{j\omega C_{gs}}{1 + j\omega R_i C_{gs}}$$

$$Y_{11} = \frac{j\omega C_{gs}}{1 + j\omega R_i C_{gs}}$$

$$I_2 = g_m V_{gs} ; \quad V_{gs} = \frac{V_1 (1/j\omega C_{gs})}{R_i + (1/j\omega C_{gs})} = \frac{V_1}{1 + j\omega R_i C_{gs}}$$

$$\Rightarrow Y_{21} = \frac{g_m}{1 + j\omega R_i C_{gs}}$$

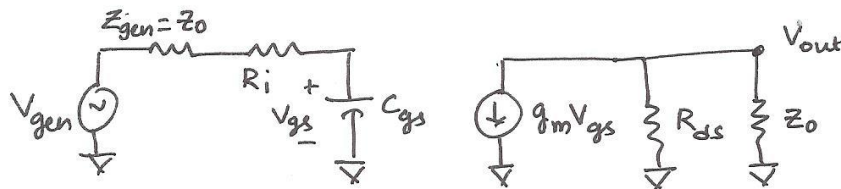$S_{21}$ :  $Z_{gen} = Z_L = Z_0 ; \quad S_{21} = \frac{2V_{out}}{V_{gen}}$



(5)

$$V_{out} = -g_m V_{gs} [R_{ds} \parallel Z_o]$$

$$V_{gs} = \frac{V_{gen} \left( \frac{1}{j\omega C_{gs}} \right)}{(Z_o + R_i) + \left( \frac{1}{j\omega C_{gs}} \right)} = \frac{V_{gen}}{1 + j\omega C_{gs} (R_i + Z_o)}$$

$$\Rightarrow V_{out} = \frac{-g_m V_{gen} \cdot R_{ds} Z_o}{[1 + j\omega C_{gs} (R_i + Z_o)]} \cdot \frac{1}{[R_{ds} + Z_o]}$$

$$\boxed{\frac{2V_{out}}{V_{gen}} = S_{21} = \frac{-2g_m}{1 + j\omega C_{gs} (R_i + Z_o)} \cdot [R_{ds} \parallel Z_o]}$$

1(d)  $f = 100 \text{ GHz}$ ;  $g_m = 1.5 \text{ ms}/\mu\text{m} \cdot W_g = 0.15 \text{ S} = 150 \text{ ms}$

$W_g = 100 \mu\text{m}$ ;  $R_i = 6.67 \Omega$

$Z_o = 50 \Omega$ ;  $C_{gs} = 1 \text{ fF}/\mu\text{m} \cdot W_g = 100 \text{ fF}$

$g_{ds} = 0.1 \text{ ms}/\mu\text{m} \cdot W_g = 10 \text{ ms} \Rightarrow R_{ds} = \frac{1}{10 \text{ ms}} = 100 \Omega$

$j\omega C_{gs} = j0.063 \text{ S}$

(i) Insertion Power gain:  $|S_{21}|^2$  Gain with  $50 \Omega$  source, Load Impedance.

$$S_{21} = \frac{-2 \times 0.15 \text{ S}}{1 + j0.063 (56.67)} \cdot [100 \Omega \parallel 50 \Omega] \quad \left\{ \text{from (c)} \right\}$$


$$= \frac{-0.3 \times \left( \frac{100}{3} \right)}{1 + j3.56} = \frac{-10}{1 + j3.56}$$

$$||S_{21}||^2 = \left[ \frac{10}{\sqrt{1 + (3.56)^2}} \right]^2 = \frac{100}{1 + 12.678} = 7.31$$

$$10 \cdot \log ||S_{21}||^2 \approx \boxed{8.64 \text{ dB} = G_i}$$

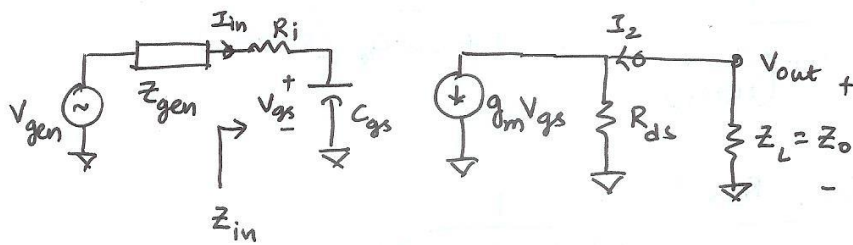(i) operating power gain :  $G_p$  : Gain w/ input matched.

$$Z_{gen} = Z_{in}^* ; Z_L = Z_o = 50\Omega$$



AS in pr #1,  $P_{in} = |I_{in}^2 R_i|$  and  $I_{in} = V_{gs} (j\omega C_{gs})$

$$\Rightarrow \frac{1}{4} P_{in} = \omega^2 C_{gs}^2 V_{gs}^2 R_i$$

$$P_{out} = I_{out}^2 Z_L = \left[ g_m V_{gs} \cdot \frac{R_{ds}}{R_{ds} + Z_o} \right]^2 \times Z_o$$

current divider

$$G_p = \frac{P_{out}}{P_{in}} = \frac{g_m^2 V_{gs}^2 R_{ds}^2 Z_o}{(R_{ds} + Z_o)^2 \omega^2 C_{gs}^2 V_{gs}^2 R_i}$$

$$G_p = \left[ \frac{g_m R_{ds}}{(R_{ds} + Z_o) \omega C_{gs}} \right]^2 \times \frac{Z_o}{R_i}$$

@ 100kHz  $G_p = \left[ \frac{0.15 \times 100}{150 \times 0.063} \right]^2 \times \frac{50}{6.67} = 18.89$

$$10 \log_{10}(G_p) = 12.76 \text{ dB}$$

$$G_p = 12.76 \text{ dB}$$

(ii) Available Power Gain :  $G_a$  : Gain w/ output matched =  $\frac{P_{av, amp}}{P_{av, gen}}$


$$P_{out} = \frac{1}{4} g_m^2 V_{gs}^2 R_{ds} \quad \left\{ \text{same as MAG's } P_{out} \right\}$$

see 1(a)

$$V_{gs} = I_{in} / j\omega C$$
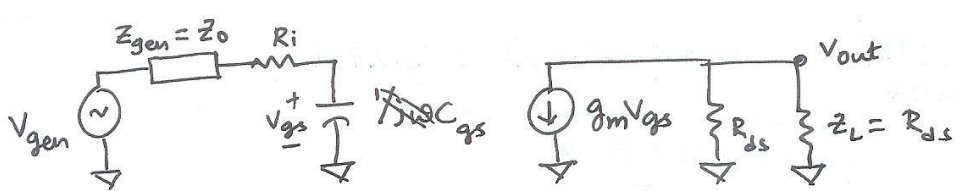
$$I_{in} = \frac{V_{gen}}{Z_{gen} + Z_{in}} = \frac{V_{gen}}{Z_o + R_i + \frac{1}{j\omega C}}$$





(2)

$$\Rightarrow V_{gs} = \frac{V_{gen}}{1 + j\omega C (R_i + Z_0)}$$

$$\text{and } P_{out} = \frac{\frac{1}{4} g_m^2 V_{gen}^2 R_{ds}}{(1 + j\omega C (R_i + Z_0))^2}$$

$$P_{in} = P_{av, gen} = \frac{1}{4} \frac{V_{gen}^2}{Z_0}$$

$$G_a = \frac{P_{out}}{P_{in}} = \frac{\frac{1}{4} g_m^2 V_{gen}^2 R_{ds} Z_0}{\frac{1}{4} V_{gen}^2 [(1 + j\omega C (R_i + Z_0))]^2}$$

$$G_a = \frac{g_m^2 R_{ds} Z_0}{[1 + j\omega (R_i + Z_0) C]^2}$$

$$\text{@ } 100 \text{ GHz, } |G_a| = \frac{0.15 \times 100 \times 50 \times 0.15}{1 + (\omega C_{gs})^2 (R_i + Z_0)^2}$$

$$= \frac{750 \times 0.15}{1 + [0.063 \times 56.67]^2}$$

$$= \frac{750 \times 0.15}{13.678} = \frac{54.83}{13.678} = 8.2245$$

$$G_a |_{dB} = 10 \log_{10} (8.2245) = 17.939 \text{ dB} \quad 9.151$$

$$\boxed{G_a = 17.939 \text{ dB}}$$

$$\boxed{G_a = 9.151 \text{ dB}}$$

$$\text{(ii) From 1(a), MAG @ } 100 \text{ GHz} = \frac{g_m^2 R_{ds}}{4 \omega^2 C_{gs}^2 R_i} = \frac{0.15 \times 0.15 \times 100}{4 (0.063)^2 \times 6.67} = 21.24$$

$$\text{MAG} \Big|_{f=100\text{kHz}} \text{ (dB)} = 10 \log_{10} (21.24) = 13.27 \text{ dB}$$

⑧

$$\boxed{\text{MAG} = 13.27 \text{ dB}}$$

All the calculated values match well with simulated values.

2.  $S_{11} = 0.5$

$$S_{22} = 0.7071$$

$$S_{12} = 0$$

$$S_{21} = 10$$

(a)  $Z_{\text{gen}} = 50 \Omega$

$$P_{\text{av, gen}} = 1 \text{ mW}$$

$$Z_L = Z_0 = 50 \Omega$$

$$\text{Insertion Gain} = \frac{|S_{21}|^2}{|S_{11}|^2} = \frac{\text{Power delivered to } Z_0 \text{ Load}}{\text{Power available from } Z_0 \text{ generator}}$$

( $Z_s = Z_L = Z_0$ )

$$\text{Power delivered to } Z_0 \text{ load} = \underline{\underline{0.1 \text{ W}}}$$

(b)  $Z_{\text{gen}} = 75 \Omega ; Z_L = 25 \Omega$

$$\Gamma_s = \frac{75-50}{75+50}$$

$$= \frac{1}{5}$$

$$\Gamma_L = \frac{25-50}{25+50}$$

$$= -\frac{1}{3}$$

$$G_T = \frac{|S_{21}|^2 (1-|\Gamma_s|^2) (1-|\Gamma_L|^2)}{|(1-\Gamma_s S_{11})(1-\Gamma_L S_{22}) - S_{21} S_{12} \Gamma_s \Gamma_L|^2}$$


substituting the values,

$$G_T = \frac{(10)^2 \left(1 - \frac{1}{25}\right) \left(1 - \frac{1}{9}\right)}{\left| \left(1 - \left(\frac{1}{5}\right)(0.5)\right) \left(1 - \left(-\frac{1}{3}\right)\left(\frac{1}{\sqrt{2}}\right)\right) \right|^2} = 69.25$$

$$\text{Power delivered to load} \rightarrow 69.25 \text{ mW}$$



Problem 1(d)

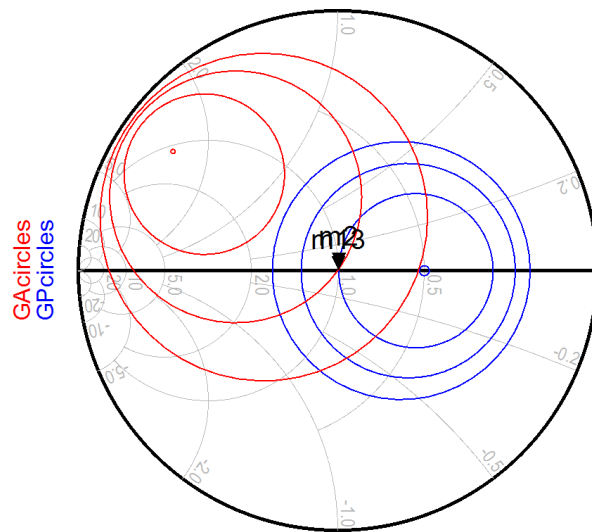

m2  
 indep(m2)=25  
 GPcircles=0.019 / 78.351  
 gain=12.793631  
 impedance = Z0 \* (1.007 + j0.037)


m13  
 indep(m13)=46  
 GAcircles=0.005 / 60.020  
 gain=9.153631  
 impedance = Z0 \* (1.005 + j0.008)

cir\_pts (0.000 to 51.000)

- Eqn GAstep\_size=2.07    Eqn GPstep\_size=0.5    Eqn InsertionGain= mag(S(2,1))\*\*2  
 Eqn num\_GAcircles=3    Eqn num\_GPcircles=3    Eqn InsertionGaindB = 10\*log10(InsertionGain)

freq	InsertionGain	InsertionGaindB	MaxGain
100.0 GHz	7.310	8.639	13.296

Problem 1(e)

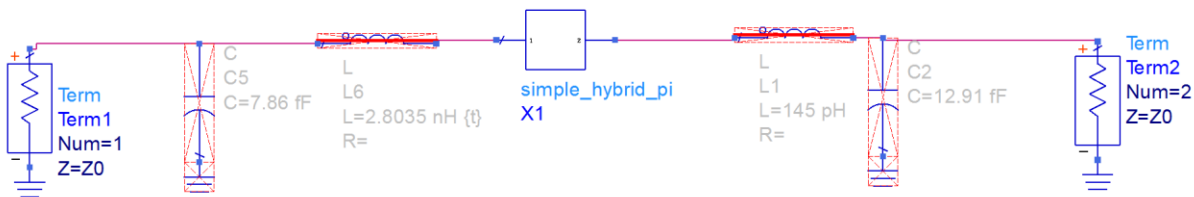


Var  
 Eqn VAR  
 VAR3  
 Z0=50

S-PARAMETERS

S\_Param  
 SP1  
 Start=9 GHz  
 Stop=11 GHz  
 Step=0.1 GHz  
 CalcNoise=yes  
 Freq=

S(1,1), S(2,2) Before Matching

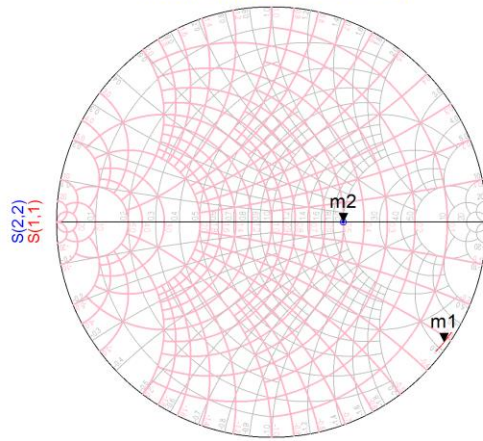


m1  
freq=10.00GHz  
S(1,1)=0.976 / -34.831  
admittance =  $Y_0 * (0.013 + j0.314)$

m2  
freq=10.00GHz  
S(2,2)=0.333 / -0.004  
impedance =  $Z_0 * (2.000 - j1.074E-4)$

freq (9.000GHz to 11.00GHz)

**MATCHING PART - 1:**

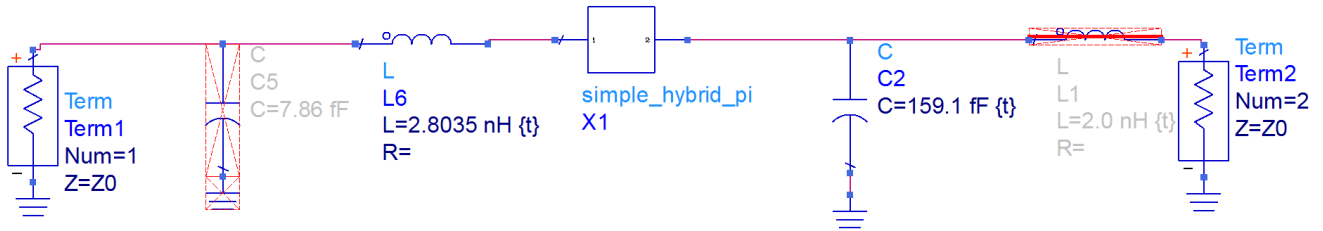

Var Egn VAR3  
Z0=50

**S-PARAMETERS**

S\_Param  
SP1  
Start=9 GHz  
Stop=11 GHz

**C2.C**  
(fF)

Value: 159.1

Max: 200

Min: 0

Step: 0.1

Scale: Lin

**L6.L**  
(nH)

Value: 2.8035


Max: 5

Min: 0

Step: 0.1

Scale: Lin

S(1,1), S(2,2) Matching - 1

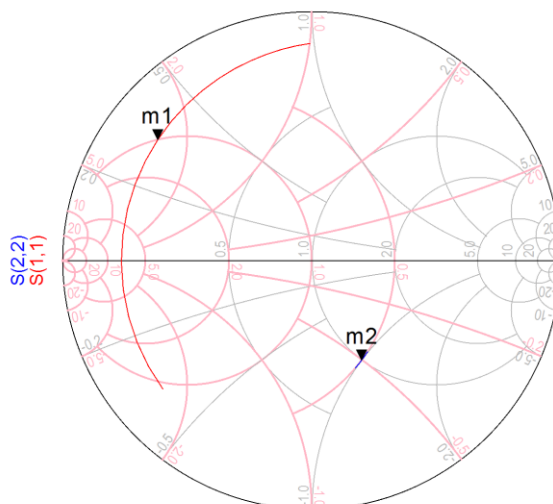


m1  
freq=10.00GHz  
S(1,1)=0.787 / 141.873  
admittance =  $Y_0 * (1.000 - j2.548)$

m2  
freq=10.00GHz  
S(2,2)=0.447 / -63.443  
impedance =  $Z_0 * (1.000 - j1.000)$

freq (9.000GHz to 11.00GHz)

## MATCHING PART – 2:

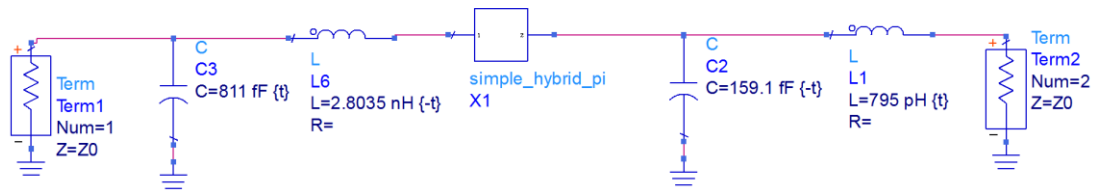

VAR  
Eqn  
VAR3  
Z0=50

S-PARAMETERS

S\_Param  
SP1  
Start=9 GHz  
Stop=11 GHz  
Step=0.1 GHz  
CalcNoise=yes  
Freq=

**C3.C**  
(fF)

Value: 811

Max: 1000

Min: 0

Step: 0.1

Scale: Lin

**L1.L**  
(pH)

Value: 795


Max: 1000

Min: 0

Step: 1



Scale: Lin

S(1,1) and S(2,2) Matching -2

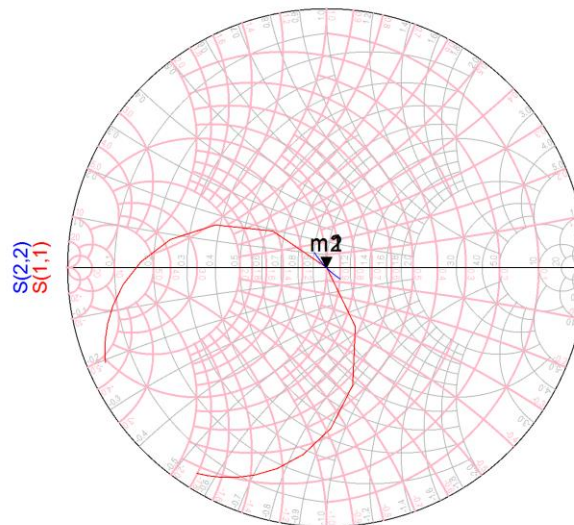

m1  
freq=10.00GHz  
S(1,1)=3.809E-4 / 10.231  
impedance = Z0 \* (1.001 + j1.354E-4)

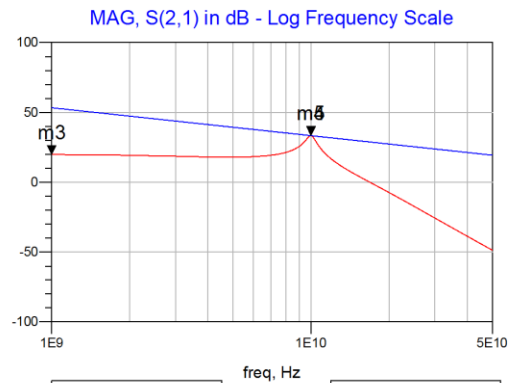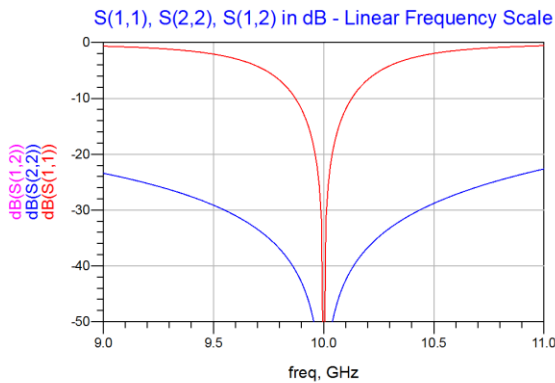m2  
freq=10.00GHz  
S(2,2)=8.340E-4 / -150.349  
impedance = Z0 \* (0.999 - j8.239E-4)



m3  
freq=1.000GHz  
dB(S(2,1))=19.762

m4  
freq=10.00GHz  
dB(S(2,1))=33.296

m5  
freq=10.00GHz  
10\*log10(MAG)=33.296 / 0.000

Eqn  $MAG = (StabFact1 - \sqrt{StabFact1^2 - 1}) * \text{mag}(S(2,1)) / \text{mag}(S(1,2))$

2(c) Gain w/ input matched,  $\Rightarrow$  operating power gain,  $G_p$

$$G_p = \frac{1}{1 - |\Gamma_{in}|^2} \cdot |S_{21}|^2 \frac{1 - |\Gamma_L|^2}{|1 - \Gamma_L S_{22}|^2}$$

$\because$  the device is unilateral, i.e.,  $S_{12} = 0$ ,

$$\textcircled{1} \Gamma_{in} = S_{11} + \frac{S_{21} S_{12} \Gamma_L}{1 - S_{22} \Gamma_L} = S_{11} = 0.15$$

$$\left[ \text{and } \Gamma_{out} = S_{22} + \frac{S_{21} S_{12} \Gamma_S}{1 - S_{11} \Gamma_S} = S_{22} = 0.707 \right]$$

$$\textcircled{2} \Gamma_L = \frac{Z_L - Z_0}{Z_L + Z_0} = \frac{30 - 50}{30 + 50} = -0.25$$


$$\begin{aligned} \Rightarrow G_p &= \frac{1}{1 - 0.25} \cdot 100 \cdot \frac{1 - (-0.25)^2}{|1 - (-0.25)(0.707)|^2} \\ &= \frac{4}{3} \cdot 100 \cdot \frac{\left(1 - \frac{1}{16}\right)}{\left(1 + \frac{1}{4\sqrt{2}}\right)^2} = \frac{400 \times \sqrt{3}}{16 \times 3} = \frac{4000}{(4\sqrt{2} + 1)^2} = \frac{4000}{16 \times 2} \\ &= \frac{4000}{33 + 8\sqrt{2}} \end{aligned}$$

$$G_p = 103.476$$

$$\Rightarrow \text{o/p Power} = 103.476 \text{ mW}$$

$$P_{out} \approx 0.103 \text{ W}$$

2(d)

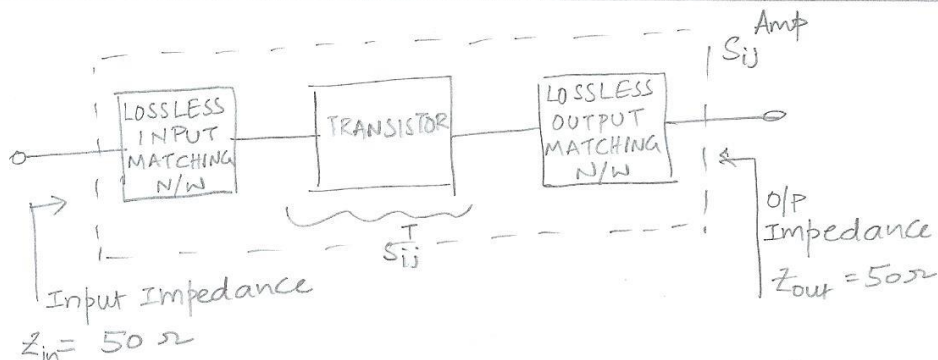

We will find S-params of this n/w & use them to find  $P_{out}$  for given  $Z_{gen}, Z_L$

Since the transistor is already matched at the input and output to  $50\Omega$ , the input and output reflection coefficients of the total network,  $S_{11}^{\text{Amp}} = S_{22}^{\text{Amp}} = 0$ . Since the network is unilateral,  $S_{12}^{\text{Amp}} = 0$ . We need to find  $S_{21}^{\text{Amp}}$ .

$$\text{For a unilateral device, } G_{\text{Max}}^{\text{Trans}} = \frac{1}{1 - |S_{11}^{\text{Trans}}|^2} |S_{21}^{\text{Trans}}|^2 \frac{1}{1 - |S_{22}^{\text{Trans}}|^2}$$

$$= \frac{1}{1 - (0.15)^2} \cdot (10)^2 \frac{1}{1 - \left(\frac{1}{\sqrt{2}}\right)^2}$$

$$G_{\text{Max}}^{\text{Trans}} = \frac{4}{3} \times 100 \times 2$$

$$= 100 \left[ \frac{8}{3} \right]$$

By definition,  $G_{\text{Max}}^{\text{Trans}} = G_{\text{Max}}^{\text{Amp}}$

$$\text{So, } \frac{1}{1 - |S_{11}^{\text{Amp}}|^2} |S_{21}^{\text{Amp}}|^2 \frac{1}{1 - |S_{22}^{\text{Amp}}|^2} = 100 \left[ \frac{8}{3} \right]$$

$$\because S_{11}^{\text{Amp}} = S_{22}^{\text{Amp}} = 0 \Rightarrow S_{21}^{\text{Amp}} = 10 \sqrt{\frac{8}{3}}$$

$$\Rightarrow [S]^{\text{Amp}} = \begin{bmatrix} 0 & 0 \\ 10\sqrt{\frac{8}{3}} & 0 \end{bmatrix}$$

Now, with  $Z_{\text{gen}} = 25\Omega$ ,  $\Gamma_s = \frac{25 - 50}{25 + 50} = -\frac{1}{3}$

and  $Z_L = 100\Omega$ ,  $\Gamma_L = \frac{100 - 50}{100 + 50} = \frac{1}{3}$

$$\Rightarrow G_T^{\text{Amp}} = \frac{|S_{21}^{\text{Amp}}|^2 [1 - |\Gamma_s|^2] [1 - |\Gamma_L|^2]}{|(1 - \Gamma_s S_{11}^{\text{Amp}})(1 - \Gamma_L S_{22}^{\text{Amp}}) - S_{21}^{\text{Amp}} S_{12}^{\text{Amp}} \Gamma_s \Gamma_L|^2}$$


$$= 100 \cdot \left(\frac{8}{3}\right) \cdot \left(1 - \frac{1}{9}\right)^2 \quad \left\{ \because S_{11}^{\text{Amp}} = S_{22}^{\text{Amp}} = S_{12}^{\text{Amp}} = 0 \right\}$$

$$= 100 \cdot \frac{8}{3} \cdot \frac{64}{81} \approx 210.7 \Rightarrow \boxed{P_{\text{Load}} = 210.7 \text{ mW}} = 0.21 \text{ W}$$




Pr-4:  $[S]_{\text{laser}} = \begin{bmatrix} 0.1 & 10 \\ 10 & 0.1 \end{bmatrix}$ ;  $[S]_{\text{iso}} = \begin{bmatrix} 0 & 0.25 \\ 0.25 & 0 \end{bmatrix}$ ;  $[S]_{\text{att}} = \begin{bmatrix} R & T \\ T & R \end{bmatrix}$

Drawing the signal flow graph,

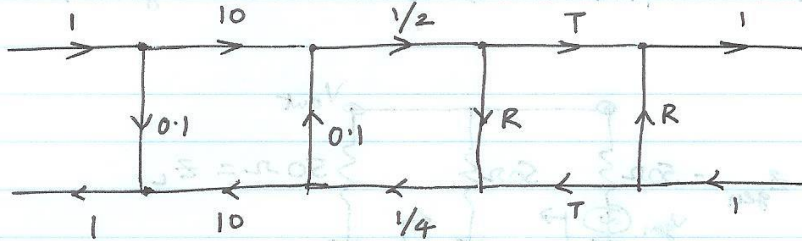

Only 1 loop in the path,

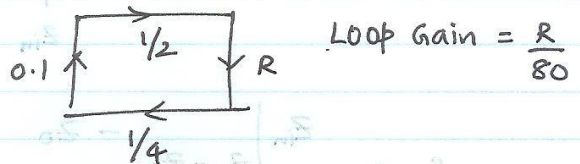


$$\rightarrow S_{21} = \frac{\text{Forward Gain}}{1 - \text{Loop Gain}} = \frac{[1 * 10 * \frac{1}{2} * T * 1]}{1 - \frac{R}{80}} = \frac{5T}{1 - \frac{R}{80}}$$

$$\rightarrow S_{11} = \text{Sum of 2 reflection paths} = 0.1 + \frac{10 * \frac{1}{2} * R * \frac{1}{4} * 10}{1 - \frac{R}{80}} = 0.1 + \frac{100R/8}{1 - \frac{R}{80}}$$


$$\rightarrow S_{22} = R + \frac{T * \frac{1}{4} * 0.1 * \frac{1}{2} * T}{1 - \frac{R}{80}} = R + \frac{T^2/80}{1 - \frac{R}{80}}$$

$$\rightarrow S_{12} = \frac{T * \frac{1}{4} * 10}{1 - \frac{R}{80}} = \frac{2.5T}{1 - \frac{R}{80}}$$

Pr-3 (a)

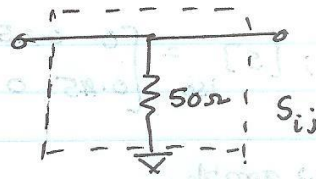

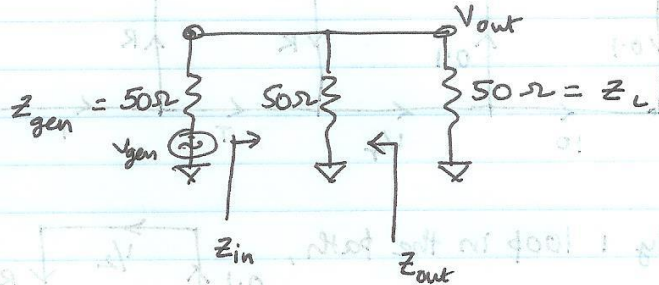Calculate S-parameters with a 50 ohm system



$$S_{11} = \frac{Z_{in} \Big|_{Z_L = Z_0} - Z_0}{Z_{in} \Big|_{Z_L = Z_0} + Z_0} ; Z_{in} \Big|_{Z_L = Z_0} = 25 \Omega$$

$$= \frac{-25}{75} = -0.33 \quad \boxed{S_{11} = -0.33}$$

Similarly,

$$S_{22} = \frac{Z_{out} \Big|_{Z_{gen} = Z_0} - Z_0}{Z_{out} \Big|_{Z_{gen} = Z_0} + Z_0} ; Z_{out} \Big|_{Z_{gen} = Z_0} = 25 \Omega$$

$$\boxed{S_{22} = -0.33}$$

$$S_{21} = \frac{2V_{out}}{V_{gen}} \Big|_{Z_L = Z_{gen} = Z_0}$$

$$V_{out} = \frac{V_{gen} [50 \parallel 50] \Omega}{(50 + [50 \parallel 50]) \Omega} = \frac{V_{gen}}{3}$$


$$\Rightarrow S_{21} = \frac{2}{3} = 0.67$$

$$\boxed{S_{21} = 0.67}$$


$S_{12} \rightarrow$  Circuit is symmetrical  $\Rightarrow S_{12} = S_{21} = \frac{2}{3} = 0.67$

$$[S]_{ij} = \begin{matrix} \text{(Res)} \\ \text{(Res)} \end{matrix} \begin{bmatrix} -0.33 & 0.67 \\ 0.67 & -0.33 \end{bmatrix}$$

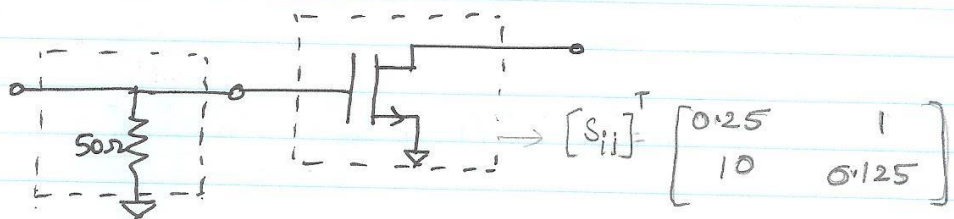
(b) Resistor is connected b/w FET input and GND. Find S-parameter of Combined N/w



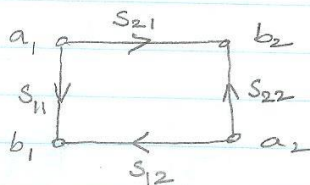
SAMPLE SIGNAL FLOW GRAPH FOR A 2-PORT N/w



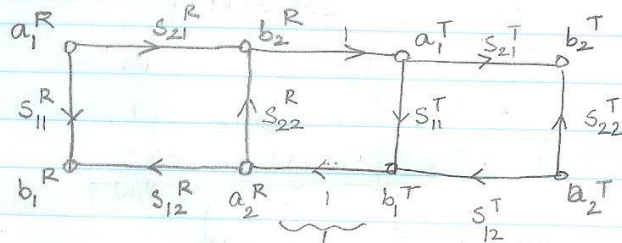COMBINED N/W OF THE RESISTOR AND TRANSISTOR



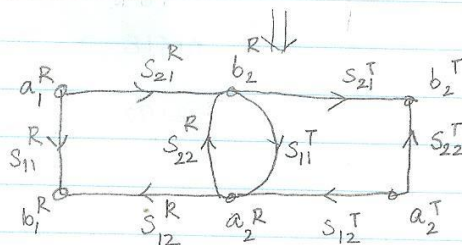Indicating Direct Connection (NO DELAYS!)



$$\begin{array}{l|l} S_{11} = \frac{b_1^R}{a_1^R} & S_{12} = \frac{b_1^R}{a_2^T} \\ S_{22} = \frac{b_2^T}{a_2^T} & S_{21} = \frac{b_2^T}{a_1^R} \end{array}$$

Use Mason's GAIN RULE, 
$$\frac{P_1 [1 - \sum L(1) + \sum L(2) + \dots] + P_2 [1 - \sum L^2(1) + \sum L^2(2) + \dots] + \dots}{1 - \sum L(1) + \sum L(2) - \sum L(3) + \dots}$$



EASE OF CALCULATION: ONLY ONE LOOP

$$\frac{1}{1 - S_{22}^R S_{11}^T} \rightarrow \frac{1}{1 - \left(-\frac{1}{3}\right)\left(\frac{1}{4}\right)} = \frac{12}{13} = \underline{\underline{0.923}}$$

Using the above rule, s-parameters of the new N/W will be computed.

$$S_{11} = \frac{S_{11}^R [1 - S_{22}^R S_{11}^T] + S_{21}^R S_{11}^T S_{12}^R}{1 - S_{22}^R S_{11}^T}$$

$$S_{11} = S_{11}^R + \frac{S_{21}^R S_{11}^T S_{12}^R}{1 - S_{22}^R S_{11}^T} = -0.33 + (0.67)(0.25)(0.67)(0.923)$$

$$S_{11}^{N/W} = -0.225$$

$$S_{22} = \frac{S_{22}^T [1 - S_{11}^T S_{22}^R] + S_{12}^T S_{22}^R S_{21}^T}{1 - S_{11}^T S_{22}^R}$$

$$S_{22} = S_{22}^T + \frac{S_{12}^T S_{22}^R S_{21}^T}{1 - S_{11}^T S_{22}^R} = (0.125) + (1)(-0.33)(10)(0.923)$$

$$S_{22}^{N/W} = -2.92$$

$$S_{21} = \frac{S_{21}^R S_{21}^T}{1 - S_{11}^T S_{22}^R} = (0.67)(10)(0.923)$$

$$S_{21}^{N/W} = 6.18$$

$$S_{12} = \frac{S_{12}^T S_{12}^R}{1 - S_{11}^T S_{22}^R} = (1)(0.67)(0.923)$$

$$S_{12}^{N/W} = 0.618$$

$$[S_{ij}]^{N/W} = \begin{bmatrix} -0.225 & 0.618 \\ 6.18 & -2.92 \end{bmatrix}$$