

ECE137B Notes set 6: Method of time constants

General circuit transfer function:

$$\frac{\overline{v_o}}{\overline{v_{in}}} = \frac{\overline{v_o}}{\overline{v_{in}}} \bigg|_{ms} \frac{1 + b_1 A + b_2 A^2 + \dots}{1 + a_1 A + a_2 A^2 + \dots}$$



Methods of solution

- Nodal analysis: hard to do for complex ckts
answers often hard to interpret
- Miller Approximations: intuitive
often very wrong
- SPICE: equivalent to randomly building and testing.
zero understanding.
SPICE is for design verification, not synthesis.

• Time constant method.


exact - for the information it gives
easy and fast
answers often physically interpretable

let us start with a specific π circuit:

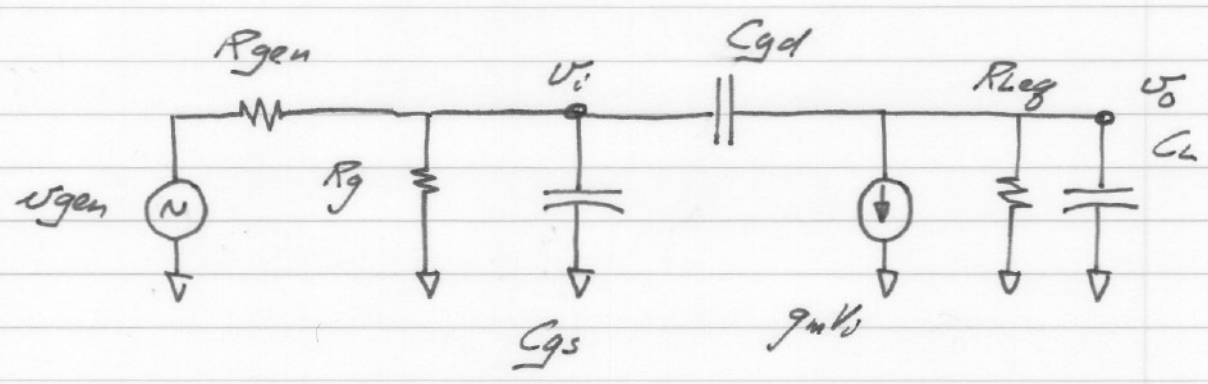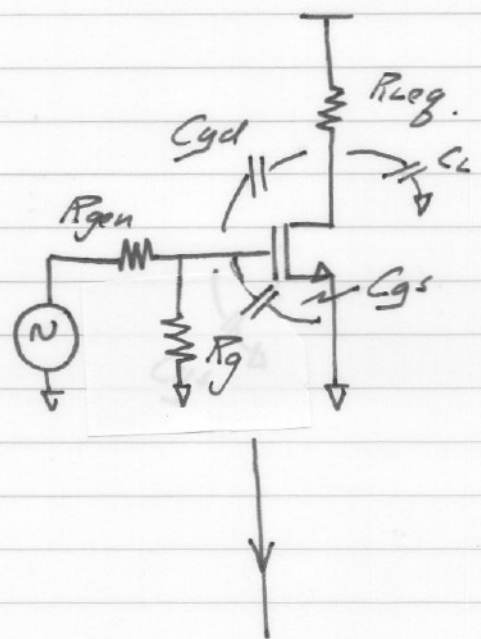


turn off independent voltage sources \rightarrow short circuits
 turn off independent current sources \rightarrow open circuits
 dependent sources must be kept.

General picture: C_2 ports

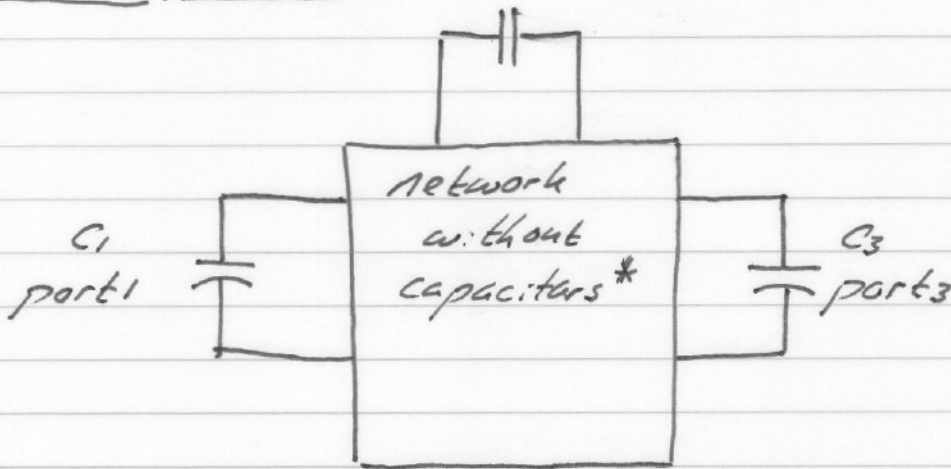

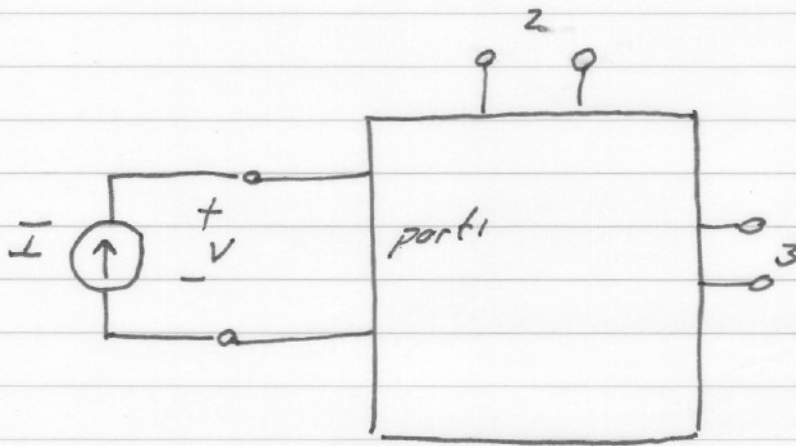Define R_{11}° : resistance at port 1 with all capacitors replaced with open circuits



$$R_{11}^{\circ} \triangleq V / I$$

(one can also force a voltage & measure I)



* inductors, transmission lines, time delay elements, or anything with frequency dependence is not allowed.

It can be shown that


$$a_1 = R_{11}^o C_1 + R_{22}^o C_2 + R_{33}^o C_3 + \dots$$

these are called the open circuit time constants.

Example:

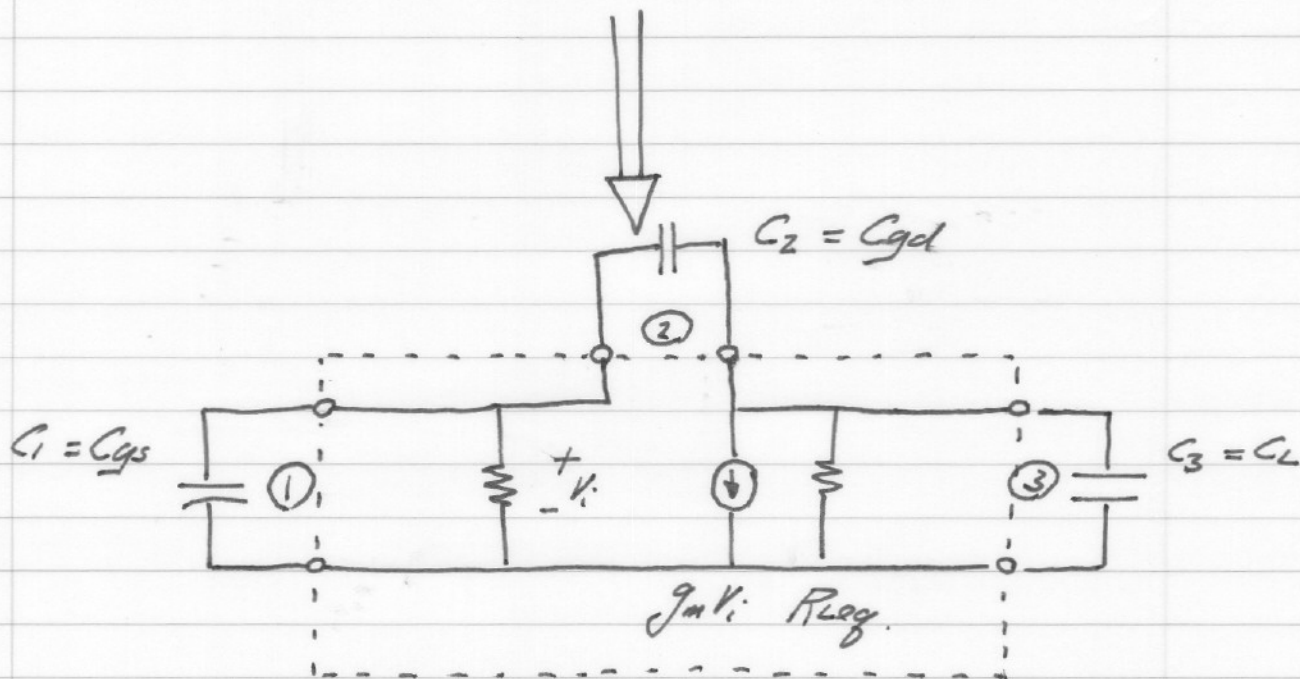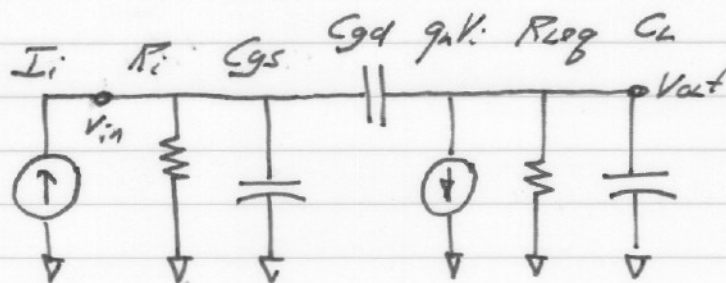

What is R_{11}^0 ? - easy!

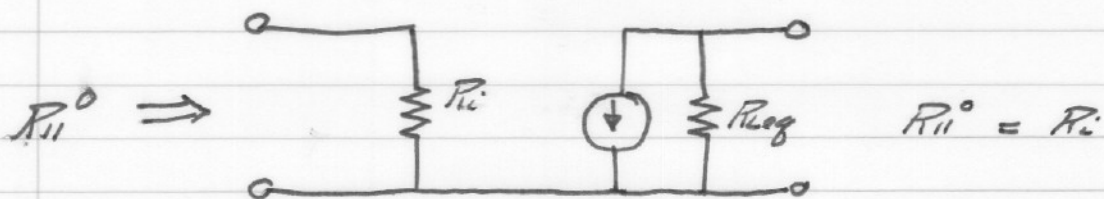

- so, first time constant is $C_{gs} R_i$


What is R_{33}^0 ? - easy!





so, third time constant is $R_{eq} C_L$

what is R_{22}^o ? - harder

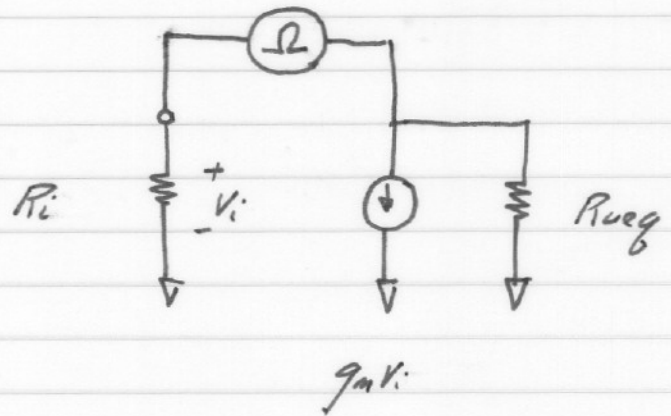
we are faced with analyzing this problem:



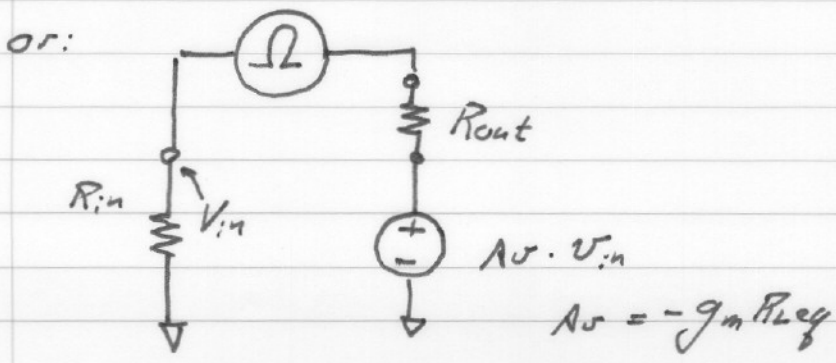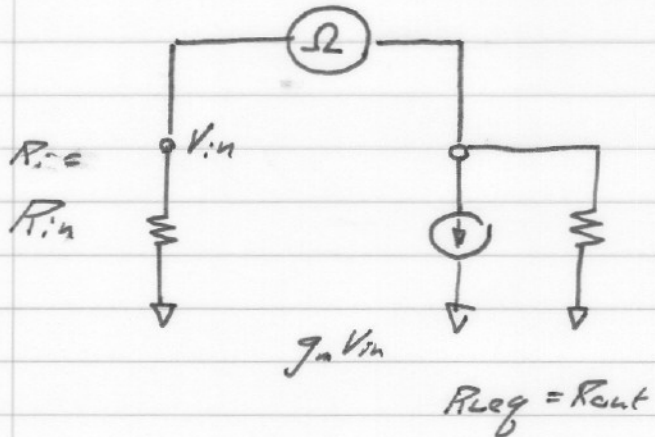- this situation is going to show up with common emitter/source and common collector/drain.
- Let us analyze the problem once in a general way.



6

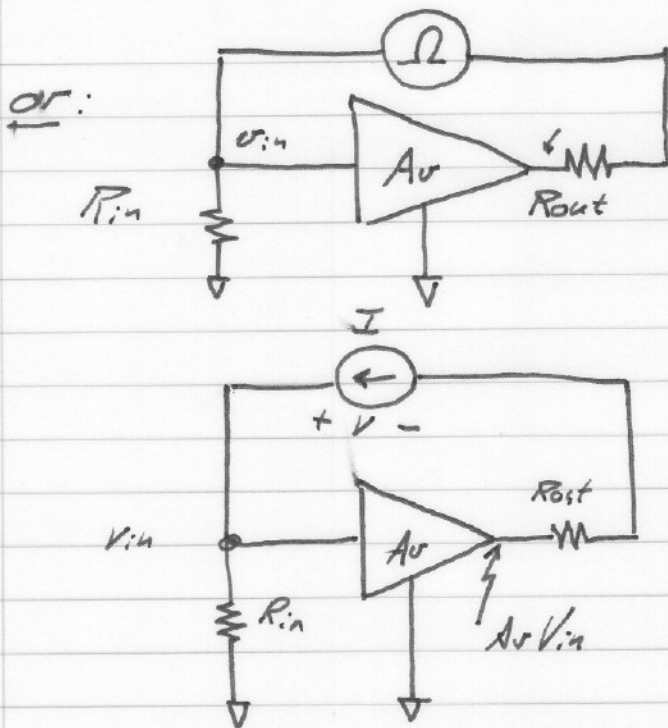

the 3 diagrams are equivalent.

$V_{in} = R_{in} \cdot I,$
 voltage at amplifier output = $+A_v R_{in} \cdot I$
 voltage drop across $R_{out} := I \cdot R_{out}$

$$\Rightarrow V = I \cdot R_{in} - I \cdot R_{in} \cdot A_v + I \cdot R_{out}$$

$$\Rightarrow R_{22}^{\circ} = R_{in} (1 - A_v) + R_{out}$$

general answer.
similar to Miller Effect

For our specific common-source example:

$$R_{22}^{\circ} = R_i (1 + g_m R_{leg}) + R_{leg}$$

we will use the general form several times.

so the second time constant is $C_{gd} \cdot R_{22}^{\circ}$

e.g. $C_{gd} \cdot [R_i(1 + g_m R_{leg}) + R_{leg}]$

The sum of time constants is

$$\tau_1 = R_i C_{gs} + R_{leg} C_E + C_{gd} [R_i(1 + g_m R_{leg}) + R_{leg}]$$

Recognize that this is the same as that found by nodal analysis.

What about higher order poles?

$$v_o/v_{gen} = v_o/v_{gen}|_{MS} \frac{1 + b_1A + b_2A^2 + \dots}{1 + a_1A + a_2A^2 + \dots}$$

1) If a_3 and a_4 etc are small

-and-

2) If $a_2/a_1 \ll a_1$


-then-

$$v_o/v_{gen} \approx \frac{v_o}{v_{gen}|_{MS}} \frac{1 + b_1A + b_2A^2 + \dots}{(1 + a_1A)(1 + a_2/a_1 \cdot A)}$$

(Separated pole approximation)

Whether or not we use the SPA,


- How do we find a_2 ? -

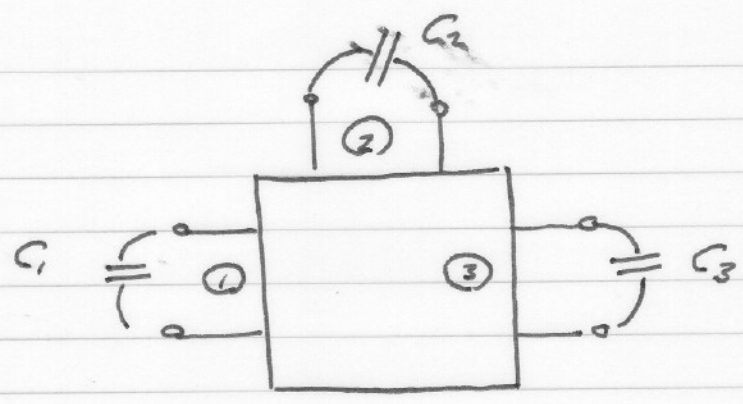

$$a_2 = R_{11}^0 C_1 C_2 R_{22}' + R_{11}^0 C_1 C_3 R_{33}' + R_{22}^0 C_2 C_3 R_{33}^2$$


(can be applied this way to more than 3 $\frac{1}{s}$)

Where we define R_{22}' as below:

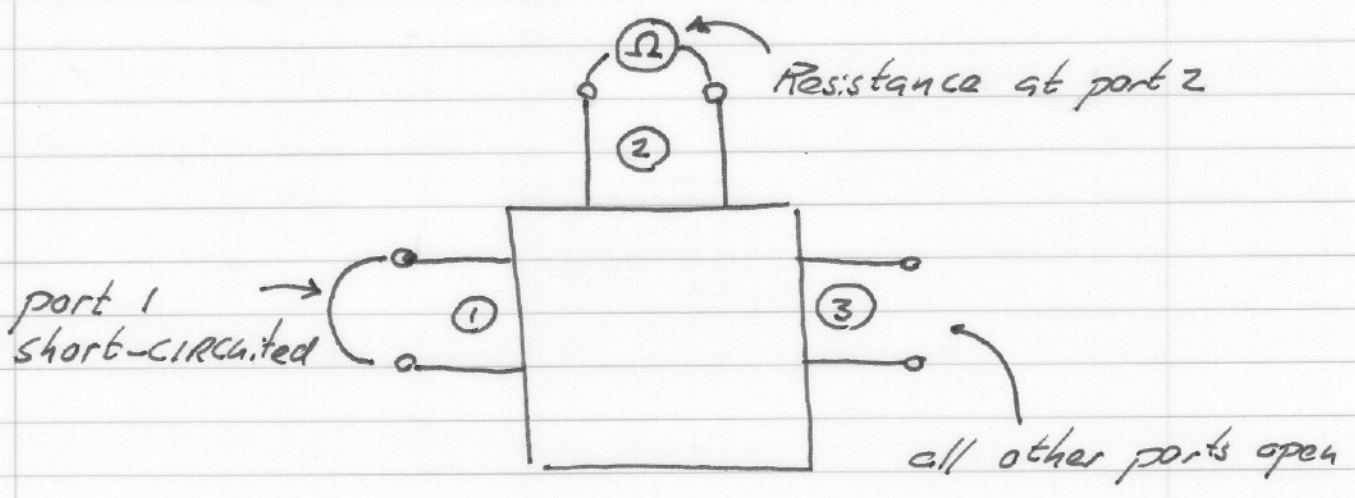

$R_{22}' =$ "resistance at port 2
 with port 1 short-circuited
 but all other ports open-circuited"

Now Consider a 2-port For a Moment:

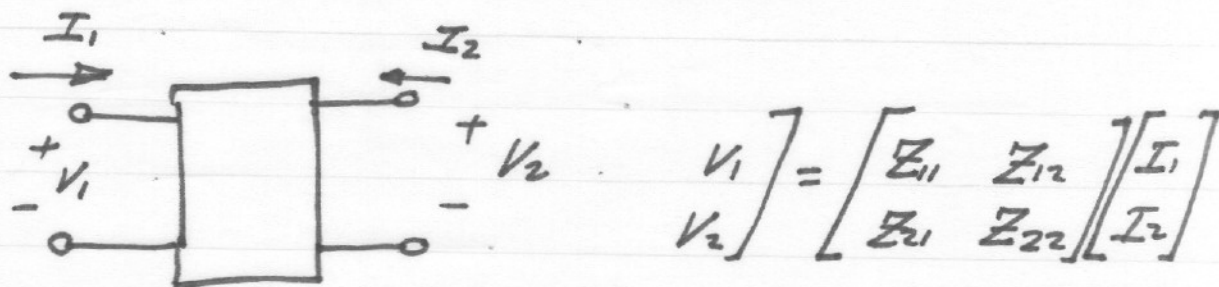

$$R_{11}^0 = Z_{11} = \left. \frac{V_1}{I_1} \right|_{I_2=0} \quad \& \quad R_{11}^2 = \left. \frac{V_1}{I_1} \right|_{V_2=0}$$

$$\text{If } V_2 = 0 \Rightarrow Z_{21} I_1 + Z_{22} I_2 = 0 \Rightarrow \frac{V_1}{I_1} = \boxed{Z_{11} + \frac{Z_{12}(-Z_{21})}{Z_{22}} = R_{11}^2}$$

$$\text{Similarly: } R_{22}^1 = Z_{22} - \frac{Z_{12} Z_{21}}{Z_{11}}$$

$$\text{So: } R_{11}^0 R_{22}^1 = Z_{11} \left[Z_{22} - \frac{Z_{12} Z_{21}}{Z_{11}} \right] = Z_{11} Z_{22} - Z_{12} Z_{21} = \Delta Z$$

$$\text{and } R_{11}^2 R_{22}^0 = \left[Z_{11} - \frac{Z_{12} Z_{21}}{Z_{22}} \right] Z_{22} = \dots = \Delta Z$$

$$\underline{\text{So:}} \quad \boxed{R_{11}^0 R_{22}^1 = R_{22}^0 R_{11}^2 = \Delta Z}$$


So:

$$a_2 = R_{11}^0 C_1 C_2 R_{22}^1 + R_{11}^0 C_1 C_3 R_{33}^1 + R_{22}^0 C_2 C_3 R_{33}^2$$

$$= R_{11}^2 C_1 C_2 R_{22}^0 + R_{11}^3 C_1 C_3 R_{33}^0 + R_{22}^3 C_2 C_3 R_{33}^0$$

- Each term can be calculated two ways.

Returning to our example:

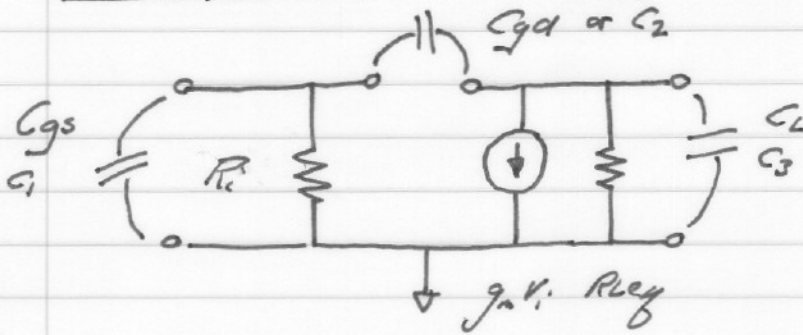

$$\left. \begin{array}{l} \underline{C_1 R_{11}^0 R_{22}^1 C_2} \quad R_{11}^0 = R_i \\ R_{22}^1 = R_{leg} \end{array} \right\} \text{DRAW sketches for each case}$$

$$\underline{C_1 R_{11}^0 R_{33}^1 C_3} \quad R_{11}^0 = R_i$$

$$R_{33}^1 = R_{leg}$$

$$\underline{C_2 R_{22}^0 R_{33}^2 C_3} = C_2 R_{22}^3 R_{33}^0 C_3$$

$$R_{33}^0 = R_{leg} \quad R_{22}^3 = R_i$$

So: $R_{11} \circ R_{22}' = R_{11} \circ R_{33}' = R_{22} \circ R_{33}'^2$ for this case only
 $= R_i R_{eq}$

hence: $a_1 = R_i R_{eq} [C_{gs} C_{gd} + C_{gs} C_L + C_{gd} C_L]$

For our example

$$v_o/v_{gen} = v_o/v_{gen}/ms \frac{1 + b_1 A}{1 + a_1 A + a_2 A^2}$$

$$a_1 = R_i C_{gs} + R_{eq} C_L + [R_i (1 + g_m R_{eq}) + R_{eq}] C_{gd}$$

$$a_2 = R_i R_{eq} [C_{gs} C_{gd} + C_{gs} C_L + C_{gd} C_L]$$

... as was found earlier by nodal analysis.