

ECE ECE145A (undergrad) and ECE218A (graduate)

Mid-Term Exam. February 11, 2009

Do not open exam until instructed to.

Open notes, open books, etc

You have 1 hr and 15 minutes.

Use any and all reasonable approximations (5% accuracy is fine.), **AFTER STATING THEM.**


Problem	Points Received	Points Possible
1		20
2		25
3a		10
3b		10
3c		10
4a		5
4b		20
total		100

Name: Answer key


Problem 1, 20 points

The Smith Chart and Frequency-Dependent Impedances.


(a)

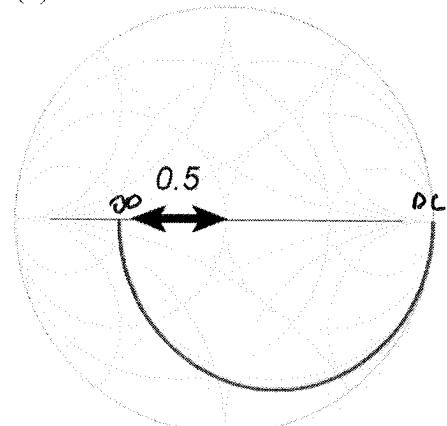


(b)

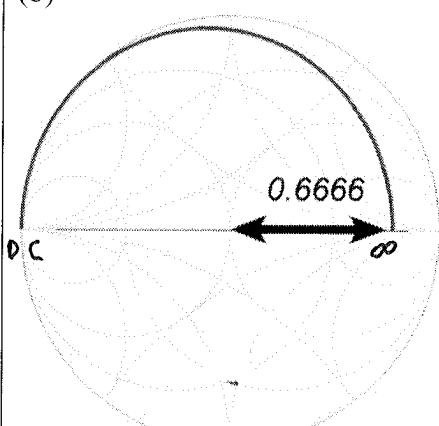


(c)

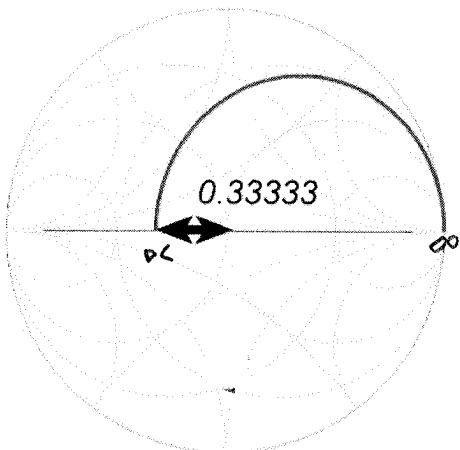




(d)

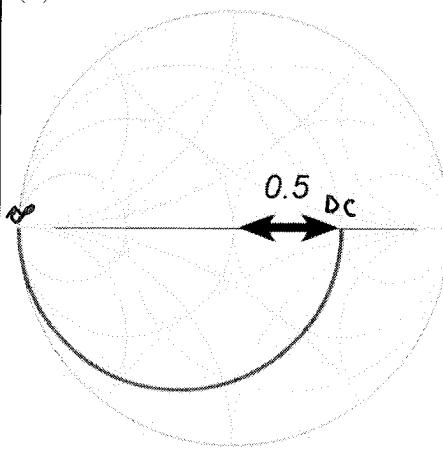

(e)

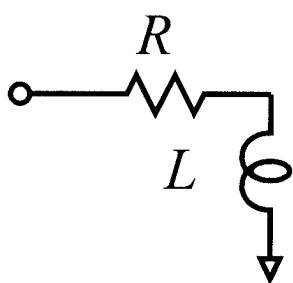

(f)

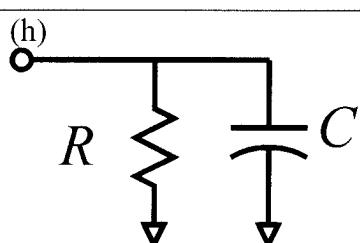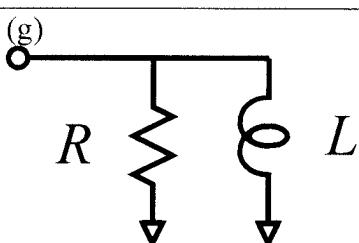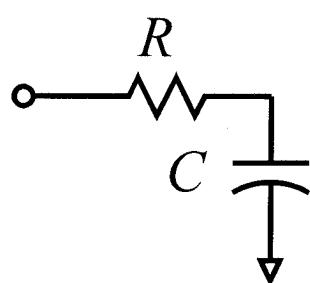

Match each Smith Chart with each circuit, and give all resistor values:

Circuit (e): Smith chart = C R = 25Ω

Circuit (f): Smith chart = A R = 16.67Ω

Circuit (g): Smith chart = B R = 250Ω

Circuit (h): Smith chart = D R = 150Ω

$$Z = Z_0 \cdot \frac{1 + \Gamma}{1 - \Gamma}$$

E/C

$$\Gamma = \frac{1}{3} \angle 180^\circ = -\frac{1}{3}$$

$$R = 50 \cdot \frac{1 - \frac{1}{3}}{1 + \frac{1}{3}} = 25$$

F/A

$$\Gamma = -0.5$$

$$R = 50 \cdot \frac{1 - 0.5}{1 + 0.5} = 16.67$$

$$Z = R + j\omega L$$

$$Z = R - j/\omega C$$

G/D

$$\Gamma = +\frac{2}{3}$$

$$R = 50 \cdot \frac{1 + \frac{2}{3}}{1 - \frac{2}{3}} = 250$$

$$Y = \frac{1}{R} - j \frac{1}{\omega L}$$

H/D

$$\Gamma = +0.5$$

$$R = 50 \cdot \frac{1 + 0.5}{1 - 0.5} = 150$$


$$Y = \frac{1}{R} + j \omega C$$

Problem 2, 25 points

Transistor models and S-parameters.
To the left is a simplified model of a
MOSFET.

With element values as defined, first give algebraic expressions of the four S-parameters as a function of frequency.

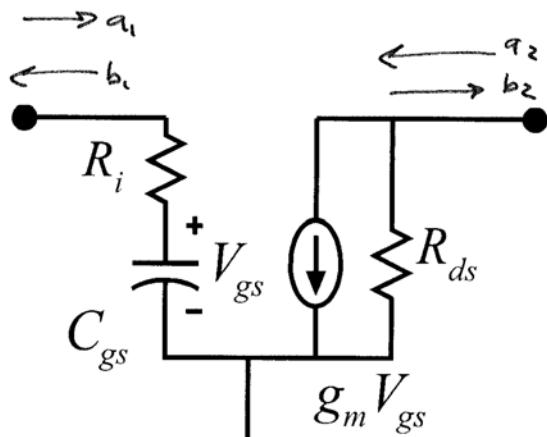Then using $C_{gs}=31.8 \text{ fF}$, $R_i=200 \text{ Ohms}$,
 $gm= 20 \text{ mS}$, $R_{ds}=250 \text{ Ohms}$, give
numerical values at $f=50 \text{ GHz}$.




$$\boxed{S_{11} = 0.655 - j \cdot 0.130}$$

$$\underline{S}_{22} = \Gamma_{out} = \frac{R_{DS} - Z_0}{R_{DS} + Z_0} = \frac{200}{300} = \boxed{\frac{2}{3}}$$

$\underline{S}_{12} = \boxed{0}$ By inspection we see that no signal at Port 2 will couple to Port 1 since $C_{20} = 0$


$$\underline{S}_{21} = \frac{2 V_{out}}{V_{gen}}$$

Find Your:

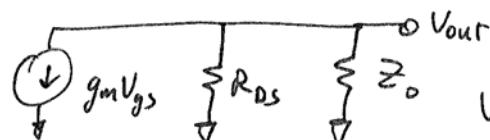

$$V_{out} = -g_m V_{gs} (R_{out}/Z_0)$$

Find V_{gs} in
terms of V_{gen}

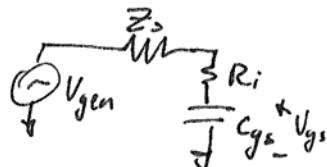

$$V_{gs} = \frac{V_{2e1}}{sC_{gs} + R_i + Z_0} V_{gm} = \frac{V_{2e1}}{1 + sC_{gs}(R_i + Z_0)}$$

$$\text{Thus: } V_{out} = -g_m \cdot \frac{V_{gen}}{1 + sC_{gs}(R_i + Z_0)} \cdot (R_{DS} // Z_0)$$


$$S_{21} = \frac{2V_{out}}{V_{gen}} = \frac{-2g_m(R_o/(Z_0))}{1 + sG_s(R_i + Z_0)} = \frac{-2 \times 0.02 \left(\frac{1}{250} + \frac{1}{50}\right)^{-1}}{1 + j 2\pi \cdot 50 \times 10^9 (250) \times 31.8 \times 10^{-15}}$$

$$S_{21} = -0.230 + j \times 0.575$$

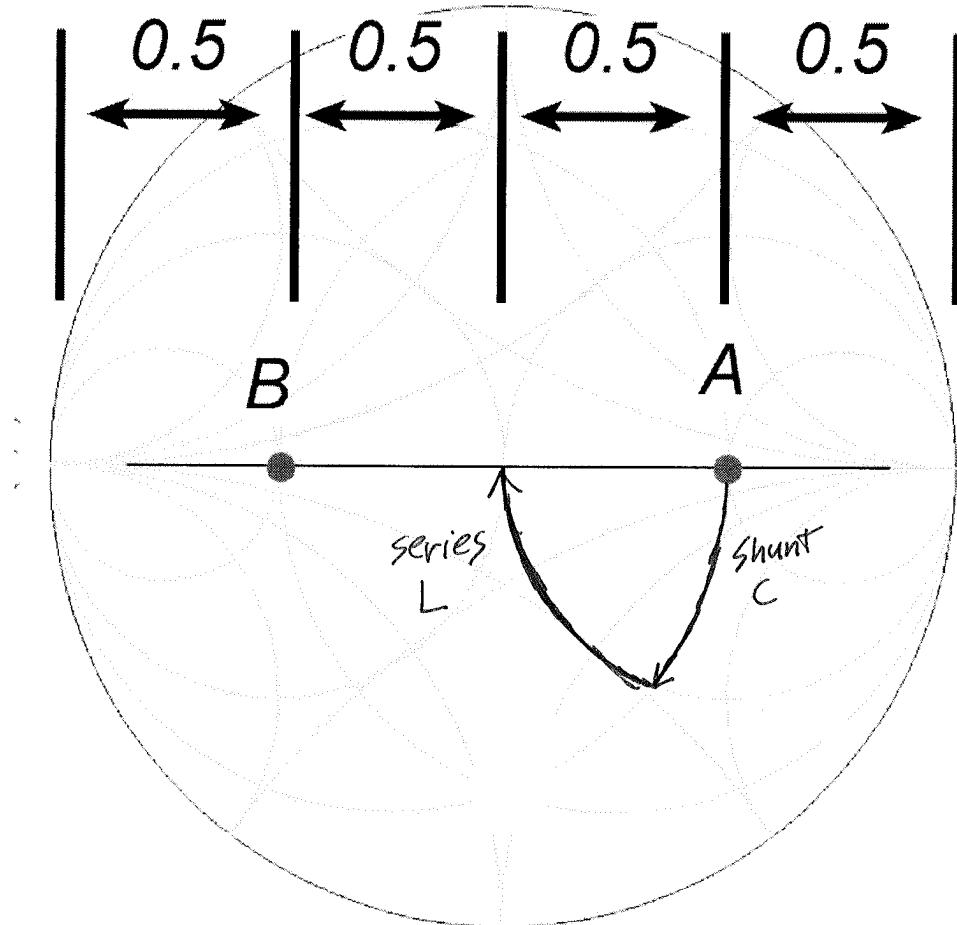Problem 3, 30 points

Elementary impedance matching network design.


Use the impedance-admittance chart below. Assume a 50 Ohm impedance normalization. To keep the problem simple, if certain Admittance and Impedance coordinate lines almost cross, use the approximation that they exactly cross.



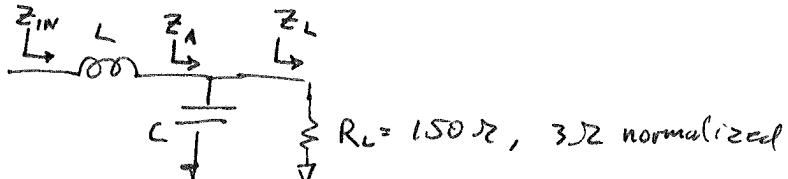Part (a), 10 points.

Design a series-L, shunt-C impedance matching network to match impedance "A" to 50 Ohms at 20 GHz. Give the circuit diagram and the element values.

$$Z_L = 50 \cdot \frac{1+0.5}{1-0.5} = 150\Omega$$



- Use shunt C to bring load to unit resistance circle, i.e. make $Re(Z_A) = 1$ (normalized)

$$Z_A = (Y_A)^{-1} = \left(\frac{1}{R_L} + j\omega C \right)^{-1} = \frac{R_L}{1 + j\omega C R_L} = \frac{R_L (1 - j\omega C R_L)}{1 + (\omega C R_L)^2}$$

$$Re(Z_A) = \frac{R_L}{1 + (\omega C R_L)^2} = 1$$

$$\Rightarrow C(\text{norm.}) = \frac{\sqrt{V_L - 1}}{\omega V_L} = \frac{\sqrt{2}}{2\pi \times 20 \times 10^9 \times 3} = 3.75 \times 10^{-12}$$

$$C = \frac{1}{50} \times 3.75 \times 10^{-12} = \boxed{75 \text{ fF} = C}$$

- Use series L to cancel remaining complex component of Z_A

$$Z_{in} = 50\Omega = j\omega L + Z_A = 50 + j\left(\omega L - \underbrace{\frac{\omega C R_L^2}{1 + (\omega C R_L)^2}}_{\text{set to 0}}\right)$$

$$L = \frac{C R_L^2}{1 + (\omega C R_L)^2} = \frac{75 \text{ fF} \times (150\Omega)}{1 + (2\pi \times 20 \times 10^9 \times 75 \text{ fF} \times 150\Omega)^2}$$

$$\boxed{L = 563 \text{ pH}}$$


Part (b), 10 points

Ideal inductors are not available to you. Assuming high-impedance lines of 100 Ohm impedance and low-impedance lines of 20 Ohms impedance, give an approximate distributed-element design to this matching network. The lines' effective dielectric constant is 2.0

$$L = \frac{\lambda}{Z_0}$$

$$C = \frac{\epsilon}{Z_0}$$
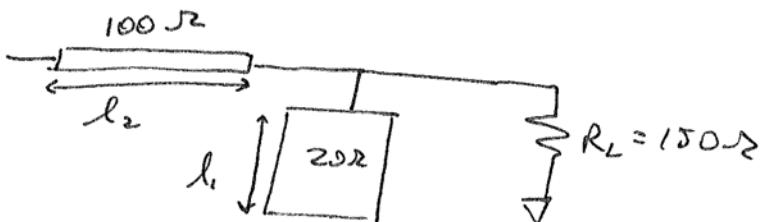
$$V_p = \sqrt{\frac{C}{\epsilon_r}} = 2.12 \times 10^8 \text{ m/s}$$



- High-Z lines are almost like inductors
- Low-Z lines are almost like capacitors

$$\lambda_1 = Z_0 C = 20 \Omega \times 75 \text{ fF} = 1.5 \mu\text{s}$$

$$l_1 = \lambda_1 V_p$$

$$\boxed{l_1 = 318 \mu\text{m}}$$


$$\lambda_2 = \frac{L}{Z_0} = \frac{56.3 \text{ pH}}{100 \Omega} = 5.63 \mu\text{s}$$

$$l_2 = \lambda_2 V_p$$

$$\boxed{l_2 = 1190 \mu\text{m}}$$

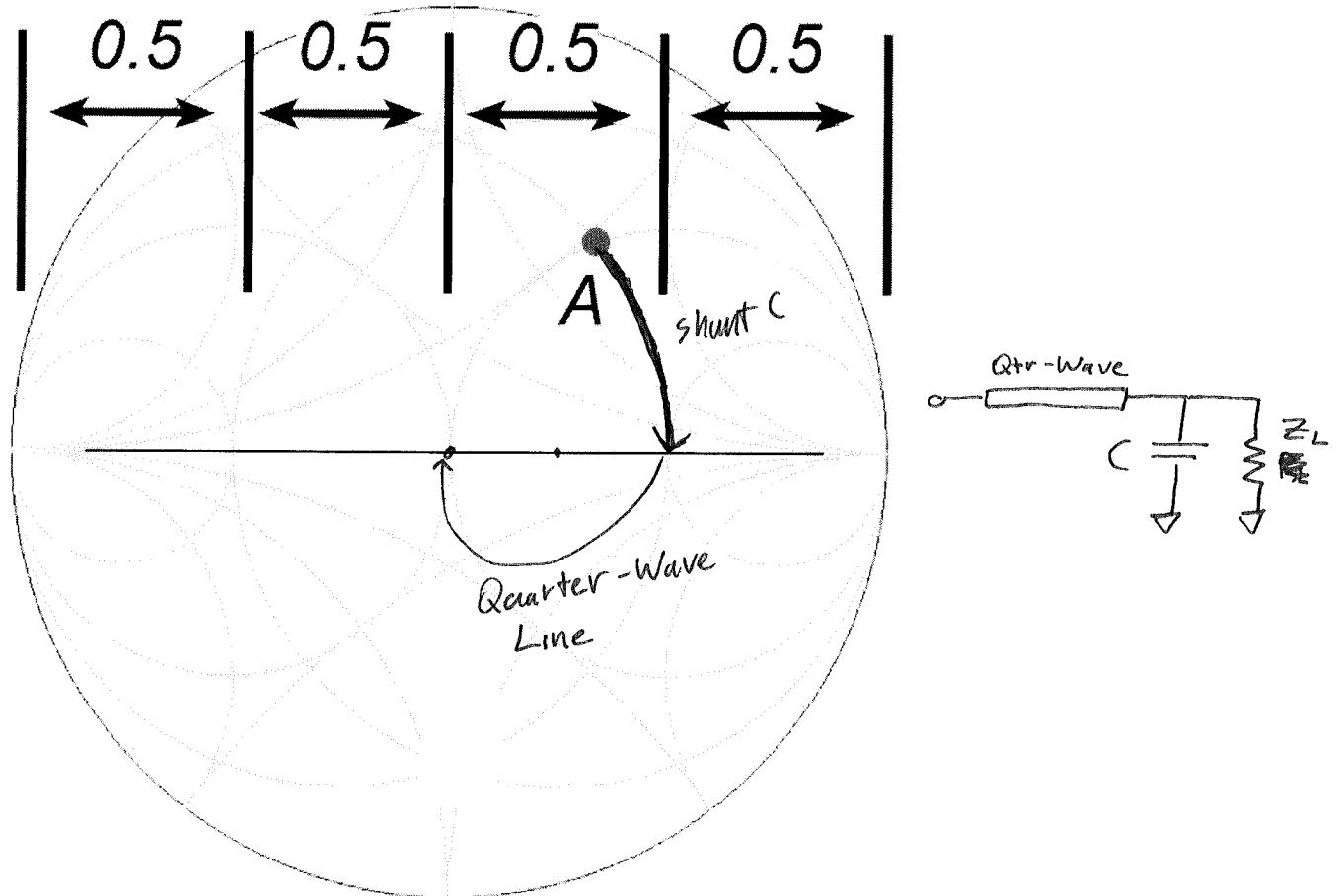Part (c), 10 points

Load impedance "A" is to be matched to $Z_0=50$ Ohms at 20 GHz (the chart below uses 50 OHms normalization) using a shunt capacitance and a series quarter-wave line. Find the value of the shunt capacitance and the required line impedance.



- From the symmetry with part (A) it is clear we will use the same capacitor

$$C = 75 \text{ fF}$$
- To match the resultant 150Ω impedance to 50Ω we use a quarter-wave line with impedance:
 same as load resistor in part A: $R = 50 \cdot \frac{1+0.5}{1-0.5} = 150\Omega$

$$Z_0 = \sqrt{Z_L \times Z_{in}} = \sqrt{150 \times 50} = 86.6\Omega$$


$$Z_0 = 86.6\Omega$$

Problem 4, 25 points

Lumped vs distributed elements

We are designing a bypass "capacitor" for use in a 60 GHz wireless transceiver IC.

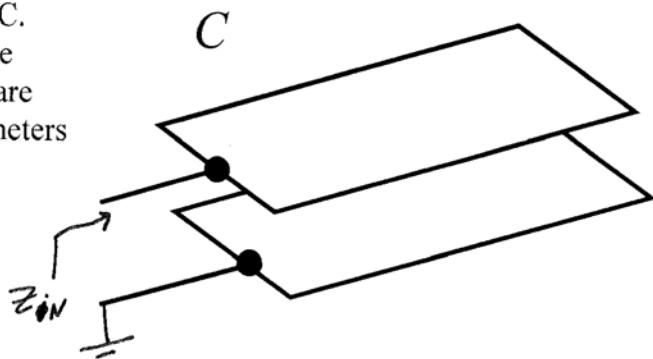The plate separation is 100 nm, and the dielectric constant is 4.0. The plates are 500 micrometers long and 100 micrometers wide.



Part (a), 5 points

What is the low-frequency capacitance C?

$$C = \frac{\epsilon A}{d} = \frac{4 \times 8.854 \times 10^{-12} \text{ F/m} \times 500 \mu\text{m} \times 100 \mu\text{m}}{100 \text{ nm}} = \boxed{17.7 \text{ pF}}$$

Part (b) 20 points

Using transmission-line relationships, what is the element's impedance at 37.5 GHz and at 75 GHz?

$$V_p = \sqrt{\epsilon_r} = 1.5 \times 10^8 \text{ m/s}$$

$$\underline{37.5 \text{ GHz}}: \lambda_{37.5 \text{ GHz}} = \frac{V_p}{f} = \frac{1.5 \times 10^8 \text{ m/s}}{37.5 \times 10^9 \text{ Hz}} = 4 \text{ mm}$$

$$\omega 37.5 \text{ GHz } L = \lambda/8 \text{ so } Z_{in} = -jZ_0 *$$



Since this is a low-Z line, $Z_0 = \epsilon/C$

$$\epsilon = l/V_p = 500 \mu\text{m} / 1.5 \times 10^8 \text{ m/s} = 3.33 \text{ pF}$$

$$\text{so } Z_0 = 0.188 \Omega, Z_{in} = -j \times 0.188$$

$$\left. \begin{array}{l} \text{or } Z_0 = \frac{n}{\sqrt{\epsilon_r}} \cdot \frac{h}{w} \\ Z_0 = 0.188 \Omega \end{array} \right\}$$

75 GHz: Now $L = \lambda/4$, so the open circuit ends appear to be short circuit

$$Z_{in} = 0$$

$$* Z_{in} = -jZ_0 \text{ because } P_{in} = P_L e^{-2j\beta l} = 1 \cdot e^{-2j \frac{2\pi}{\lambda} \frac{\lambda}{8}} = e^{-j\pi/2} = -j$$

$$Z_{in} = Z_0 \cdot \frac{1 + P_{in}}{1 - P_{in}} = Z_0 \cdot \frac{1 - j}{1 + j} = -j \frac{Z_0}{14}$$