

ECE 202A Notes set 5

Impedance Matching Lecture.





Most of what follows is best discussed (graphically) in the lecture. The following pages are intended to be used as view-graph foils in lectures. Write on your copy during the discussion.





one item will be written down here:




distributed realizations of lumped matching networks (next page.)

Impedance Matching Lecture.





(1a)

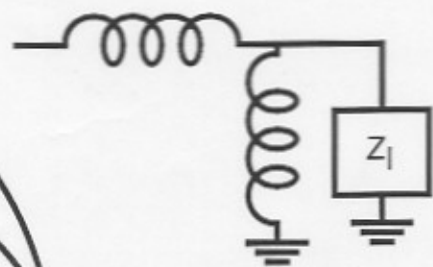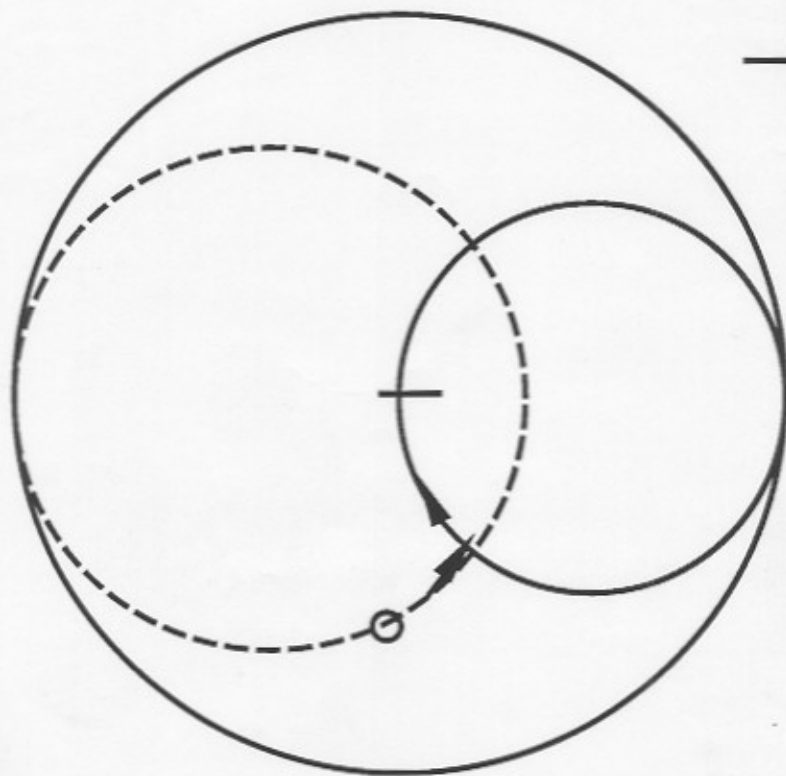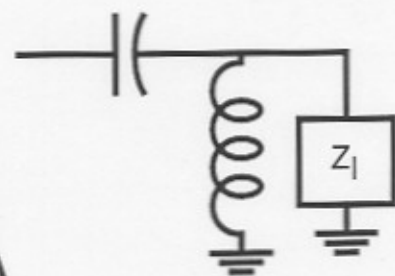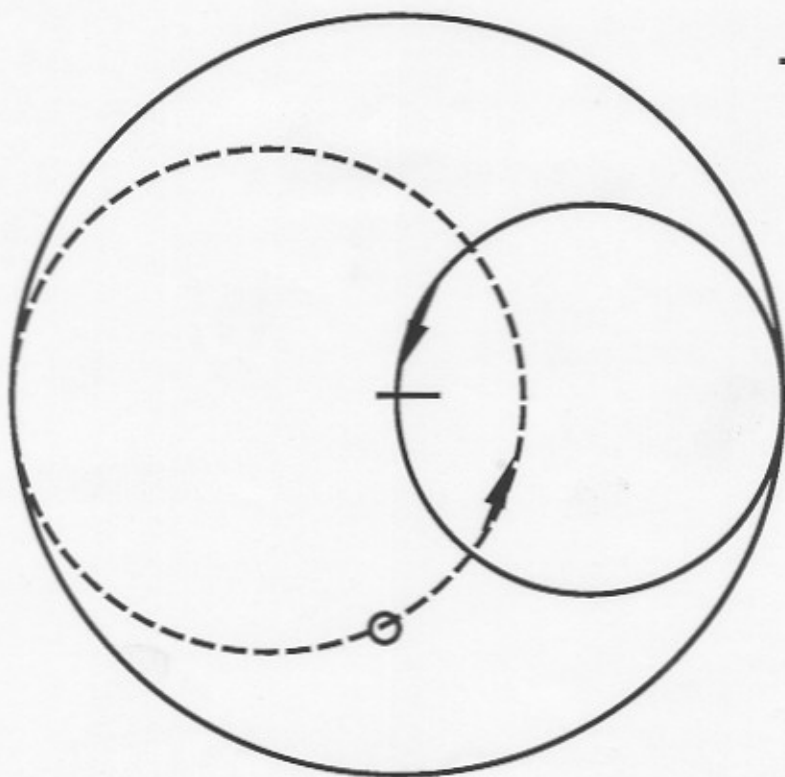

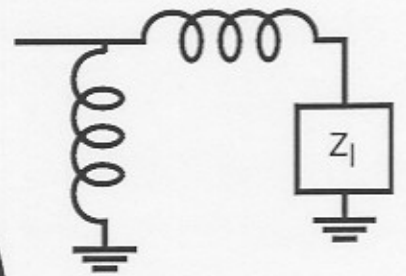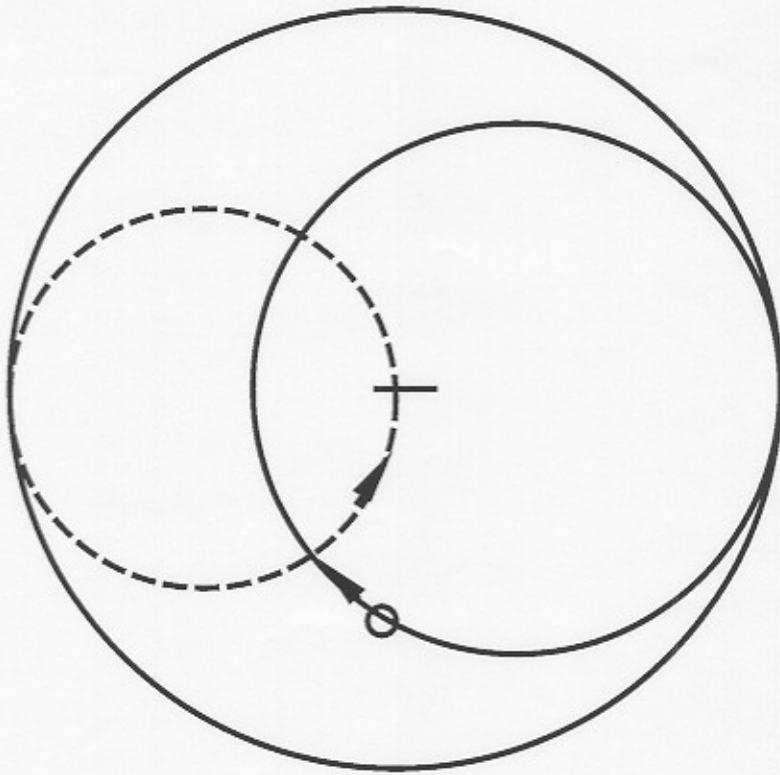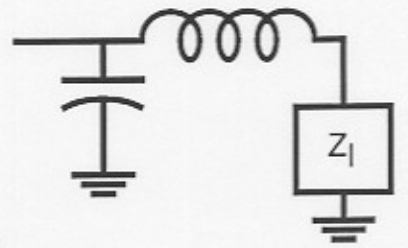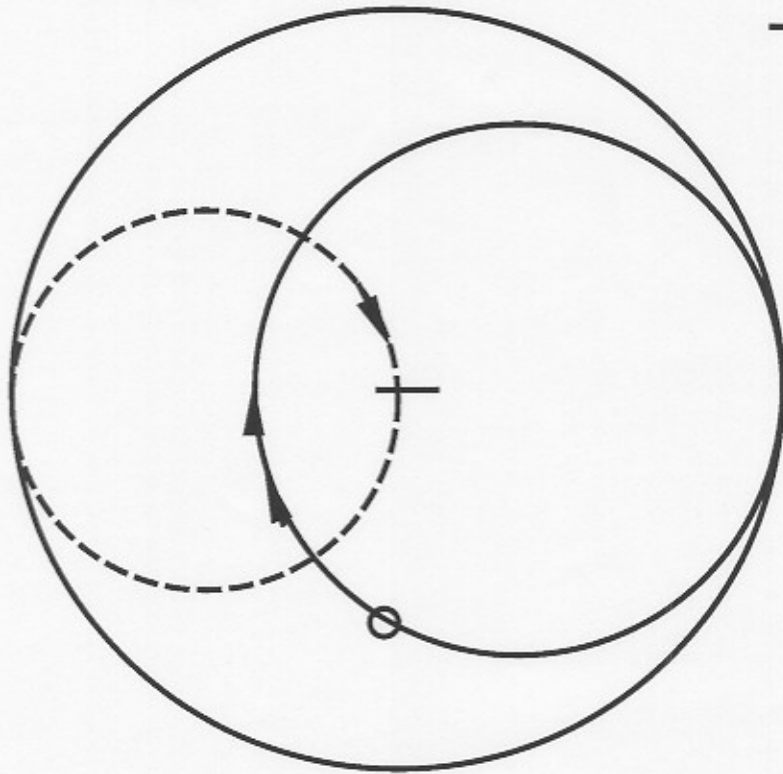


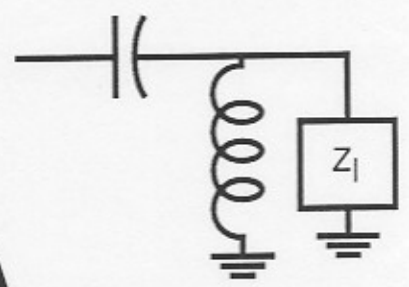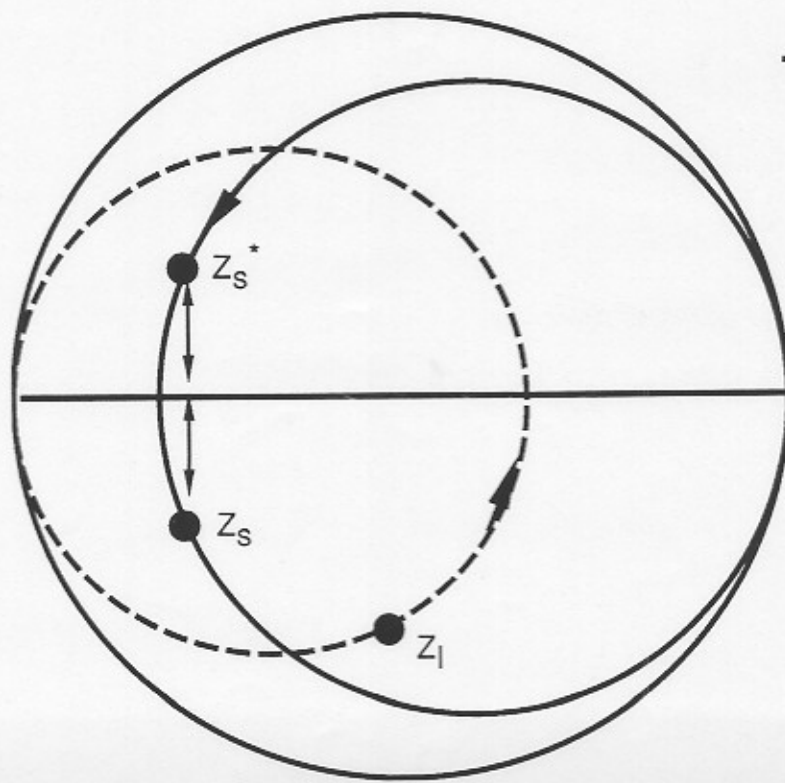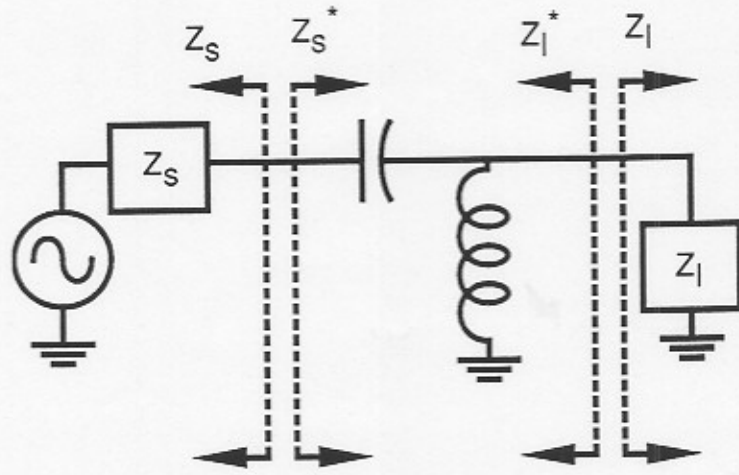

(1d)

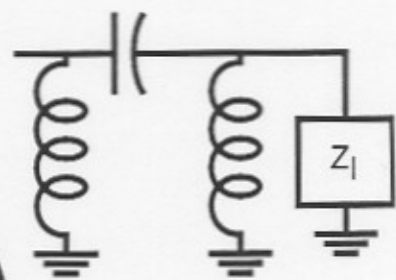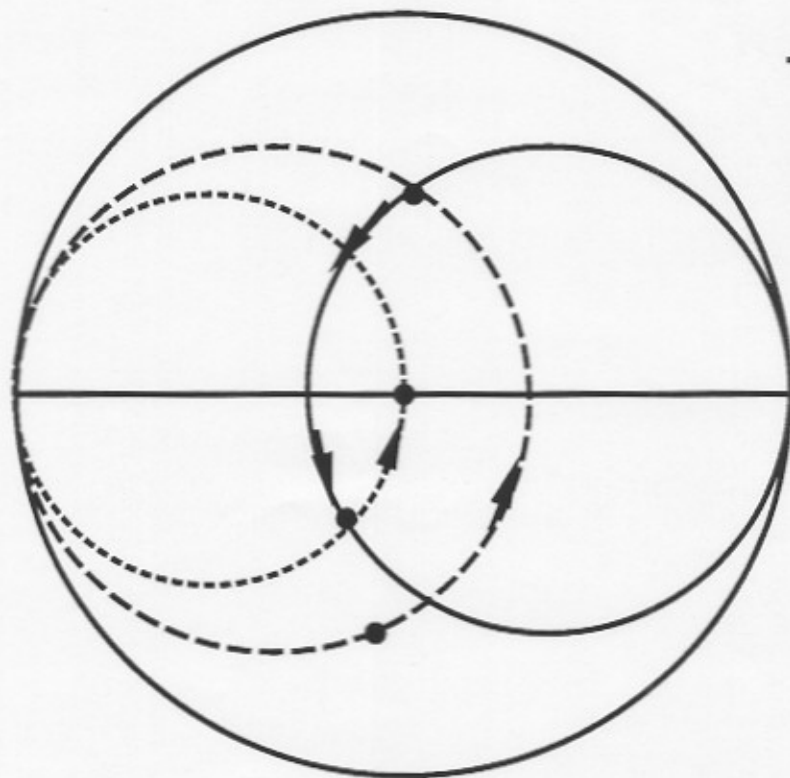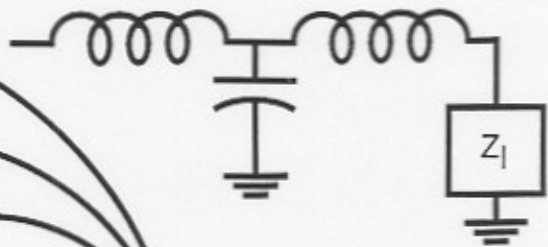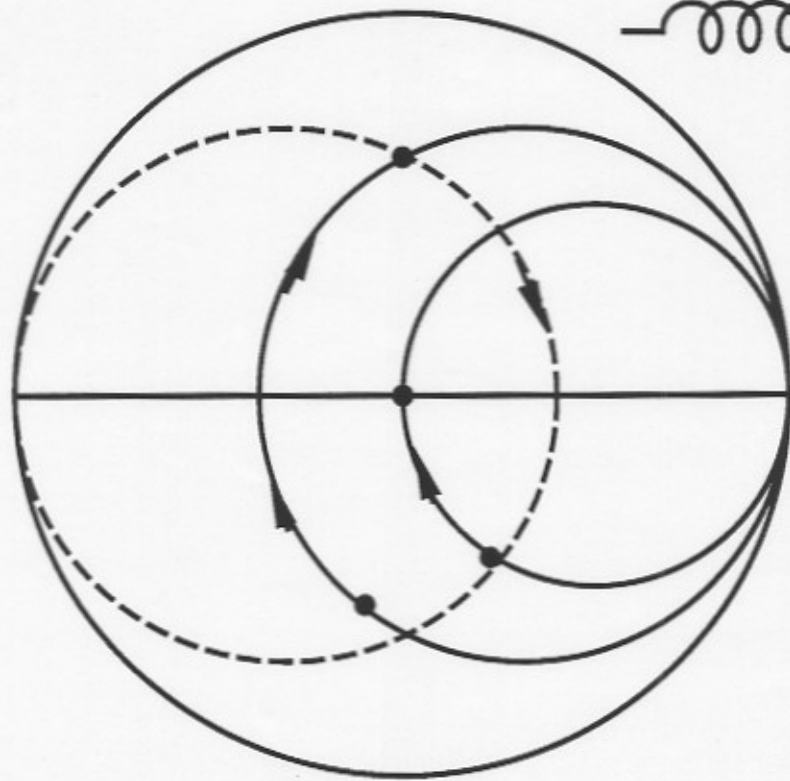

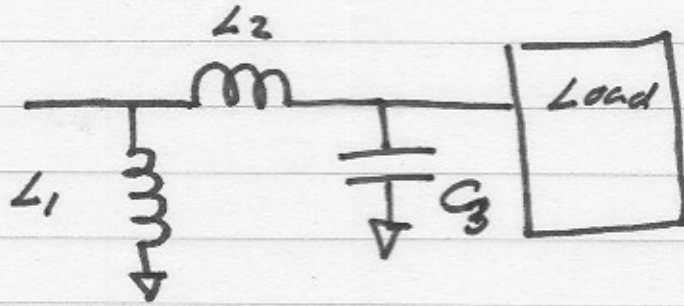Suppose we have designed a lumped impedance-matching network, thus:




this example has shunt and series inductors and a shunt capacitor. Think for a moment as to why no series capacitor has been chosen.

we may not have  $\infty$  &  $\frac{1}{\infty}$  available to us, only  $\text{---}\square\text{---}$  of impedances over the range  $Z_{min}$  to  $Z_{max}$ .

(3)

recall the models of short trans. lines:

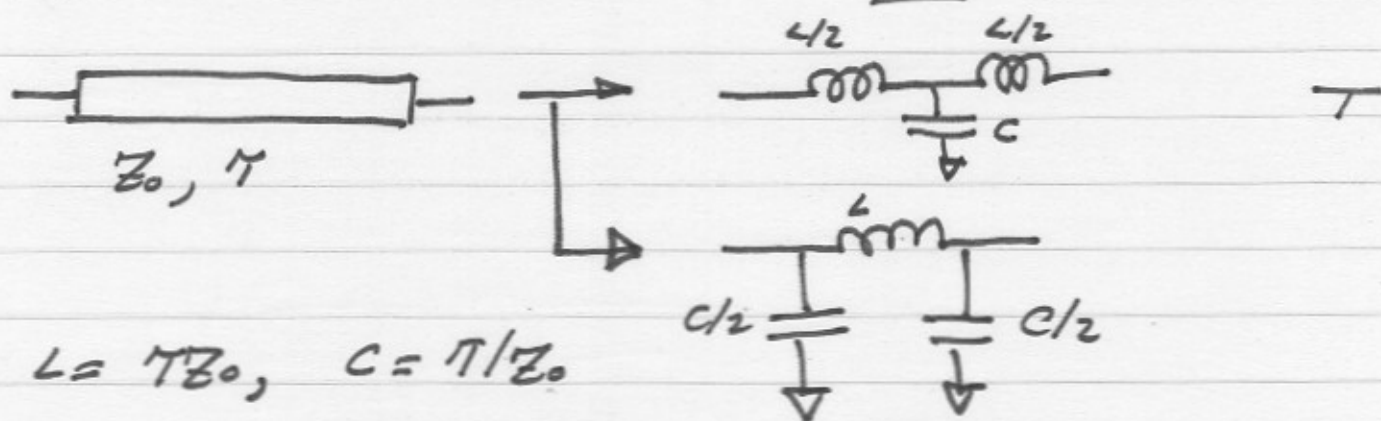

Comment on electrical length:

The Microwave literature will say a line is  $43^\circ$  long at  $5 \text{ GHz}$ . what does this mean?

freq

$$\text{Electrical length} = E = \frac{l}{\lambda_{\text{ref}}} \cdot 360^\circ$$

recall  $f \cdot \lambda = v$  so  $\text{freq } \lambda_{\text{ref}} = v$

$$\rightarrow E = \frac{l}{v / \text{freq}} \cdot 360^\circ = \frac{l}{v} \cdot \text{freq} \cdot 360^\circ$$

$$\boxed{E = \gamma \cdot \text{freq} \cdot 360^\circ}$$

I, like the people who wrote the program SPICE, find the "electrical length" description cumbersome.

a line which is 1 ns long has an electrical length  $E = 360^\circ$  at  $f_{ref} = 1 \text{ GHz}$

and

an electrical length  $E = 36^\circ$  at  $f_{ref} = 100 \text{ MHz}$ .


why not just say  $\tau = 1 \text{ ns}$ ?

... you should be conversant with

Both terminologies.



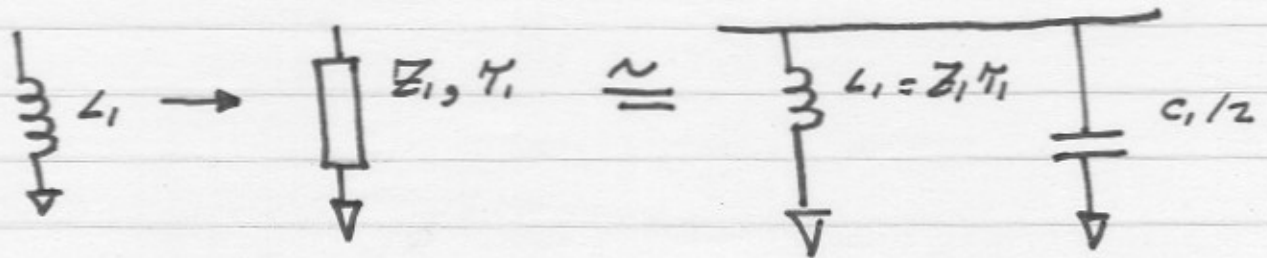... lets approximate our  $\text{---} \text{---} \text{---}$  &  $\text{---} \text{---}$  with  $\text{---}$




$$C_1 = Y_1 / Z_1 = L_1 / Z_1^2$$

So, we have obtained the inductor  $L_1$  we desire, together with a  $C_1/2$  which we do not.

$C_1$  does vary as  $1/Z_1^2$ , so using a high impedance line helps greatly in reducing  $C_1$ .

The issue will always be: is the undesired  $C_1$  sufficiently small?

approximate:

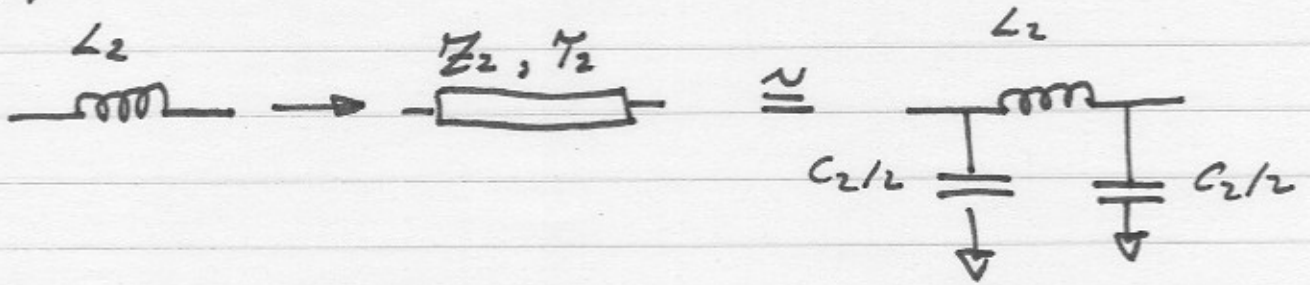


again  $L_2 = Z_2 T_2$

$$C_2 = T_2 / Z_2 = L_2 / Z_2^2$$

$\Rightarrow Z_2$  should be high.


and approximate:

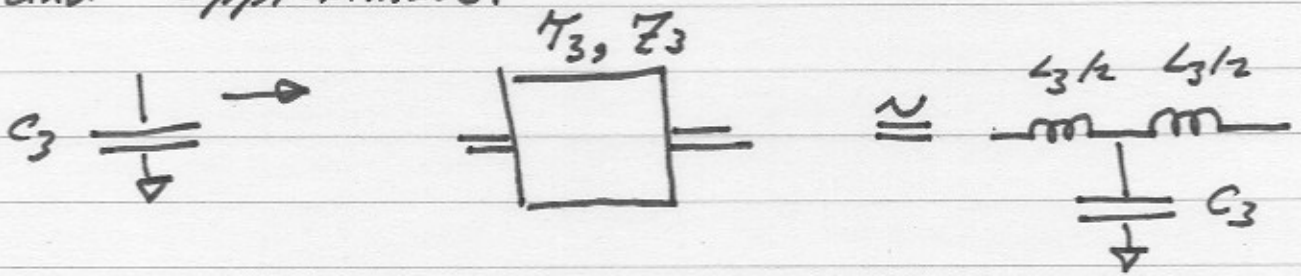


$$C_3 = T_3 / Z_3$$

$$L_3 = T_3 Z_3 = C_3 Z_3^2 \rightarrow Z_3 \text{ should be low.}$$


so we started with this

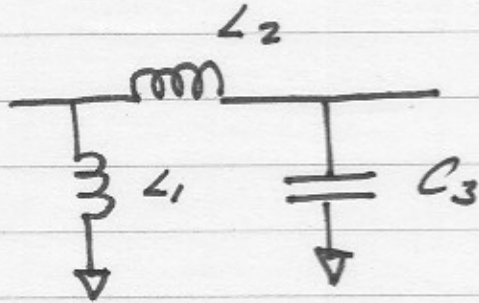

approximated it with this:


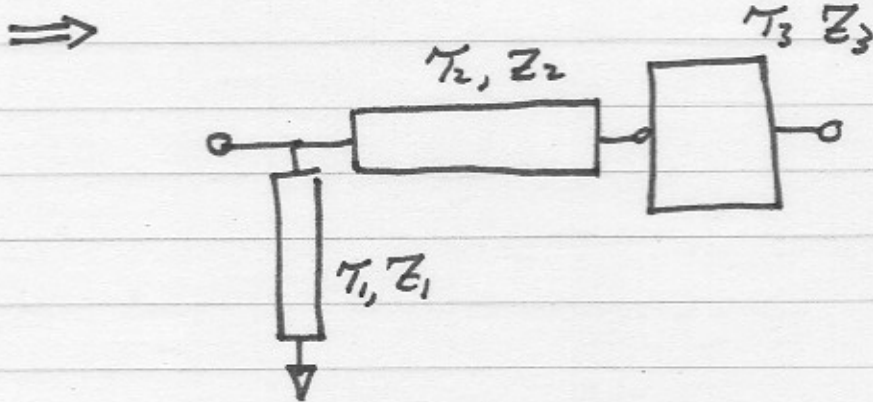


which is approximately this:

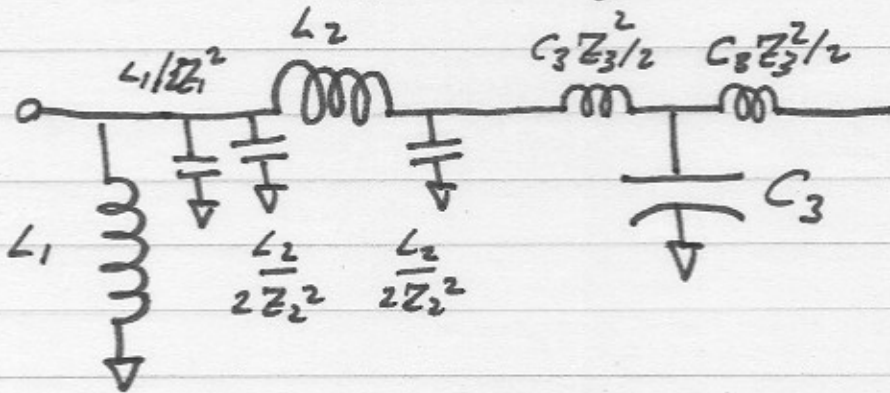


... if  $Z_1$  and  $Z_2$  are sufficiently high  
 and  $Z_3$  sufficiently low  
 this will approximate the desired network.

### Single matching section

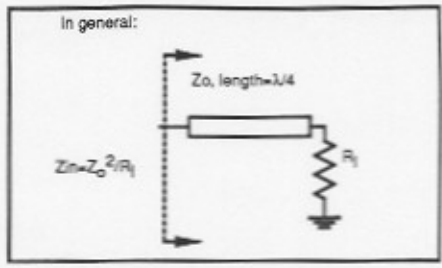
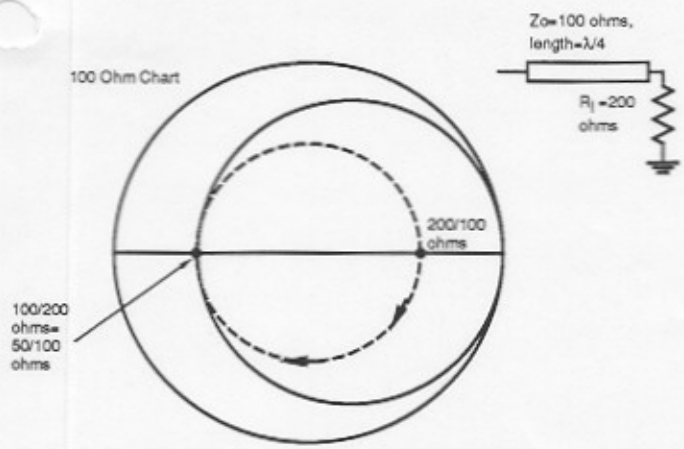


### Multi-Section

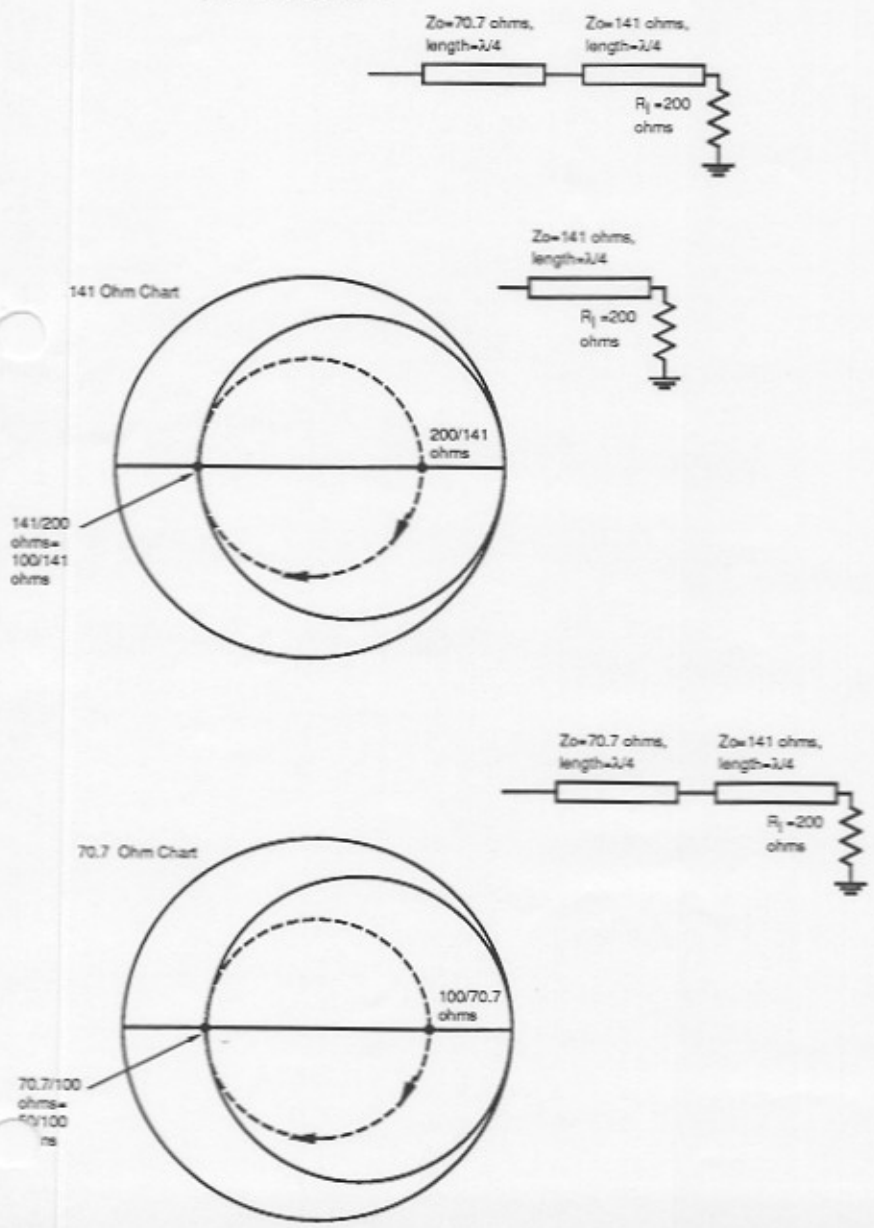

### Single-section

Chart normalized to  $Z_0$

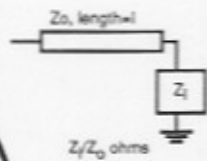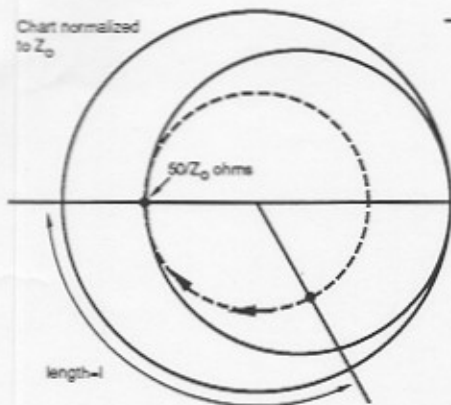

Advantage: Single element  
Disadvantage: No Clear Synthesis procedure, cut-and-try design method only

### Two-Section



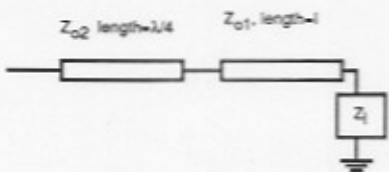
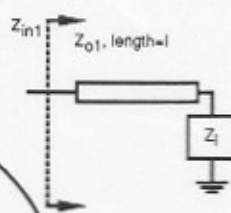
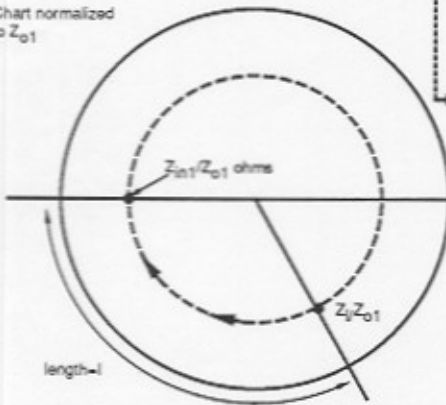


Chart normalized to  $Z_{01}$

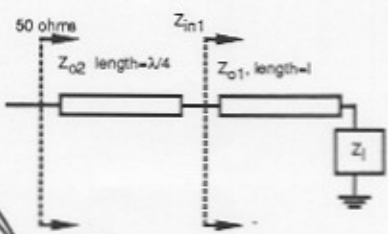


Suggestion for design:  
If Zload is capacitive, make first line high-impedance.  
If Zload is inductive, make first line low-impedance


Chart normalized to  $Z_{02}$

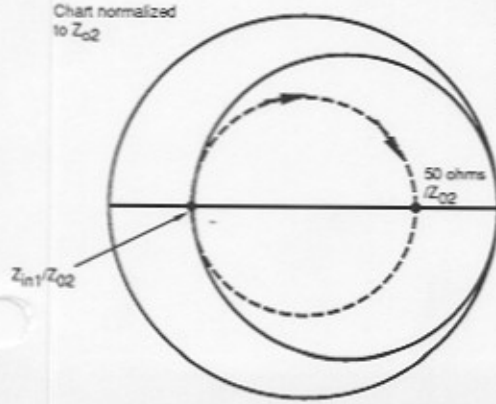


50 ohm chart

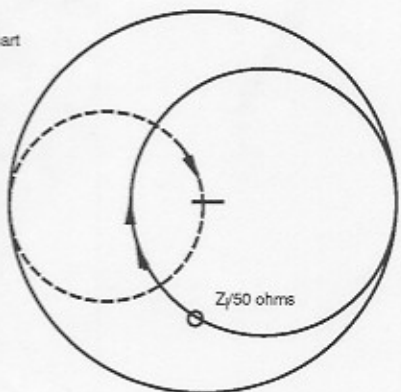



Lumped Prototype

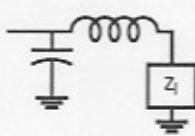




Realization

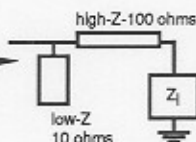



100 ohm chart

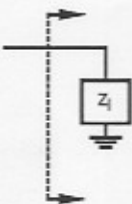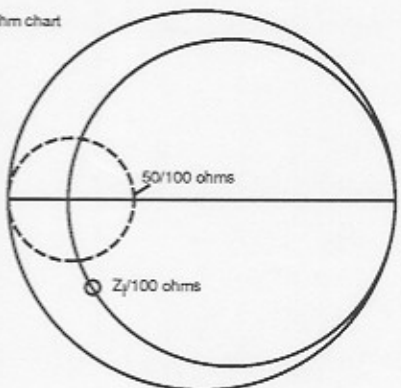



100 ohm chart

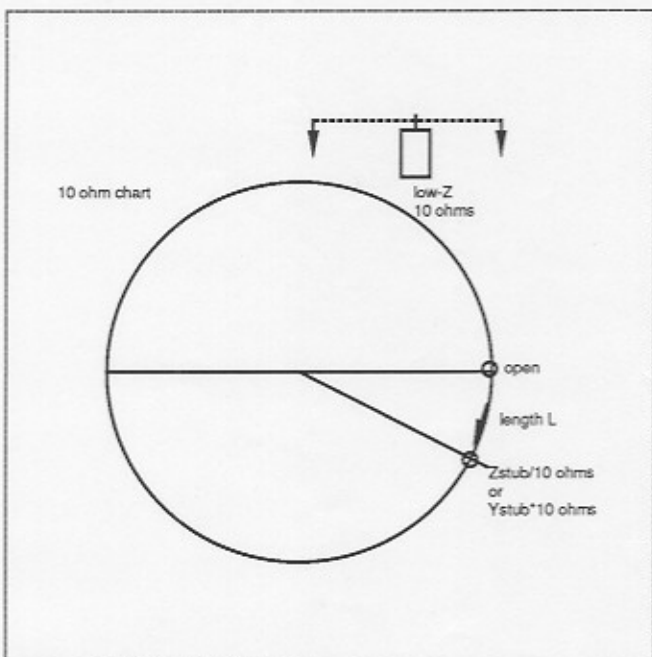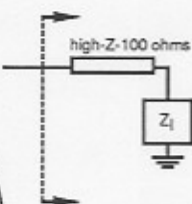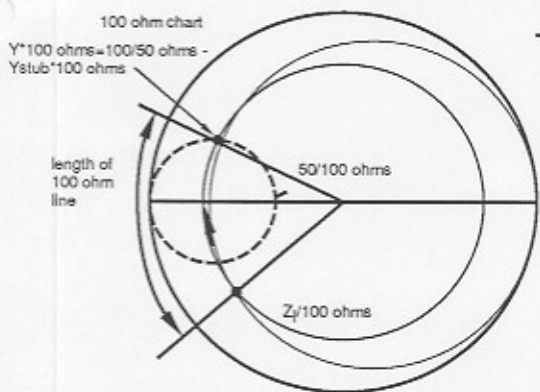


100 ohm chart

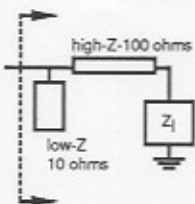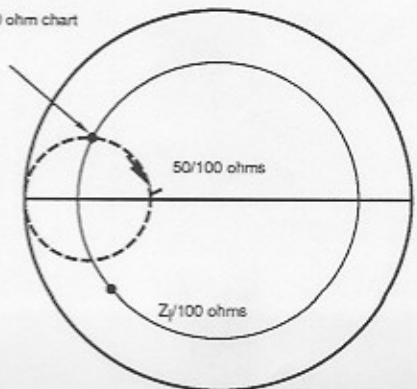



50 ohm chart

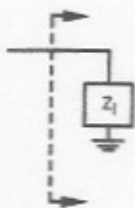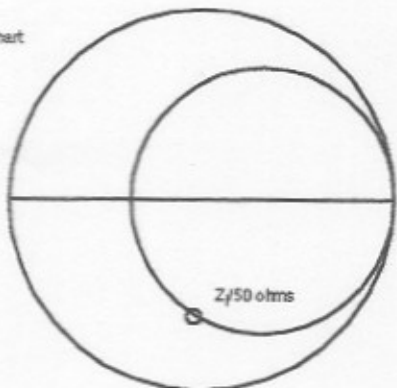

Realization

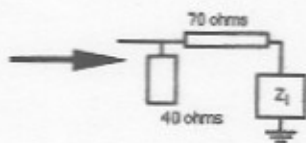



70 ohm chart

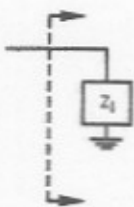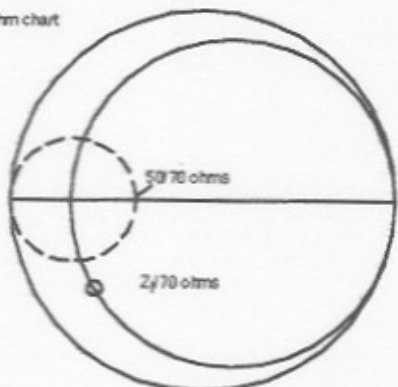


70 ohm chart

ohms = 70/50 ohms = 1.4



length of 70 ohm line

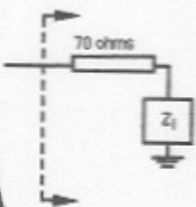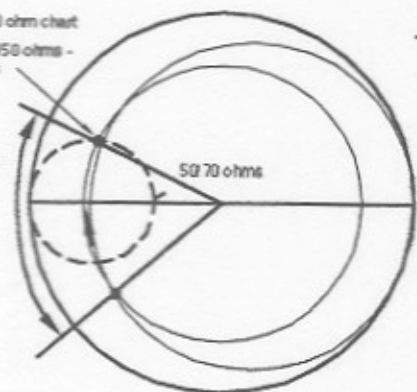



40 ohm chart

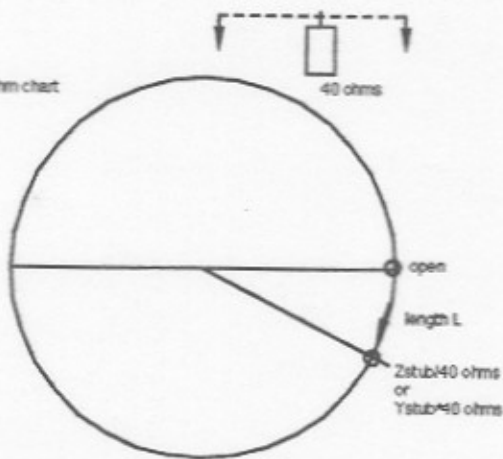


70 ohm chart

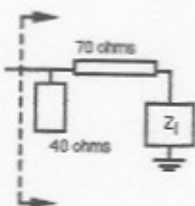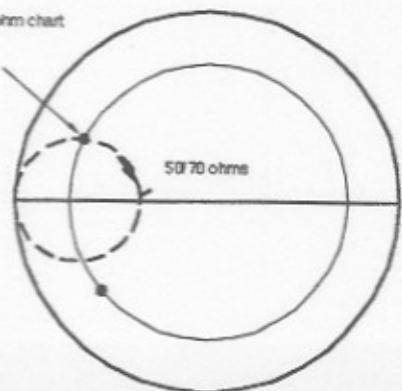



50 ohm chart

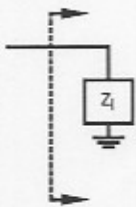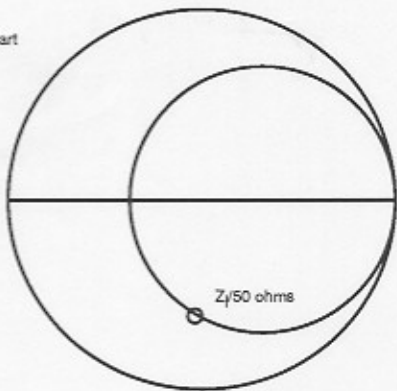

Realization

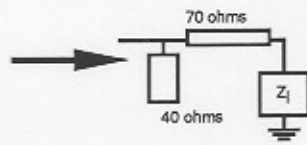



70 ohm chart

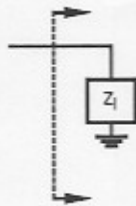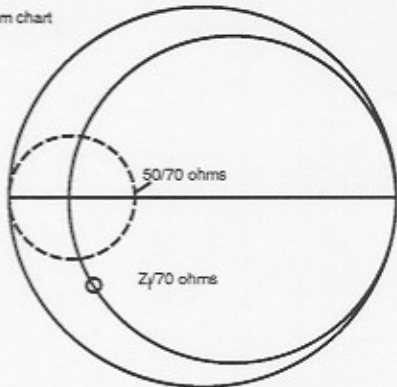



70 ohm chart

\*70 ohms = 70/50 ohms - Ystub\*70 ohms

length of 70 ohm line

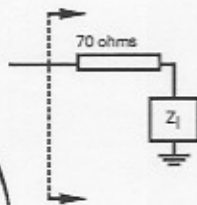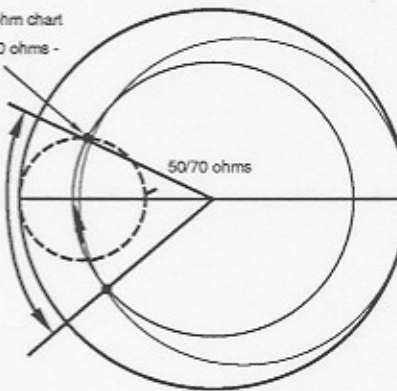

40 ohm chart

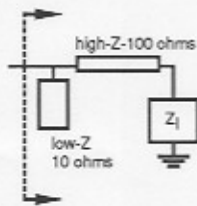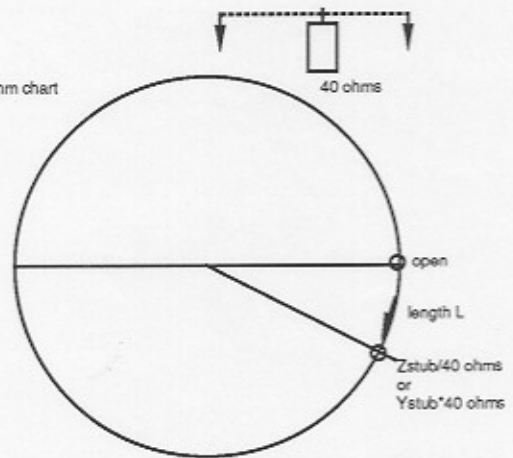

70 ohm chart

