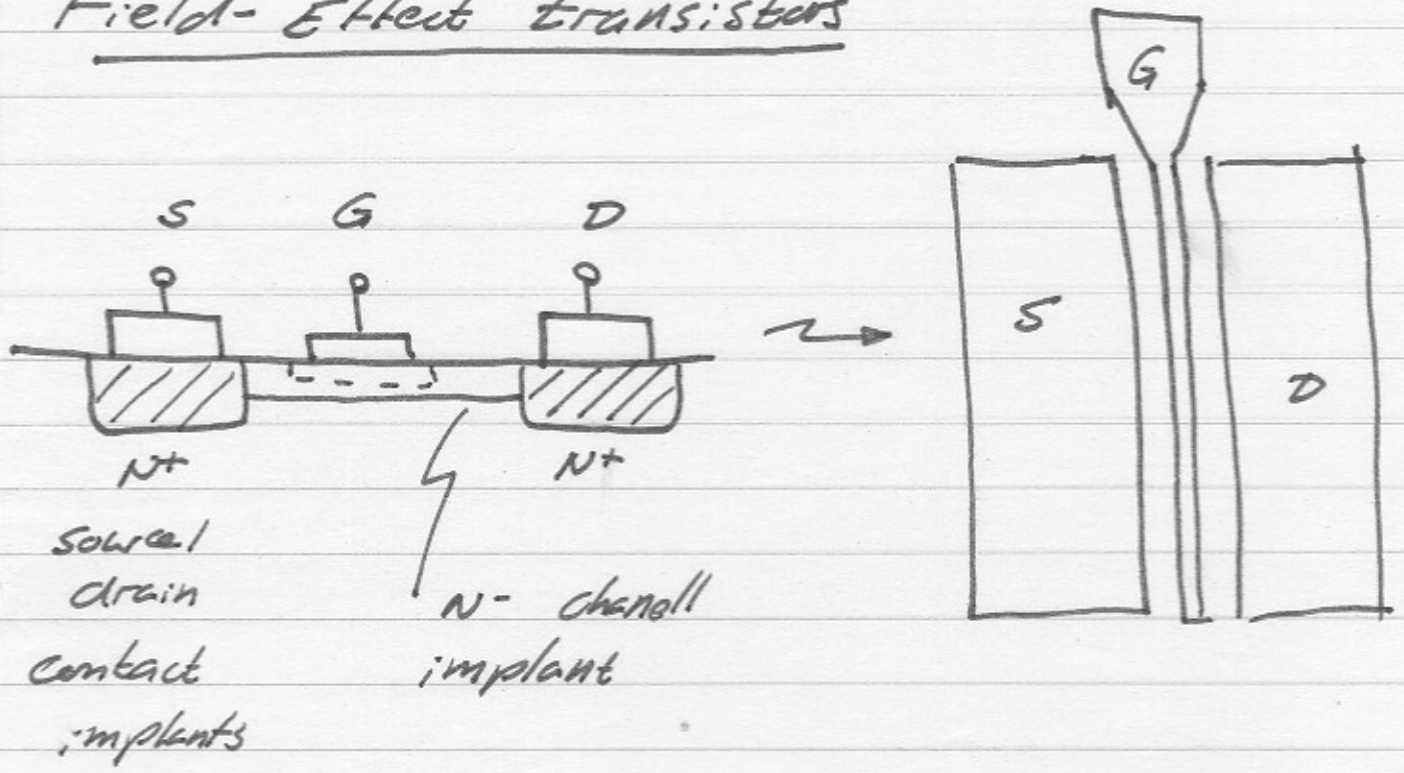


ECE 2029 Lecture Notes Set 6
Active Devices:


Field-Effect Transistors



Shown above is an ion-implanted MESFET although HEMTs differ somewhat in fabrication and in structure, terminal characteristics are similar...

bias voltage between gate & source sets depletion depth in channel region, restricting current flow between a source and drain.

I-V characteristics:

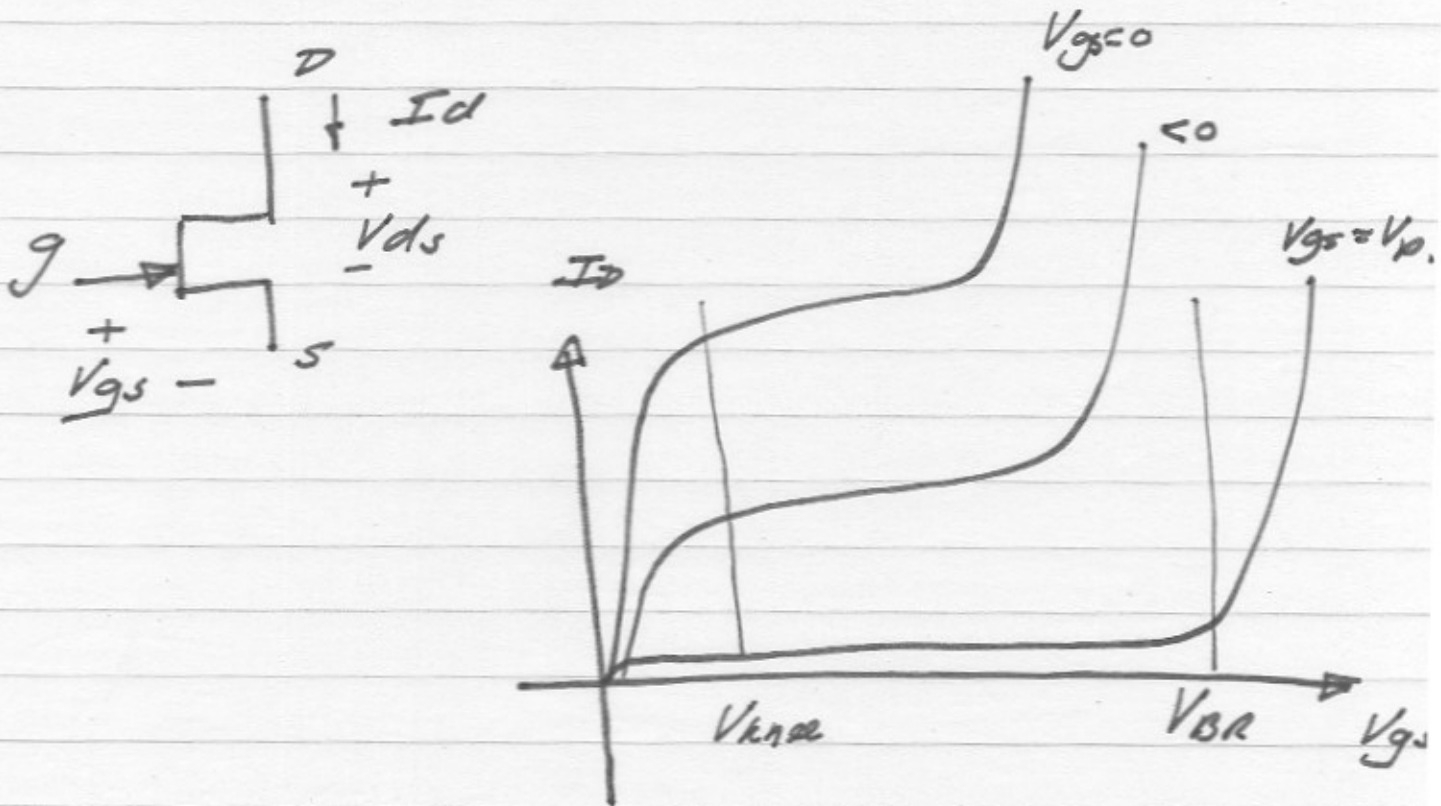

In elementary texts, for $V_{ds} > V_{knee}$,
it is given that

$$I_d \sim I_{dss} (1 - V_{gs}/V_p)^2 (1 + \lambda V_{ds})$$



... this assumes the gradual-channel approximation
and ignores velocity saturation. Neither assumption
is reliable for high-performance devices.

Models tend therefore to be either empirical or
based upon finite-element computer analysis.

gate will conduct if $V_{gs} > 0.5V$

normal operation: $\begin{cases} V_p < V_{gs} < +0.5V \\ 1.5V < V_{ds} < V_{br} \end{cases}$
 $\underbrace{\hspace{1.5cm}}_{V_{knee}}$

FET Model

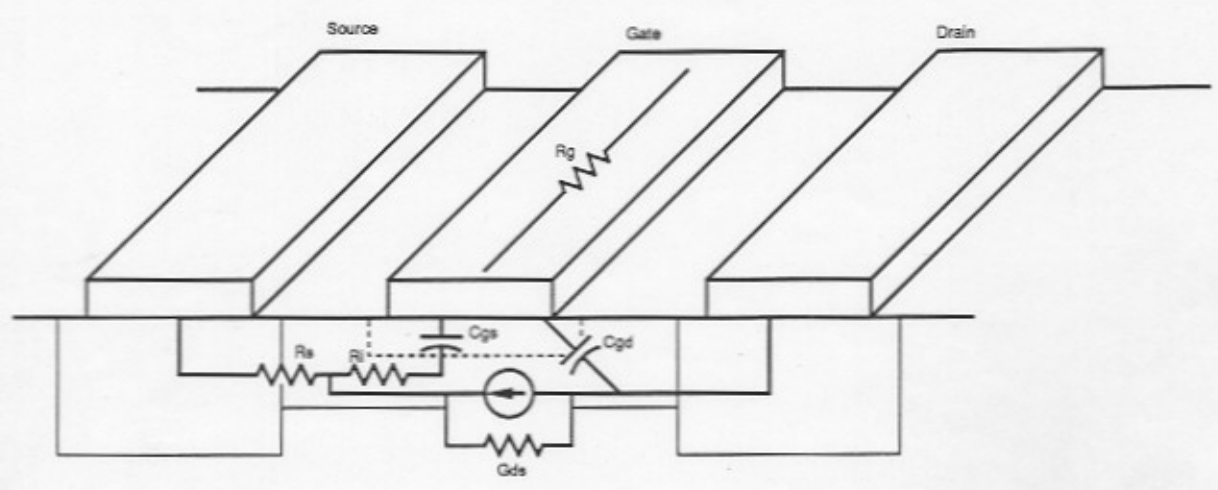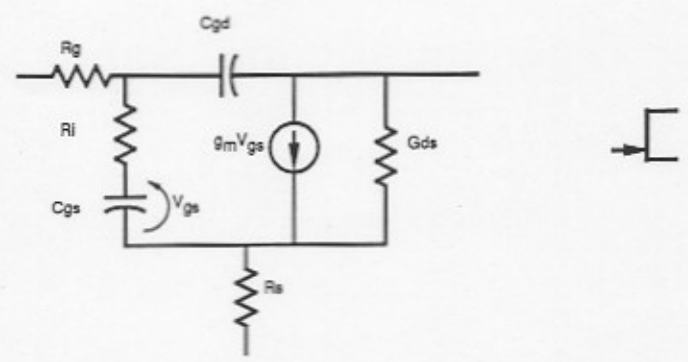

Here R_i is component of the channel resistance seen by C_{gs} .

R_s is the (bulk + ohmic) parasitic resistance of the source.

R_g is gate metallization resistance (effective)


note that for velocity-limited transistor, $\frac{v_{sat}}{l_g} = \frac{g_m}{C_{gs}}$

Biasing an FET


we need to bias the device - e.g.

force some desired V_{gs} & V_{ps}


- hence I_D is then set.

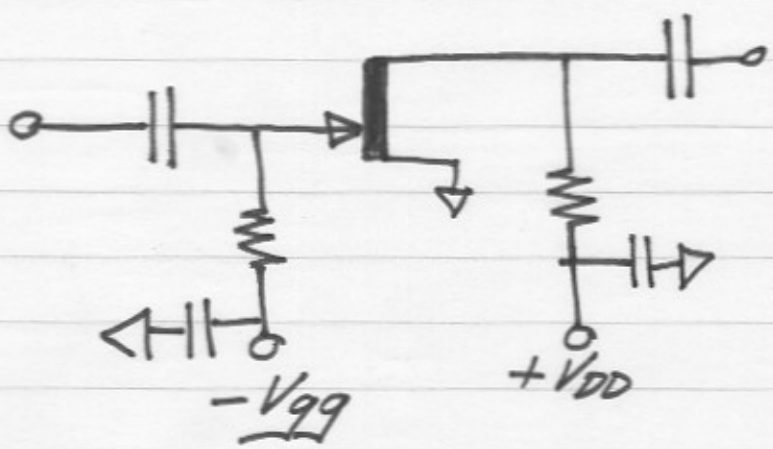

or

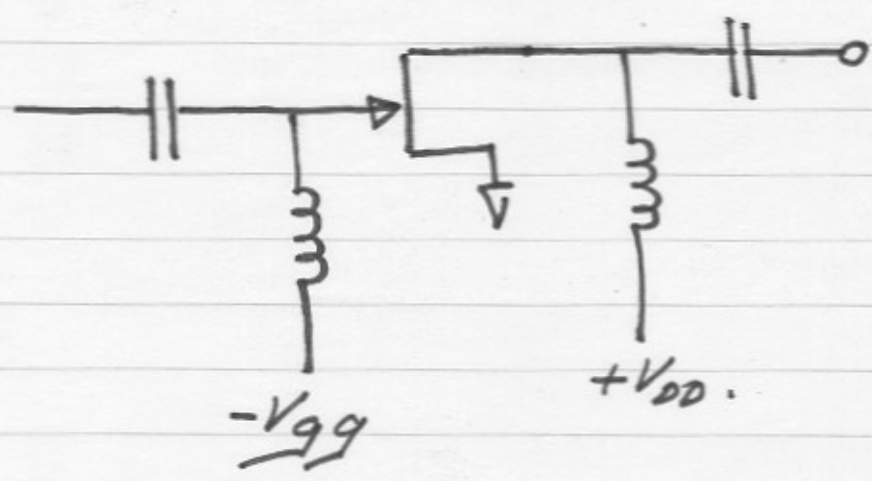

(6)

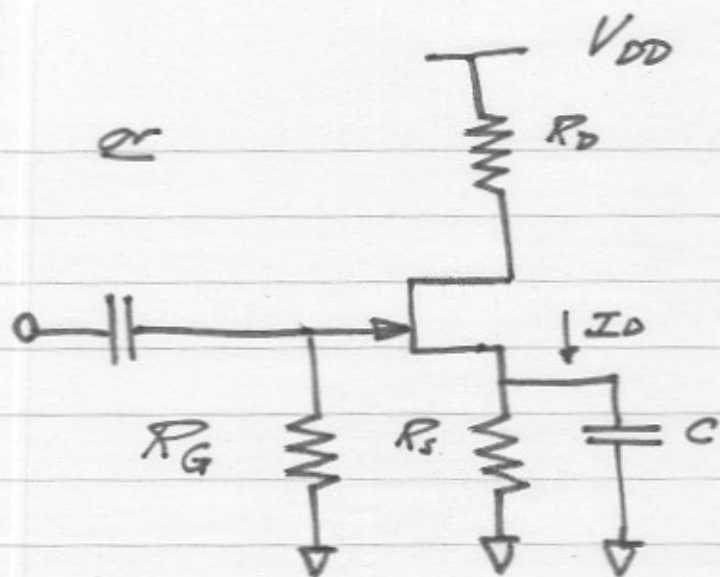


R_S is a "self-bias" resistor which

$$\text{fixes } V_{GS} = -I_D R_S$$

in order to obtain a negative gate-source voltage without a negative supply.

The problem: wiring inductance is introduced in the source circuit. This will become significant when $\omega L \sim \frac{1}{I_D} \cdot \frac{1}{g_m}$ which is generally a very small inductance!

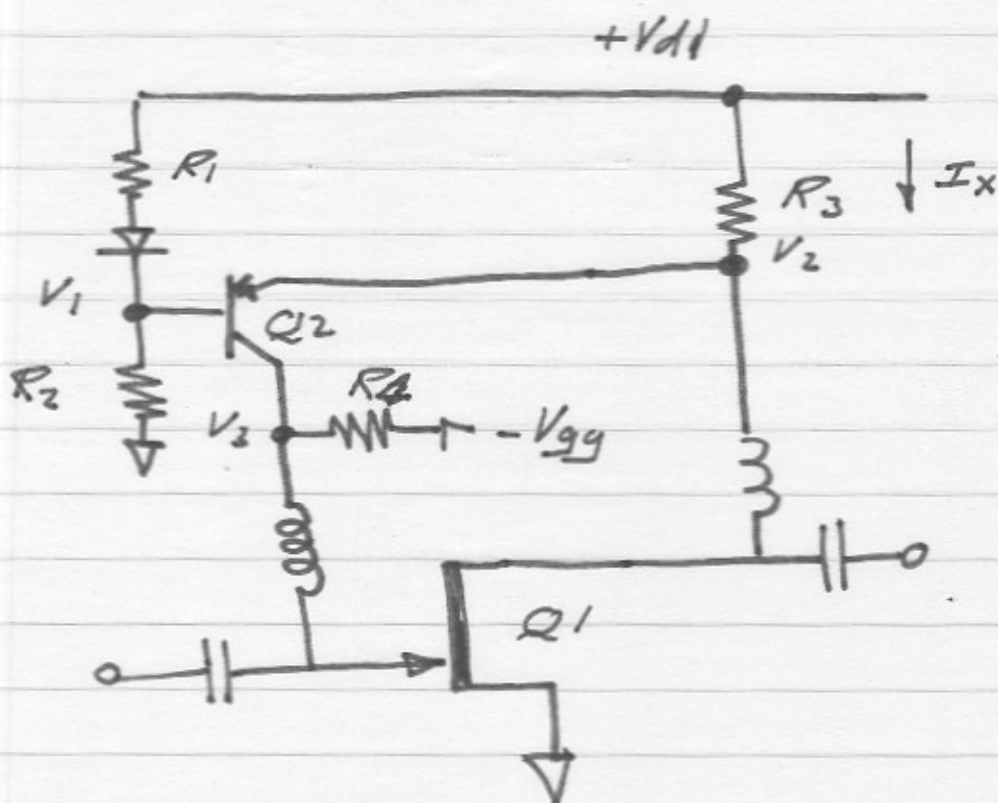Active biasing is very common in microwave systems for precise bias control:



$$V_1 = \frac{R_2}{R_1 + R_2} (V_{DD} - V_{be})$$

$$\text{make } \frac{R_2}{R_1 + R_2} \geq 0.8$$

$$V_2 = V_1 + V_{be} = V_{\text{drain}}$$

$$I_x = (V_{DD} - V_2) / R_3$$


$$I_{c2} = (V_{g1} + V_{gg}) / R_4$$

$$I_D = I_x - I_{c2}$$

$$\text{Make } I_{c2} \ll I_x.$$


... This can also be done with op-amps etc.

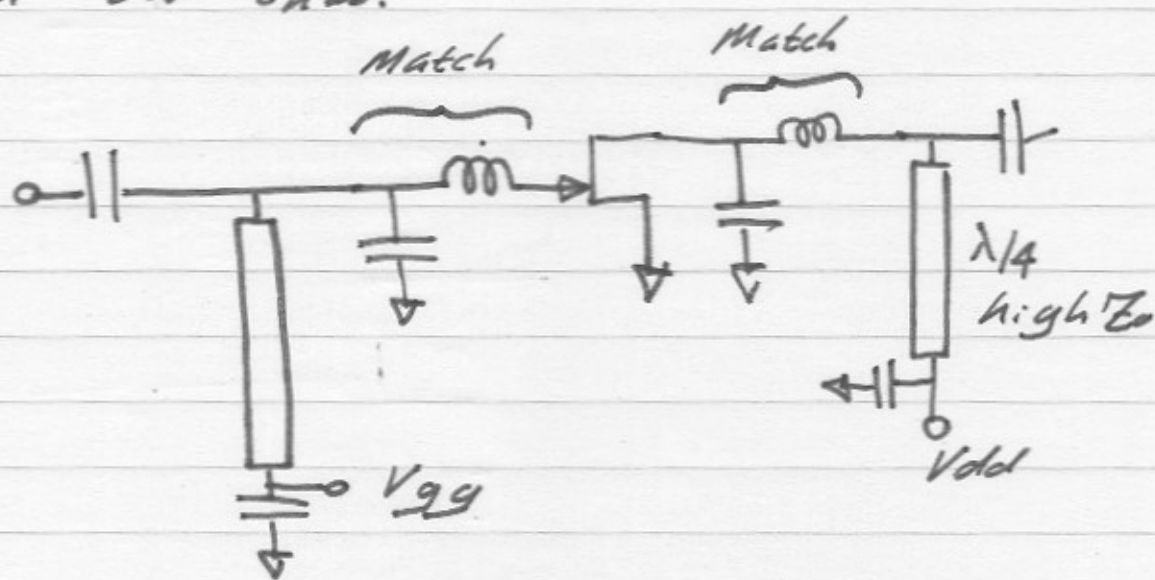LCs trees were shown on the prior page.
 where narrow bandwidths are required, we
 can do this:




this is necessarily very frequency-selective.

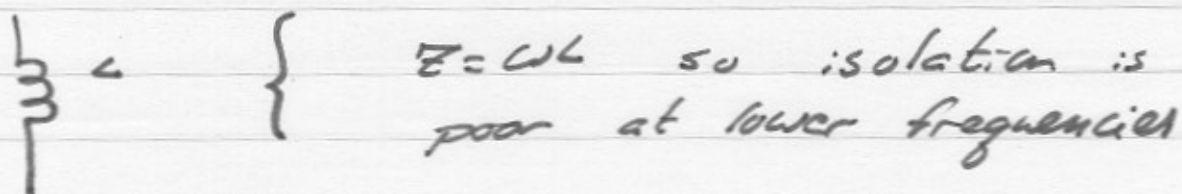Inductors can be used for bias networks too




so we want big L ! (?)

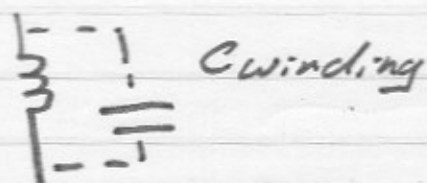

... big inductors have big parasitic winding capacitances $C_{winding}$. The network resonates


(\rightarrow zero impedance) at $\omega_{par} = (L C_{winding})^{-1/2}$

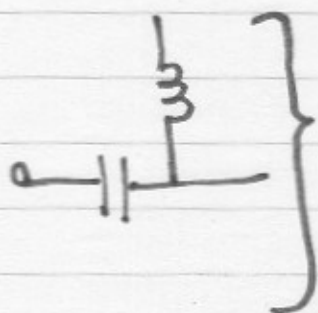so the problem is getting a wide bandwidth with inductors.



Commercial bias tees have bandwidths of e.g. 45 MHz - 60 GHz.

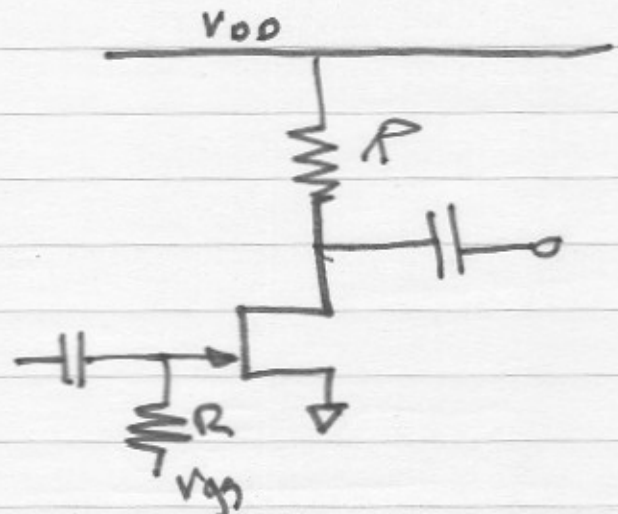If we want very-low-frequency response, we must use resistive biasing:



the penalties:

- 1) DC power is dissipated in R.
- 2) R loads the high-frequency circuit.


So we have biased the device:

small-signal models quantify the changes in the device terminal currents (with respect to the steady-state bias currents) in response to changes in the applied terminal voltages.

$$\frac{\partial I_{DRAIN}}{\partial V_{GS}} \triangleq g_m = \frac{2 I_{DSS} \left(1 - \frac{V_{GS}}{V_p}\right) (1 + \lambda V_{DS})}{V_p}$$

$$\frac{\partial I_{DRAIN}}{\partial V_{DS}} \triangleq G_{DS} = \frac{I_D}{1 + \lambda V_{DS}} \approx I_D \lambda V_{DS}$$


If square-law model

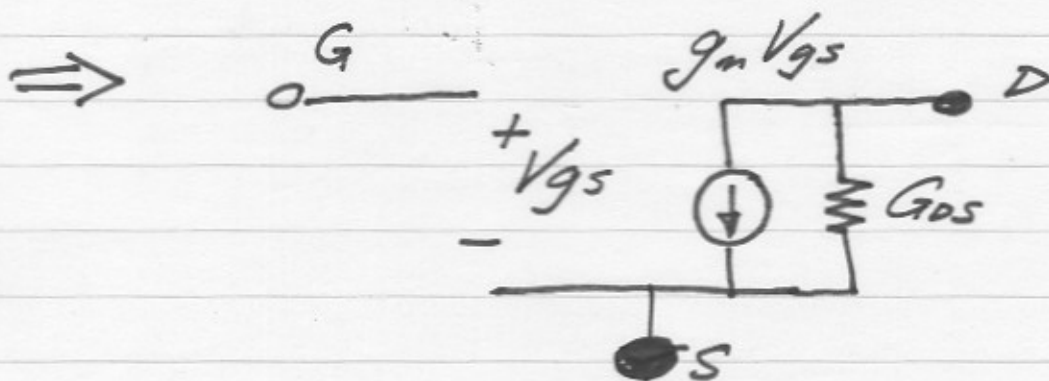

The reader is warned of the unreliability of the square-law model.

users tend to refer to an extensive database of experimentally-determined parameters.



Bipolar

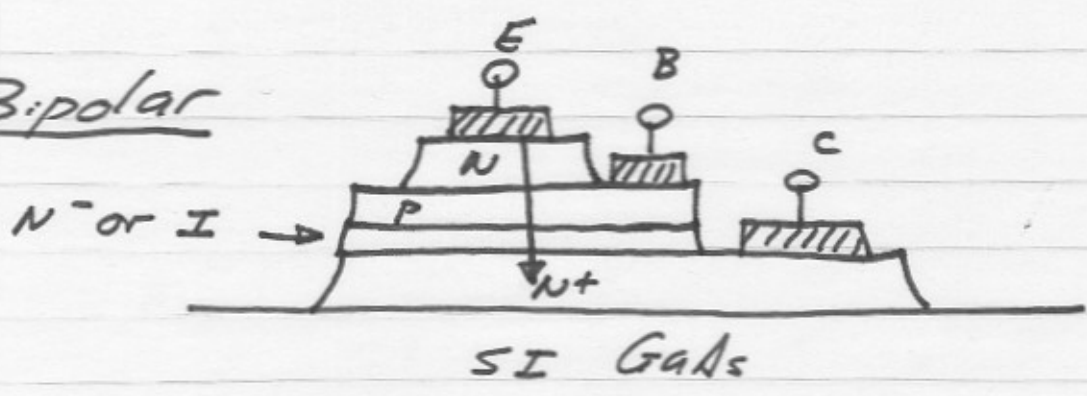

If $V_{cb} > 0$ (cb junction reverse-biased)

then $I_c \approx I_{se} \left[\exp \left\{ \frac{q V_{be}}{kT} \right\} \right] (1 + \lambda V_{ce})$

$I_B \approx I_c / \beta$

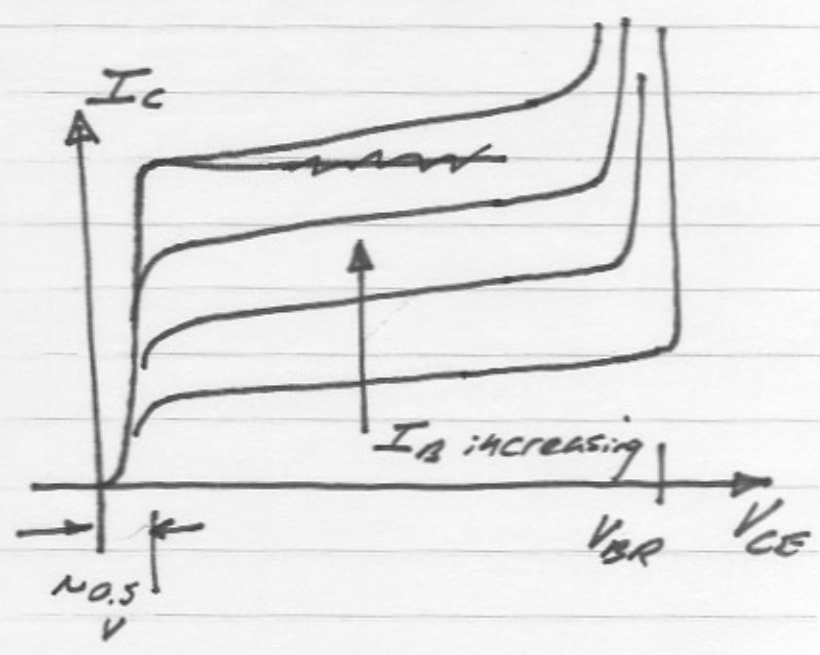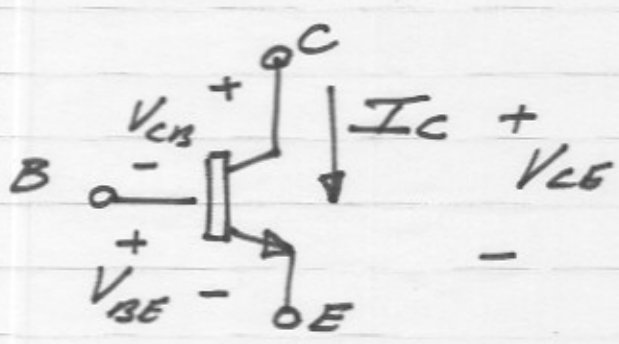

Normal operation: $0.5V < V_{ce} < V_{BR}$
& $V_{be} \approx 0.7$ Volts.

Bias circuit must force (set) V_{ce} and I_c
not V_{ce} and V_{be} .




Bipolar Bias examples

Must force V_{CE} & I_c

Never V_{BE} : $I_c = I_{se} e^{V_{be}/V_T}$ but
 I_{se} varies exponentially with temperature.

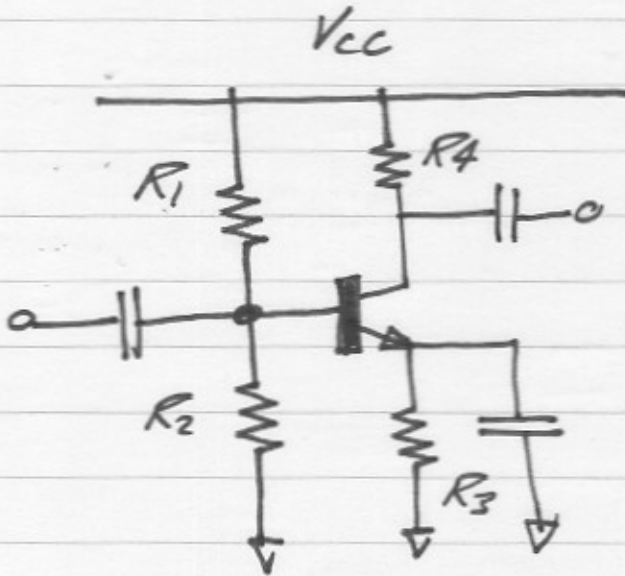Never I_B : $I_c = \beta I_B$ but β varies
 tremendously from device to device &
 also varies with temperature



$$V_{base} = V_{cc} \cdot \frac{R_2}{R_1 + R_2}$$

if I_{BQ} is small.


$$V_{emitter} = V_{base} - V_{be}$$

$$I_E = V_{emitter} / R_3$$

$$\approx I_c$$

$$V_{collector} = V_{cc} - I_c R_4$$

or:

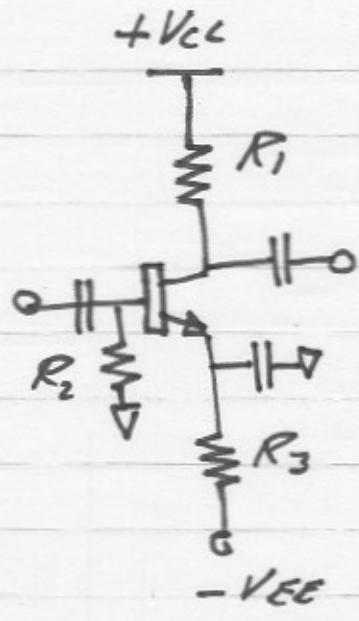

$V_{be} \approx 0$ if $I_B \cdot R_2$ small


$V_{emitter} = -V_{be}$

$I_E = (V_{EE} - V_{be}) / R_3$
 $\approx I_C$

$V_c = V_{cc} - I_c R_1$

(the Possibilities are endless)

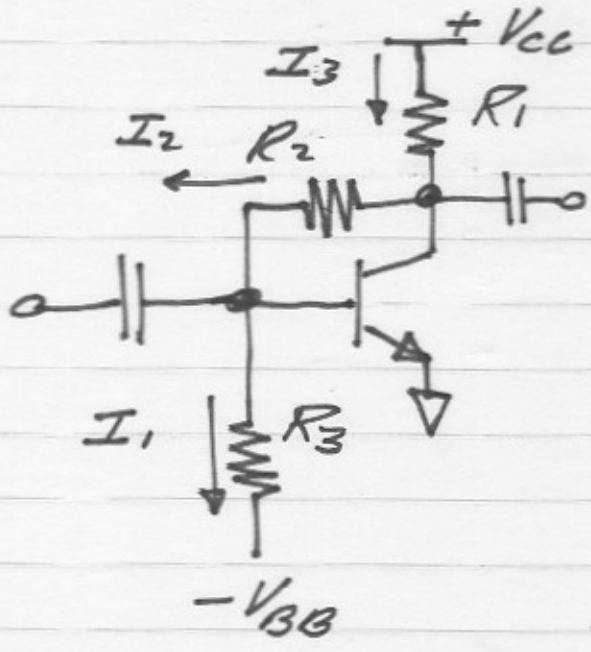feedback dc biasing - very handy with microwave feedback amplifiers:



$I_1 \approx (V_{be} + V_{BB}) / R_3$


$I_2 \approx I_1$ if I_B is small

$V_c = V_{be} + I_2 R_2$

$I_3 = (V_{cc} - V_c) / R_1$

$I_c = I_3 - I_2$

or we can use feedback:

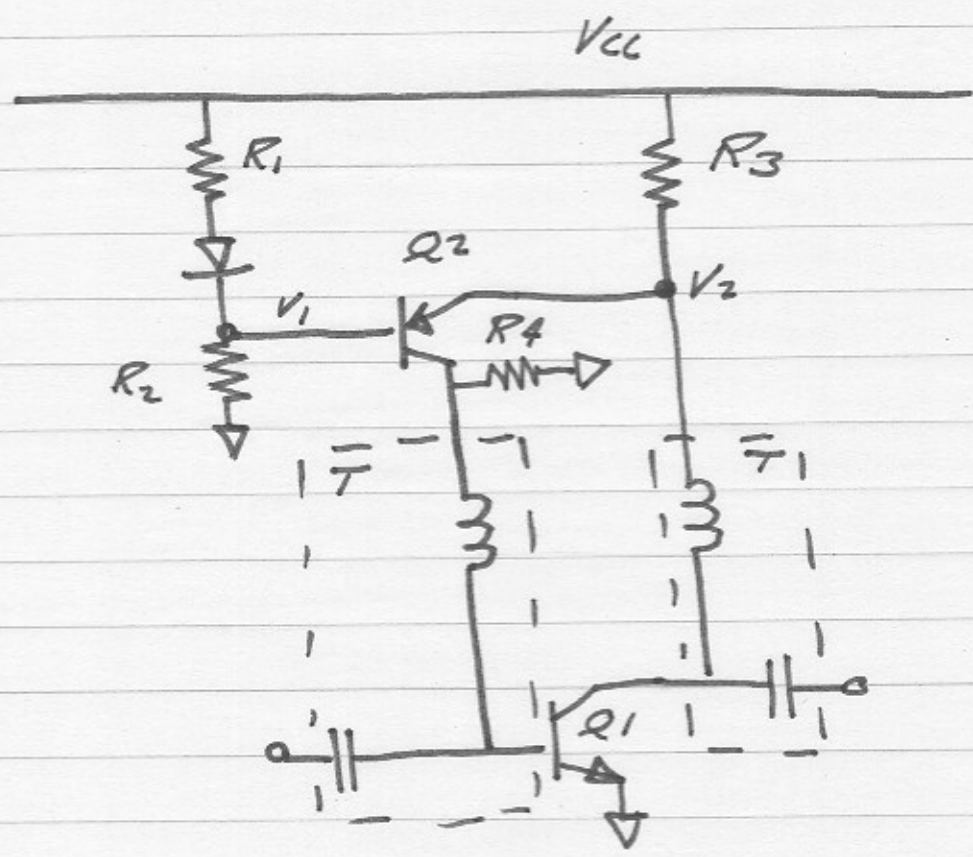

$$V_1 = \frac{R_1}{R_1 + R_2} (V_{CC} - V_{BE}) \quad \text{if } I_B \text{ small}$$

$$V_2 = V_1 + V_{BE} = V_{C1}$$

$$I_{C2} = V_{BE} / R_4 + I_{B1}$$

$$I_{C1} = \frac{V_{CC} - V_2}{R_3} - I_{C2}$$

Feedback loop must be designed not to oscillate!

Bipolar small-signal Parameters:


$$\frac{\partial I_c}{\partial V_{be}} = \frac{\partial}{\partial V_{be}} \left[I_{se} e^{V_{be}/V_T} \right] = I_c / V_T = g_m$$

$$\frac{\partial I_b}{\partial V_{be}} = \frac{\partial}{\partial V_{be}} \left[\frac{I_{se}}{\beta} e^{V_{be}/V_T} \right] = \frac{g_m}{\beta} = \frac{1}{r_{b'e}}$$

where $V_T = kT/q = 26 \text{ mV} @ 300 \text{ K}$

$$\frac{\partial I_c}{\partial V_{ce}} \approx \frac{I_c}{V_A} = 1/r_{ce}$$

\nearrow
 $\approx 25-100 \text{ V}$

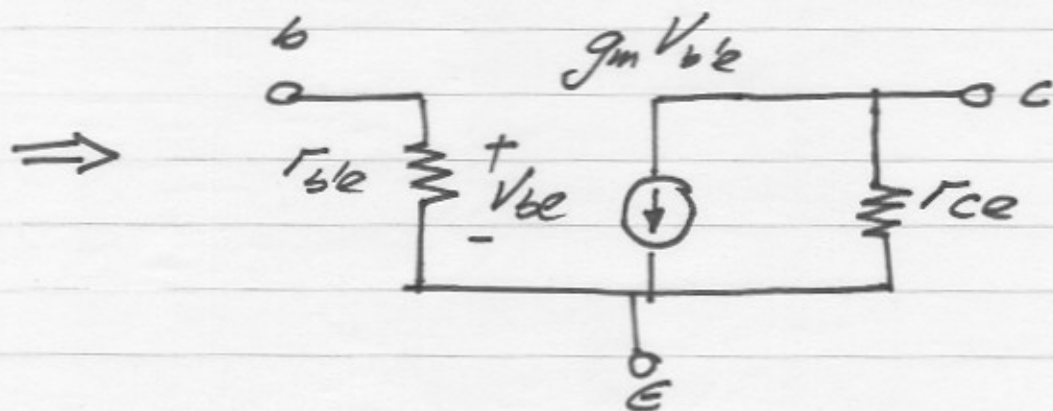

Origin of parasitics:

$$\tau_{base} \triangleq \frac{Q_{base} \text{ (stored)}}{I_c} \approx \frac{W_{base}^2}{2 D_n}$$

electron diffusivity in base

$\tau_{collector}$ = collector depletion layer transit time

$$= \frac{\text{collector depletion width}}{2 \times \text{electron velocity}}$$

$$= W_{dc} / 2 v_{set} \leftarrow v_{set} \sim 10^7 \text{ cm/sec} \quad (0.1 \mu\text{m/ps})$$

C_{cb} = base-collector junction capacitance



$C_{be}(\text{dep})$ = emitter-base depletion capacitance.

R_{ex} = emitter parasitic resistance.

$R_{b'b}$ = base parasitic series resistance.

(draw pictures of these)

τ_{base}

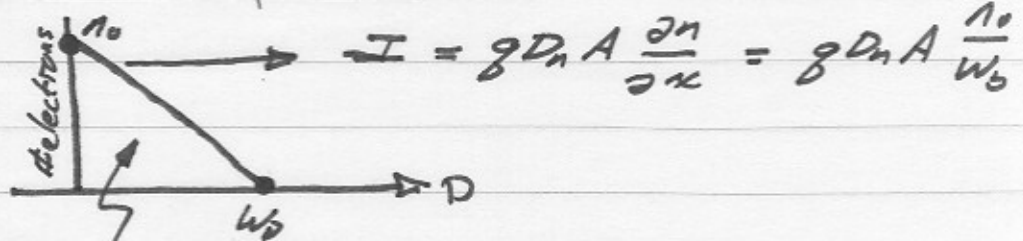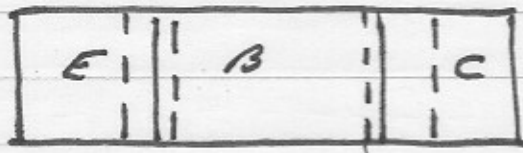


$$I = q D_n A \frac{\partial n}{\partial x} = q D_n A \frac{n_0}{W_b}$$

$$Q_s = q A n_0 W_b / 2$$

$$\Rightarrow \tau_b \triangleq Q_s / I = W_b^2 / 2 D_n + W_b / v_{sat}$$

~~Surprisingly, the W_b / v_{sat} term is dominant in modern HBTs.~~

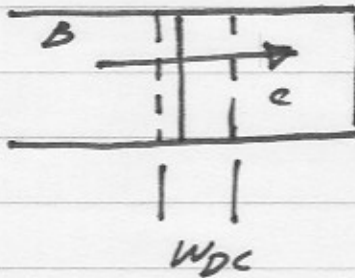
τ_c : analysis is a little harder (we will omit)




detailed analysis is necessary to get the $(1/2)$ factor.

$$\frac{Q_{stored}}{I} = W_{dc} / v_{sat}$$


ACB

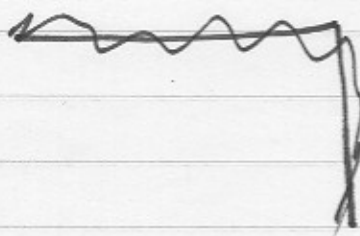

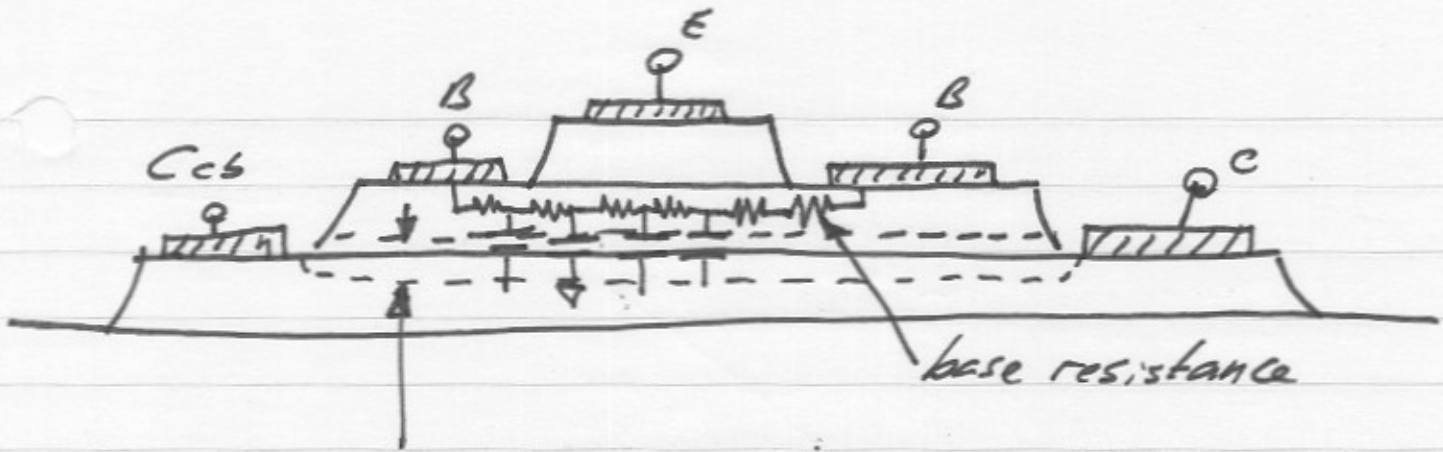


C_{cb} junction capacitance

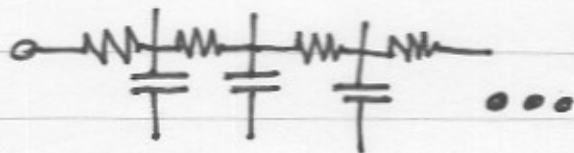
* note that base resistance & C_{cb} are a distributed network, thus:




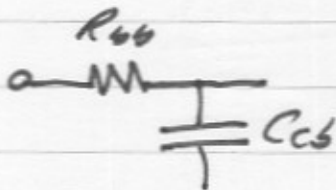
* for simplicity, this is replaced by a lumped R-C network with 2-4 elements





or

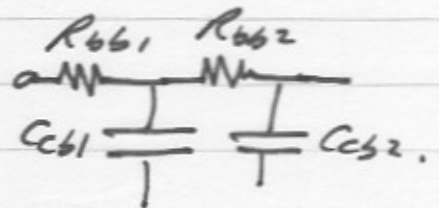

Hybrid- π Models (Derived)

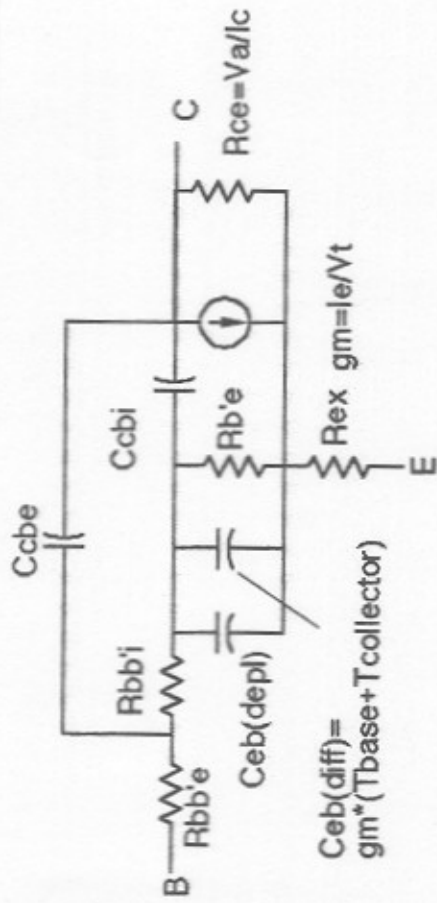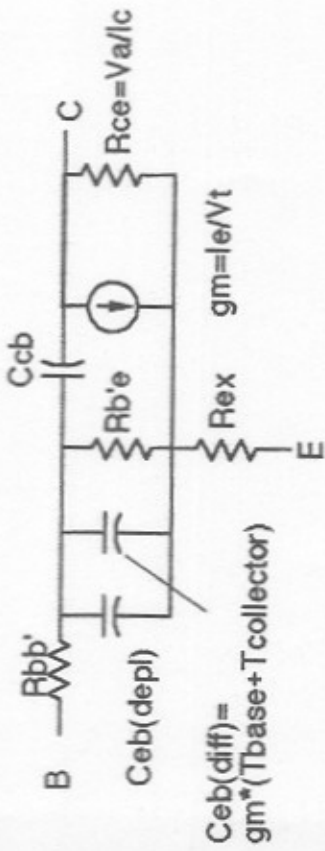


T -Models: Physically-derived.

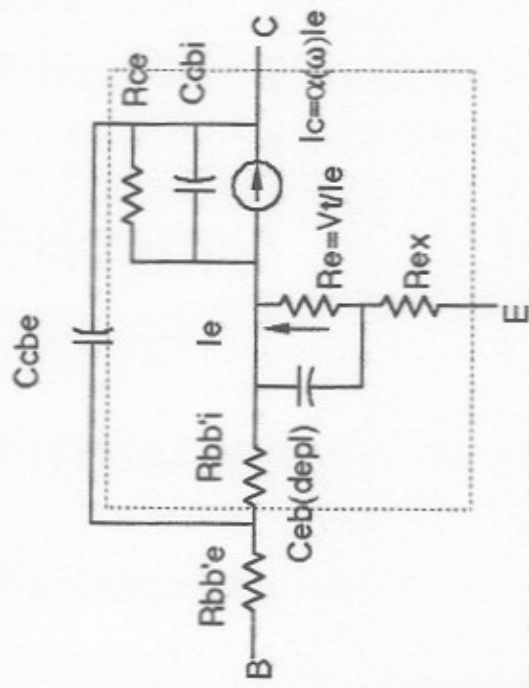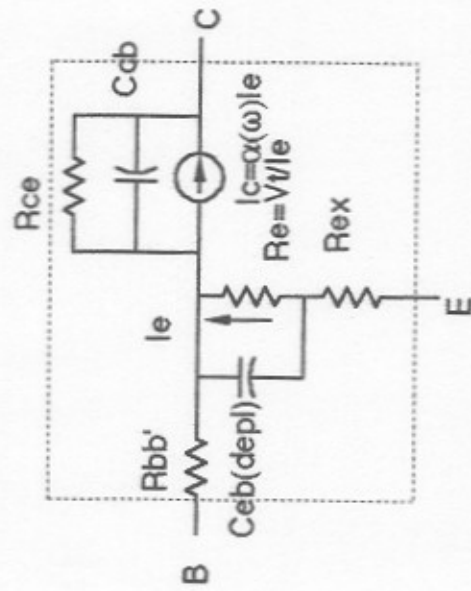

$$g(\omega) \approx g_0 \cdot \frac{1}{1 + j\omega\tau_3} \cdot e^{-j\omega\tau_c} = \frac{\sin(z\omega\tau_c)}{z\omega\tau_c}$$

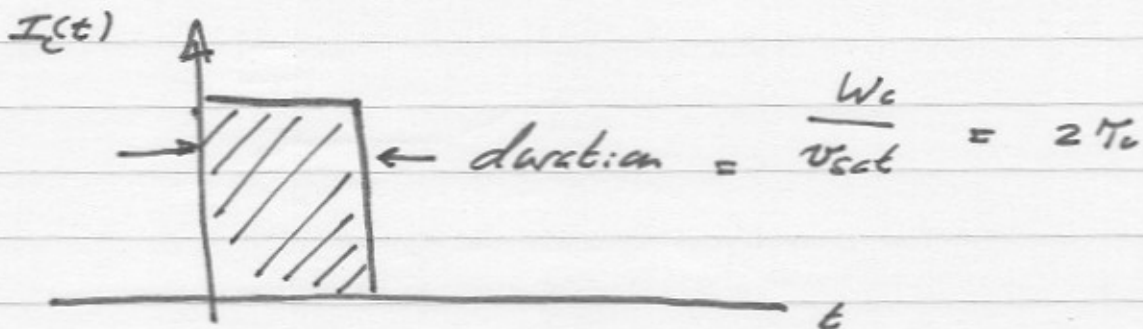If an impulse of charge enters the collector-space-charge region from the base, the collector terminal current is




the Fourier transform of this is

$$e^{-j\omega\tau_c} \cdot \frac{\text{sinc}(2\omega\tau_c)}{2\omega\tau_c}$$

How do we arrive at the hybrid- π Model? We start with the T-Model, and separate out the network below:

$$\alpha(\omega) I_E$$

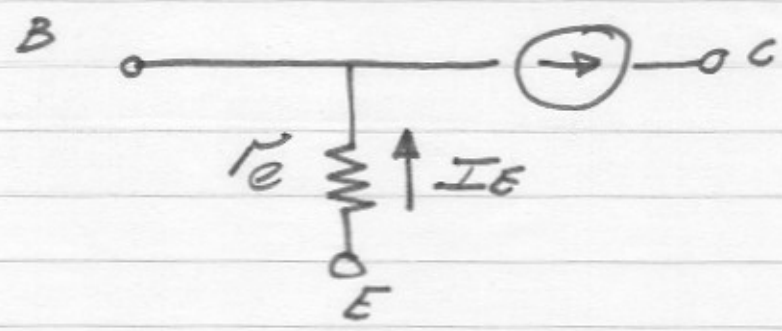

We compute the Y -parameters of this network, approximate with a Taylor series to first order in $\omega(\tau_{base} + \tau_{collector})$ and obtain




and add back the remaining elements.


This is illustrated on the (optional) following pages.

Going between common-base T-model & hybrid- π

full model:

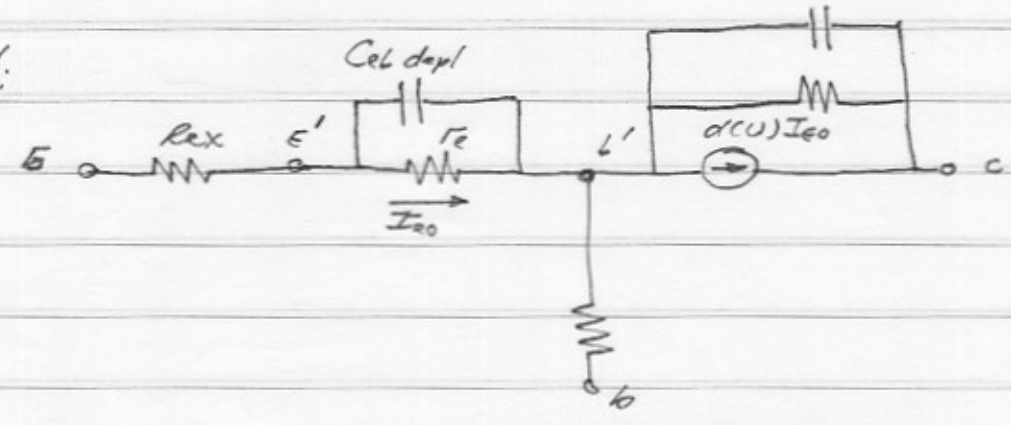

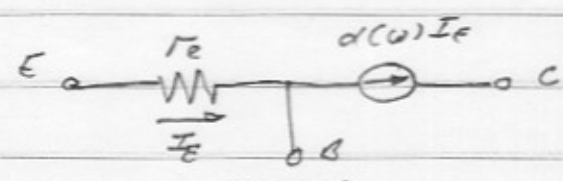first work only with E'B'C transistors and put aside $C_{cb'}$ & $C_{E'b'}$ for the time being.




$$r_e = V_T / I_{E,DC}$$



$$d(\omega) = \frac{\alpha_0 e^{-j\omega\tau_{collector}}}{1 + j\omega\tau_{base}}$$

$$\times \frac{\sin \omega\tau_{collector}}{\omega\tau_{collector}}$$
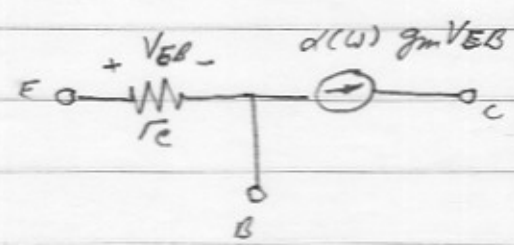
$$\approx \frac{\alpha_0}{1 + j\omega(\tau_{base} + \tau_{collector})} \approx \frac{\alpha_0}{1 + j\omega\tau_f}$$



$$g_m = 1/r_e$$

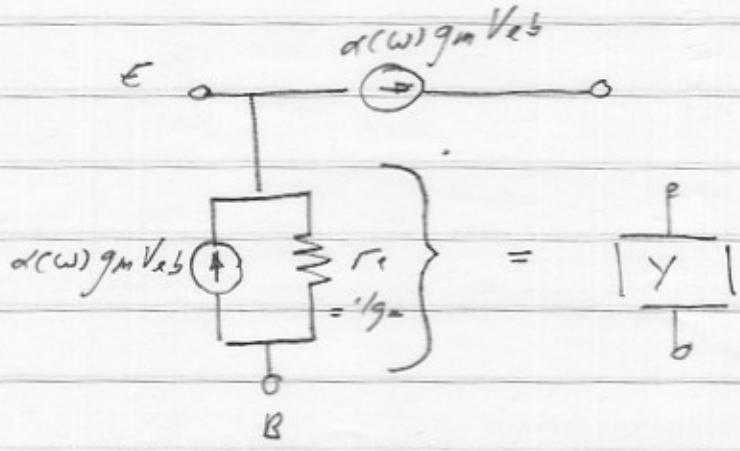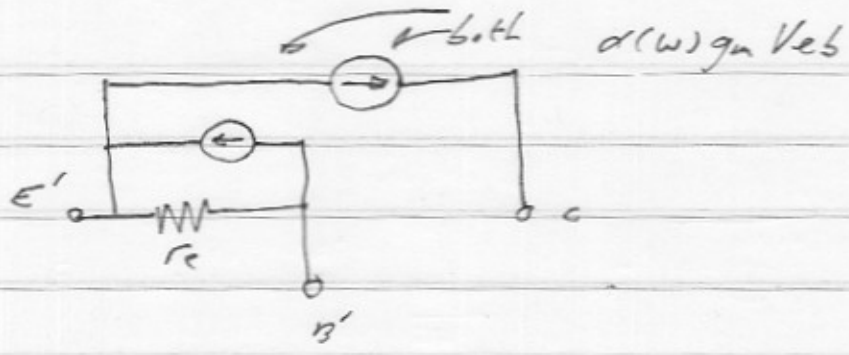

$$Y = g_m [1 - \alpha(\omega)] \approx g_m \left[\frac{1 + j\omega T_f - \alpha_0}{1 + j\omega T_f} \right]$$

$$= g_m (1 - \alpha_0) \frac{1 + j\omega T_f / (1 - \alpha_0)}{1 + j\omega T_f}$$

$$\frac{1}{1 - \alpha_0} = \beta_0$$


$$= \frac{g_m}{\beta} \frac{1 + j\omega \beta T_f}{1 + j\omega T_f}$$

$$\approx \frac{g_m}{\beta} + j\omega g_m T_f \quad \text{for } f < f_{\beta}$$


$$Y = \frac{1}{r_{b'e}} + j\omega C_{b'e}^{\text{diff}}$$

$$C_{b'e}^{\text{diff}} = g_m \tau_f$$

$$r_{b'e} = \beta / g_m$$

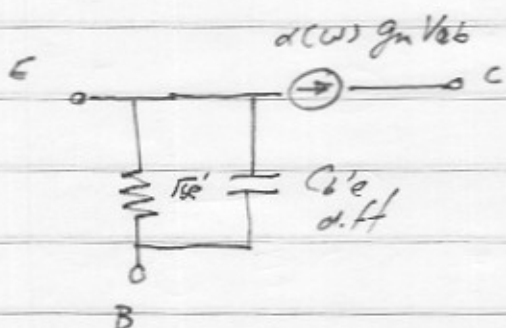

redraw, and re-add other parasitics:

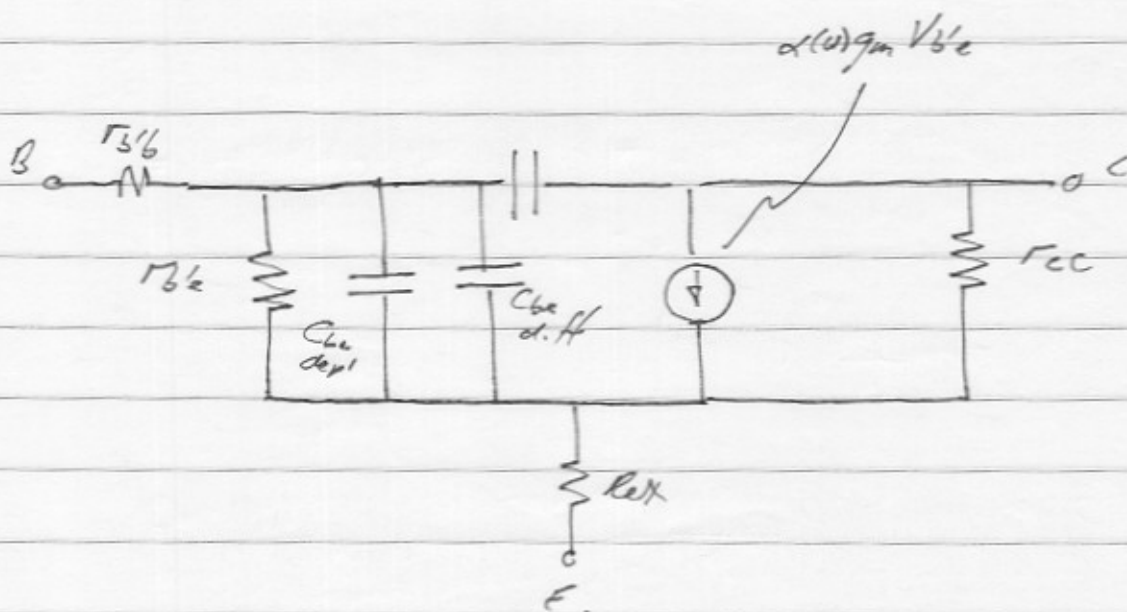

Device figures-of-merit


short-circuit current gain cutoff frequency, f_T

Rigorous definition: $\|H_{21}(f_T)\| = 1$

FET: $f_T \approx \frac{g_m}{2\pi(C_{gs} + C_{gd})} \approx \frac{g_m}{2\pi C_{gs}} \approx \frac{v_{sat}}{l_{gate}}$

Bipolar: $f_T \approx \frac{g_m}{2\pi(C_{be,depl} + C_{be,diff} + C_{bc})}$
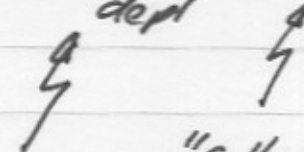
$$= \frac{1/2\pi}{r_e C_{be,depl} + r_e C_{bc} + \tau_{base} + \tau_{collector}}$$




"emitter charging time" "collector charging time"

$$(r_e = 1/g_m)$$

expressions are approximate & assume "typical" magnitudes of various parasitics.

Maximum available gain (if it exists!)

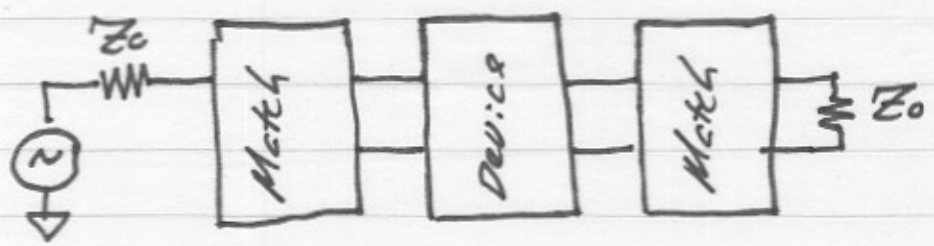

we will discuss this much more carefully later.

for now, $G_{max} = P_{out} / P_{in}$ given matching on both input and output. G_{max} (if it exists) is the maximum power gain we can obtain.

G_{max} decreases with frequency.

when $G_{max} \geq 1$, we can use the device to build an amplifier or oscillator. If $G_{max} < 1$, the device is useless. f_{max} is the frequency at which $G_{max} = 1$. Hence:

- $f < f_{max}$ device is useful.
- $f > f_{max}$ device is useless.

Again, for "typical" values, such that secondary parasitic effects are negligible, we have:

for FET's

$$f_{max} \approx \frac{f_T}{2 \sqrt{(R_i + R_g + R_s) C_{gs} + 2\pi f_T R_g C_{gd}}}$$

for Bipolars ($\beta \gg 1$)

$$f_{max} \approx \frac{f_T}{2 \sqrt{\underbrace{(R_{ex} + R_{b'b})/R_{ce}}_{\text{usually negligible}} + 2\pi f_T r_{b'b} C_{bc}}}$$

$$= \sqrt{\frac{f_T}{8\pi r_{b'b} C_{bc}}}$$

"base-collector time constant"