

Name: \_\_\_\_\_

ECE 124A–Fall 2012  
Prof. K. Banerjee

Perm No. \_\_\_\_\_

**UNIVERSITY OF CALIFORNIA, SANTA BARBARA**  
Department of Electrical and Computer Engineering

**MIDTERM EXAMINATION-ECE124A**

Room: ESB-1003, November 9, 4:00-6:00 PM

**READ CAREFULLY:**

- This is a **CLOSED BOOK** Exam. Any form of notes is not allowed. Calculators OK.
- **READ** the questions carefully before answering. Include all your answers in locations specified on these pages. Show **ALL WORKING** used to arrive at answers. Use space provided for all working. Use the back sides if necessary. There are 9 pages including the cover page. Be sure to write Your **NAME/Perm No.** on **EVERY PAGE**.

Question	Scores
#1	/50
#2	/25
#3	/25
TOTAL	/100

*Good Luck!*

Name: \_\_\_\_\_

ECE 124A–Fall 2012  
Prof. K. Banerjee

Perm No. \_\_\_\_\_

**1. Part I: (30 pts) (3 pts each) (suggested time: 25 minutes)**

For each question, choose ALL the CORRECT statements among the four. Fill the table below with your answers:

Question	1	2	3	4	5	6	7	8	9	10
Answer										

(Completely correct: 3pts; Partially Correct: 1pt; Any wrong options chosen: 0 pt)

**1) (Moore's law) Select the right statement(s):**

- A. Transistors on Lead Microprocessors double every 2 years.
- B. Die size grows by 2X every 2 years to satisfy Moore's Law.
- C. Lead Microprocessor frequency doubles every 2 years.
- D. Technology shrinks by 0.7/generation.

**2) (CMOS processing and layout) Select the right statement(s):**

- A. NMOS transistors are fabricated on n-type substrate.
- B. PMOS transistors have p<sup>+</sup>-type source and drain.
- C. Uninterrupted diffusion strips are possible only if there exists a common Euler path in the logic graph.
- D. Gate of a transistor can be connected by a metal-to-poly via.

**3) (Semiconductor physics) Select the right statement(s):**

- A. A material is metallic if it has a half-filled energy band.
- B. If the concentrations of donors and acceptors in a silicon sample are  $N_D$  and  $N_A$ , respectively, then the electron density is  $n_0 \approx N_D - N_A$  at room temperature.
- C. The probability  $F(E)$  of occupation of a state of energy  $E$  is less than 0.5 ( $F(E) < 0.5$ ) if  $E > E_F$ .
- D. Drift current arises from electron motion due to differences in carrier concentration.

**4) (Device physics, P-N Junction) Select the right statement(s):**

- A. In a P-N junction, the charges in the depletion region on p-side are due to positive fixed ions.
- B. In a P-N junction in equilibrium, electron diffusion current and hole drift current are in the same direction.
- C. The width of the depletion region is increased if the P-N junction is under forward bias.
- D. P-N junction capacitance reduces with reverse bias.

Name: \_\_\_\_\_

ECE 124A–Fall 2012  
Prof. K. Banerjee

Perm No. \_\_\_\_\_

**5) (Device physics, MOS) Select the right statement(s):**

- A. Work function of a semiconductor is the energy required to take electron from conduction band level to free space.
- B. At equilibrium, Fermi levels line up in a MOS structure.
- C. When inversion happens in NMOS, density of electrons on surface equal the density of holes in bulk.
- D. Holes “accumulate” on Si surface if PMOS is in accumulation region.

**6) (Threshold voltage of MOSFET) Select the right statement(s):**

- A. Increasing of fixed positive charged ions at boundary between oxide and substrate will increase the absolute value of threshold voltage of PMOS.
- B. For NMOS,  $V_T$  can be increased by adding acceptor ions in the channel.
- C. the absolute value of PMOS threshold voltage increases as  $V_{SB}$  increases.
- D. For NMOS, if  $t_{ox}$  increases,  $V_T$  will increase (assuming  $Q_{ox}$  is zero).

**7) (MOSFET currents) Select the right statement(s):**

- A. MOSFET current is mainly due to motion of majority carrier.
- B. Velocity saturation current varies quadratically with  $V_{GS}$ .
- C. In short channel transistors, the mechanism of current saturation is velocity saturation.
- D. In linear region, drain current increases almost linearly with  $V_{GS}$ .

**8) (MOSFET capacitance) Select the right statement(s):**

- A. Gate capacitance is due to diffusion capacitance.
- B. Gate capacitance in saturation region is smaller than that in linear region.
- C. In NMOS, drain diffusion capacitance increases if drain to body ( $V_{DB}$ ) voltage increases.
- D. The diffusion capacitances are parasitic capacitances, so they do not affect circuit performance.

**9) (MOSFET Leakage) Select the right statement(s):**

- A. Gate leakage is independent of temperature ( $T$ ).
- B. Subthreshold swing ( $S$ ) of MOSFET cannot be greater than 60 mV/decade.
- C. Electron mobility decreases with increase in  $T$ , hence,  $I_{DSAT}$  of NMOS decreases as  $T$  increases.
- D. Junction leakage is less significant than gate and subthreshold leakage.

**10) (CMOS Inverter) Select the right statement(s):**

- A. Switching threshold ( $V_M$ ) decreases if NMOS channel width reduces.
- B. VTC shifts to left if PMOS oxide thickness reduces.
- C.  $V_{IL}$  increases if PMOS is at a lower temperature than NMOS.
- D. For a CMOS inverter in highest-gain region, both NMOS and PMOS are in resistive region.

Name: \_\_\_\_\_

ECE 124A–Fall 2012  
Prof. K. Banerjee

Perm No. \_\_\_\_\_

**1. Part II: (10 pts) (suggested time: 10 minutes)**

What is a Tristate Buffer? Draw a schematic of the gate and the truth table. Using transistor level schematic, illustrate how this gate can be used to build i) an inverter and ii) a 2:1 Multiplexer.

Name: \_\_\_\_\_

**ECE 124A–Fall 2012**  
**Prof. K. Banerjee**

Perm No. \_\_\_\_\_

**1. Part III: (10 pts) (suggested time: 10 minutes)**

An unknown element X has been discovered in the planet of *Tatooine*. When an X atom sits on a lattice site in a Germanium crystal, it can act as either a donor or an acceptor.  $E_D$  and  $E_A$  levels both exist for the atom X and both are close to the middle of the Germanium bandgap. If a small concentration of X is placed in an n-type Germanium crystal, will the X behave as a donor or an acceptor? Explain with band diagrams.

Name: \_\_\_\_\_


ECE 124A–Fall 2012  
Prof. K. Banerjee

Perm No. \_\_\_\_\_

 **2. (25 pts) (suggested time: 30 minutes)**

Consider the PMOS resistive-load inverter shown below.

$$\begin{aligned}V_{CC} &= 2.5\text{V} \\V_{T0p} &= -0.8\text{ V} \\ \lambda &= 0 \\k_p' &= 74\ \mu\text{A}/\text{V}^2 \\R &= 25\ \text{k}\Omega \\L &= 2\ \mu\text{m} \\W &= 25\ \mu\text{m}\end{aligned}$$



**For PMOS in linear region:**  $I_D = k_p' \left(\frac{W}{L}\right) [(V_{GS} - V_{TP})V_{DS} - \frac{1}{2}V_{DS}^2]$

**For PMOS in saturation region:**  $I_D = k_p' \left(\frac{W}{L}\right) (V_{GS} - V_{TP})^2 = k_p' \left(\frac{W}{L}\right) (V_M - V_{CC} - V_{TP})^2$

**(a)** Find the values of  $V_{OL}$  ( $=V_{out}$  when  $V_{IN}=2.5\text{V}$ ),  $V_{OH}$  ( $=V_{out}$  when  $V_{IN}=0\text{ V}$ ) **(8 pts)**

**Hint:** Magnitude of the currents in PMOS and the resistor should be same.

Name: \_\_\_\_\_

ECE 124A–Fall 2012  
Prof. K. Banerjee

Perm No. \_\_\_\_\_

(b) Find the values of  $V_M$ . (9 pts)

(c) Find a new value for R such that  $V_{OH} = 2.0V$ . (8 pts)


Name: \_\_\_\_\_

Perm No. \_\_\_\_\_

 **3. (25 pts) (suggested time: 30 minutes)**

Consider the CMOS logic gate shown below.

- Determine the logic function of the gate.
- Draw the pull-down network (ensure that you use a **minimum** number of **equal size** transistors).
- What is the logical effort of this gate?
- Two gates and a unit size inverter are in a circuit path as shown in the figure in the next page (no branching). Find the gate sizes  $a$  and  $b$  to achieve the minimum delay, assuming  $C_L/C_{in}=10$ .





Name: \_\_\_\_\_

Perm No. \_\_\_\_\_

