
 
 


Structure of silicon crystal

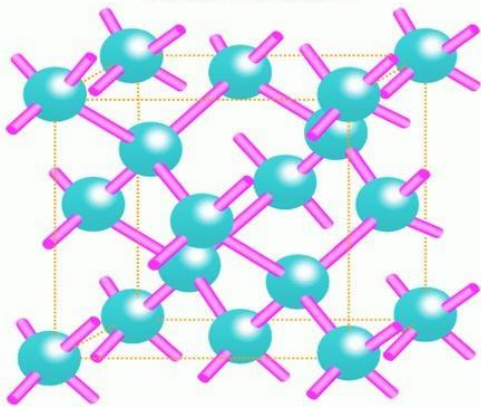


# *ECE 122A*

# *VLSI Principles*

## *Lectures 16*

Prof. Kaustav Banerjee  
Electrical and Computer Engineering  
University of California, Santa Barbara  
*E-mail: [kaustav@ece.ucsb.edu](mailto:kaustav@ece.ucsb.edu)*

# Semiconductor Memories....

 

# Memory Design...

- ❑ Increasing number of transistors in uprocessors are devoted to **cache memories**....more than 60%, see ITRS for more details.....
- ❑ At the **system level**: high-performance workstations and desktops have **several Terra-bytes** of memory
- ❑ **Audio (MP3), Video players (MPEG4) and GPUs** require large amount of memory
- ❑ Can we store Memory using **registers**? ....yes but the **area** required will be excessive (need > 10 transistors/bit)
- ❑ Memory cells are therefore combined into **large arrays**, which minimizes the overhead caused by the peripheral circuits and increases **storage density**
- ❑ Memory design can be classified as **high-performance, high density, low-power circuit design**

# *Memory Classification*

- Size
- Timing Parameters
- Function
- Access Pattern


# Memory Size

- Depends on the **level of abstraction**
- **Bits**: (used by circuit designers) are equivalent to the number of individual cells (FFs or Registers) to store data
- **Bytes**: (used by chip designers) are groups of 8 or 9 bits or their multiples: Kbyte, Mbyte, Gbyte, Tbyte
- **Words**: (used by system designers) represent a basic computational entity. For example, a group of **32 bits represent a word** in a computer that operates on 32 bit data

# Timing Parameters

- ❑ **READ-Access Time:** time it takes to retrieve (read) from the memory. This is equal to the delay between the read request and the moment the data becomes available at the O/P.
- ❑ **WRITE-Access Time:** time elapsed between a write request and the final writing of the input data into the memory
- ❑ **CYCLE Time:** minimum time required between successive reads or writes

# Memory Timing: Definitions

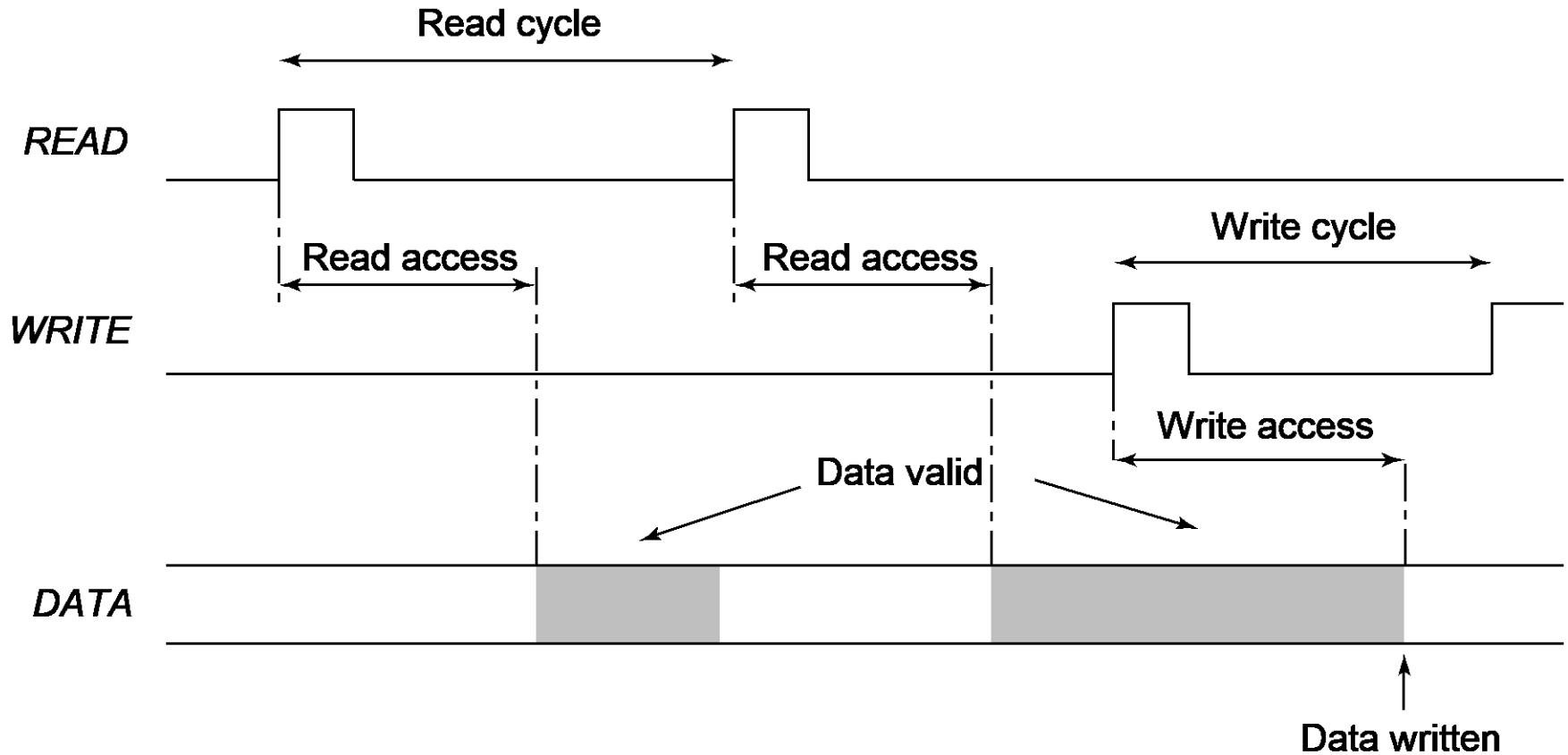

**Note:** Read and Write cycles do not necessarily have the same length but are considered to be equal for simplicity of system design.

# Function

## □ Read-Only Memory (ROM):

- encode the information into the circuit topology-by removing or adding transistors. The topology is hard wired and the **data cannot be modified....can only be read.**
- They belong to the class of **Non-volatile** memories. Disconnection of the supply voltage does not result in a loss of the stored data.

## □ Read-Write Memories (RWM): called as **RAM** (Random-Access Memories).

- **Static** (retains data if V<sub>dd</sub> is retained): example SRAM
- **Dynamic** (needs periodic refreshing): example DRAM
- They use active circuitry to store information and belong to the class of **Volatile** memories.



# Function....cont'd

## □ Non-Volatile Read-Write (NVRWM):

- Recent Non-Volatile Memories can read and write---although write function is substantially slower
- Novel, cheap and dense: Fastest growing among semiconductor memories

## □ Examples:

- EPROM: Electrically Programmable ROM
- E<sup>2</sup>PROM: Electrically Erasable and Programmable ROM
- Flash memory

# Access Pattern

- ❑ **Random-Access (RAM):**
  - memory locations can be read or written in a random manner
  - Most ROMs and NVRWMs allow random access....but “RAM” is used for the RWMs only
- ❑ **Serial Access:**
  - Restricts the order of access. Results in faster access times, smaller area, or allows special functionality
  - Examples: (Video Memories)
    - FIFO (first-in first-out)
    - LIFO (last-in first-out)
    - Shift Register
- ❑ **Content-Addressable Memory (CAM):** (non-random access)
  - Also known as associative memory
  - Doesn't use an address to locate the data.....rather **uses a word of data itself as input**... when input data matches a data word stored in memory array, a MATCH flag is raised
  - Important component of the cache architecture of most microprocessors

# Semiconductor Memory Classification

Read-Write Memory		Non-Volatile Read-Write Memory	Read-Only Memory
Random Access	Non-Random Access	EPROM E <sup>2</sup> PROM FLASH	Mask-Programmed Programmable (PROM)
SRAM  DRAM	FIFO LIFO Shift Register CAM		

***Where does your brain's memory fit into these classification schemes?***

# More Classification


## □ I/O Architecture:

- Based on the number of data input and output ports
- Most memories use a single I/O port
- **Multiport memories** offer higher bandwidth
  - Example: register files used in RISC processors
  - Adds more complexity to the design

## □ Application:


- Embedded Memories in SoCs
- For massive storage (multiples of Tbytes and beyond), more cost effective solutions are to use **magnetic tapes** and **optical disks**---they however, tend to be slower and provide limited access pattern
 
# Semiconductor Memory Trends (up to the 90's)




Memory Size as a function of time:  $\times 4$  every three years
 
# Semiconductor Memory Trends (more recent...)




From [Itoh01]

# Trends in Memory Cell Area

 


# Semiconductor Memory Trends

 

Technology feature size for different SRAM generations



# Memory Architecture: Decoders

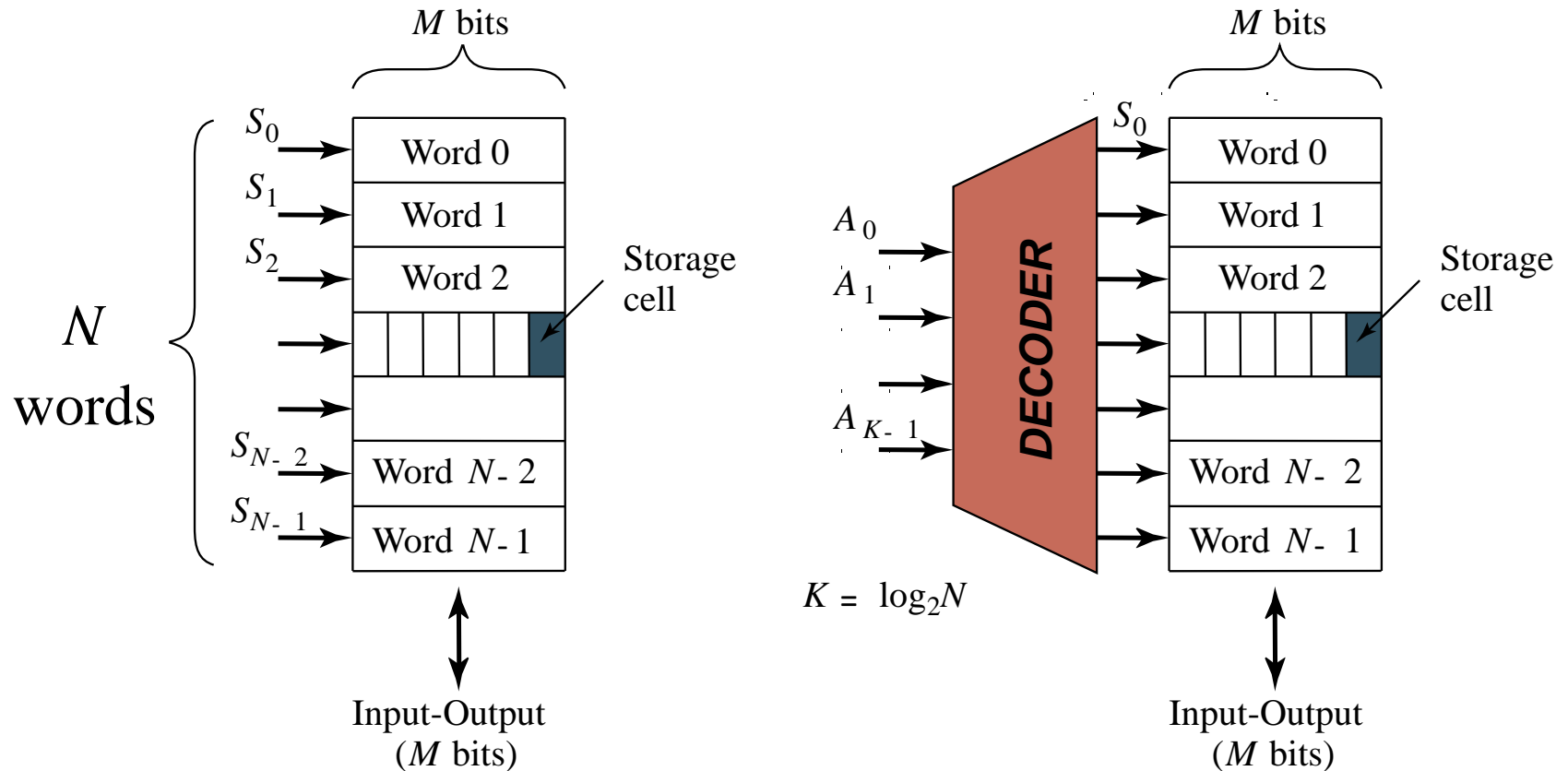


Intuitive architecture for  $N \times M$  memory  
Too many select signals:  
 $N$  words ==  $N$  select signals

Decoder reduces the number of select signals  
 $K = \log_2 N$
 
# Decoder Basic


- ❑ Recall that a decoder is a combinational circuit with **k inputs** and at most  **$2^k$  outputs**.
- ❑ Its characteristic property is that for every combination of input values only **ONE** output =1 at the same time.
- ❑ Used to route input data to specific output line.



*For example: for  $a=b=c=0$ , only  $S_0 = 1$*

# Array-Structured Memory Architecture

 **Problem:** consider ~1 million ( $N=2^{20}$ ) 8-bit ( $M=2^3$ ) words, ASPECT RATIO is very large!!! or HEIGHT  $\gg$  WIDTH, cannot be implemented and will result in very slow design.....



**Solution:** Make vertical and horizontal dimensions of the same order of magnitude

Store multiple words in one row

Use a column decoder to select the correct word

← Amplify swing to rail-to-rail amplitude  
For interfacing to the external world


← Selects appropriate word

OK for 64 Kbits to 256 Kbits beyond which speed degrades as length, C, and R of word/bit lines increase excessively

Peripheral circuitry is needed to recover the desired digital signal properties

# Hierarchical Memory Architecture


For Larger Memories....

 

## Advantages:

1. Shorter wires within blocks: faster access times
2. Block address activates only 1 block => power savings

# Block Diagram of 4 Mbit SRAM

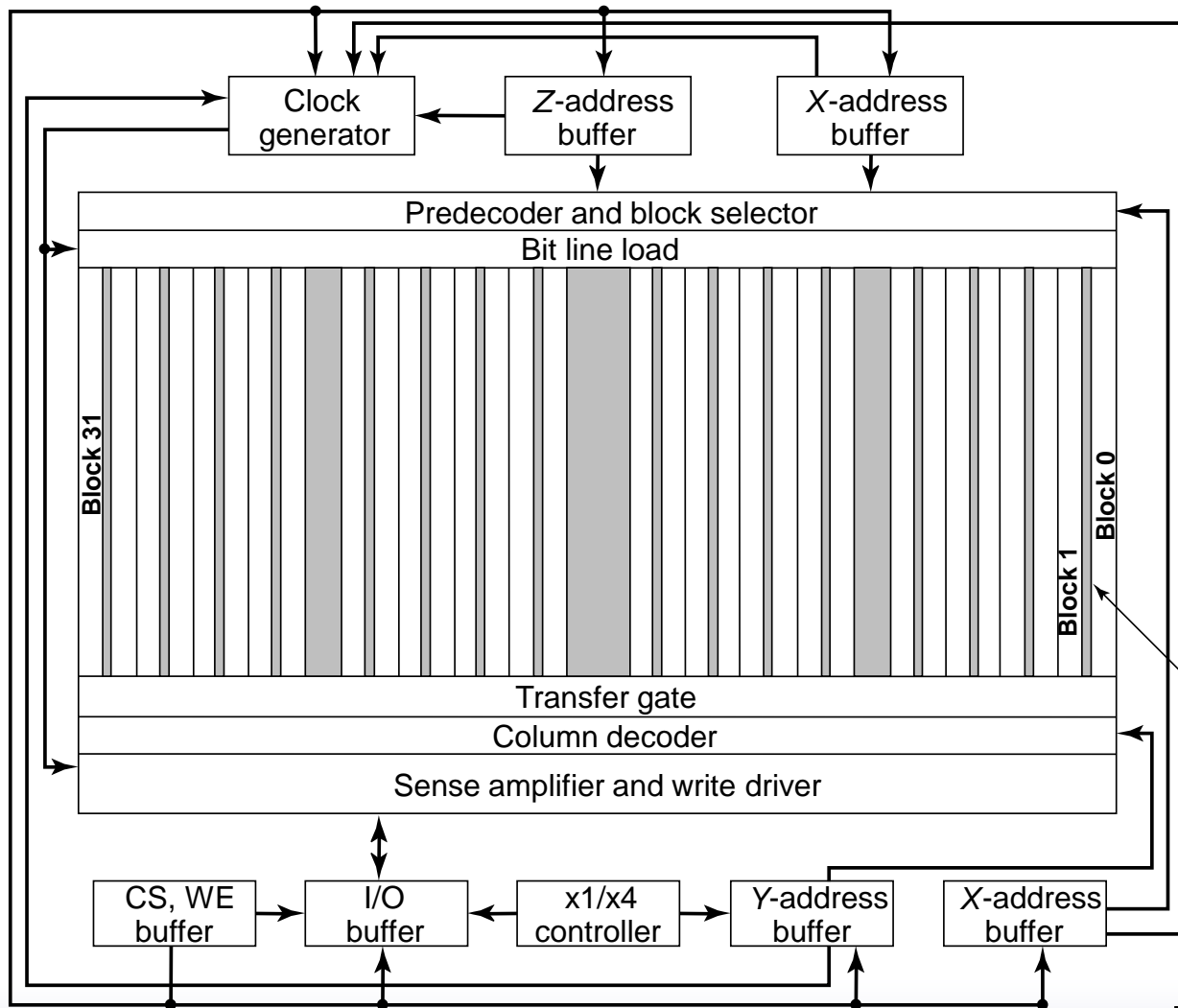

32 blocks, each containing 128 Kbits

Each block is structured as an array of 1024 rows and 128 columns

[Hirose90]

# *Read-Write Memories (RAM)*

## □ **STATIC (SRAM)**

**Data stored as long as supply is applied**

**Large (6 transistors/cell)**

**Fast**

**Differential**

## □ **DYNAMIC (DRAM)**

**Periodic refresh required**

**Small (1-3 transistors/cell)**

**Slower**

**Single Ended**

# 6-transistor CMOS SRAM Cell

*Should be minimum sized to achieve high memory density.....*

## READ Operation:

Assume 1 is stored at Q


Assume both BLs are held high before the read.

Read cycle started by asserting the WL, enables PTs M5 and M6

During a correct read operation values stored in Q and  $\bar{Q}$  are transferred to the bit lines leaving BL at its precharge value and by discharging BL through M1-M5

A "0" can be read in a similar manner (now BL gets discharged through M6 and M3)

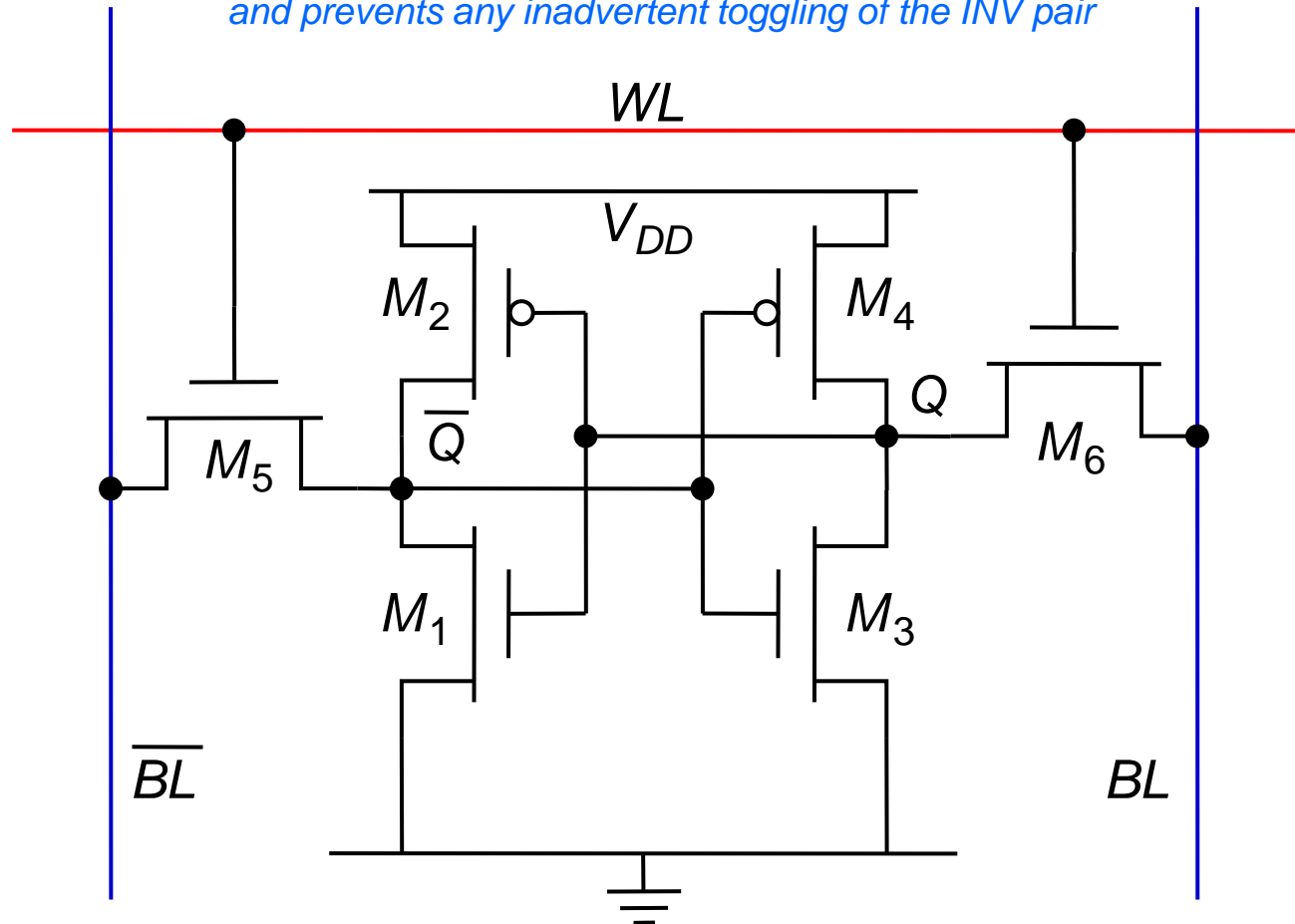*Major advantage of dual BL: Q is clamped to V<sub>DD</sub> by BL and prevents any inadvertent toggling of the INV pair*




*SRAM cell should be as small as possible.....but reliable operation requires careful sizing...*

# CMOS SRAM Analysis (Read "1" operation)

Transistor sizing is needed to avoid writing 1 accidentally, i.e., voltage at  $\bar{Q}$  becomes  $> V_M$  of Inv M3-M4

M1 must be stronger than M5

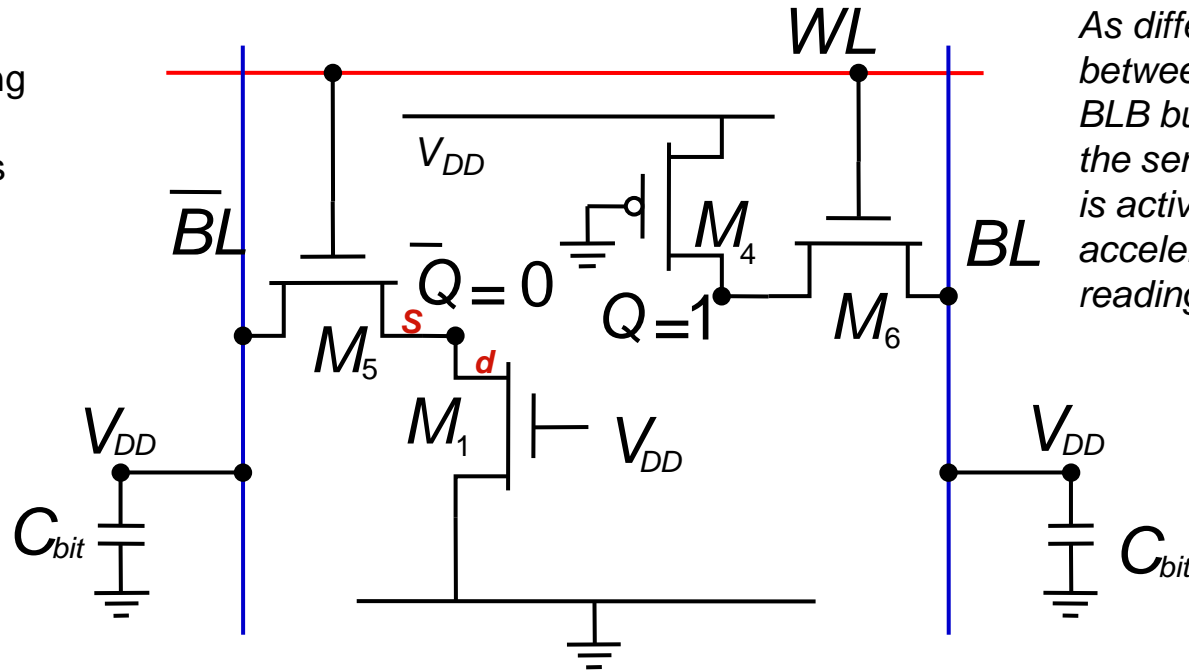$\bar{Q}$  must stay low enough so that there is no substantial current through M3-M4 INV



As difference between BL and BLB builds up, the sense amp. is activated to accelerate the reading process

$$k_{n,M5} \left( (V_{DD} - \Delta V - V_{Tn}) V_{DSATn} - \frac{V_{DSATn}^2}{2} \right) = k_{n,M1} \left( (V_{DD} - V_{Tn}) \Delta V - \frac{\Delta V^2}{2} \right)$$

(M5 in saturation)  (M1 in linear)


$$\Delta V = \frac{V_{DSATn} + CR(V_{DD} - V_{Tn}) - \sqrt{V_{DSATn}^2(1 + CR) + CR^2(V_{DD} - V_{Tn})^2}}{CR}$$

Value of the ripple voltage

CR = cell ratio = M1/M5



# CMOS SRAM Analysis (Read)

 

$$CR = \frac{W_1/L_1}{W_5/L_5}$$

**Choose  
M5 to be  
minimum  
size and  
M1 > M5**

Node voltage must stay below the  $V_{th}$  of M3: CR must be  $>1.2$

# CMOS SRAM Analysis (Write)



Assume that  $Q=1$

To write a 0 in the cell: set  $\overline{BL}=1$  and  $BL=0$

Similar to applying a reset pulse to an SR latch. FF will change state if sized properly

$\overline{Q}$  cannot be pulled high due to the sizing of M5 and M1 already done for reading

New value must be written through M6

 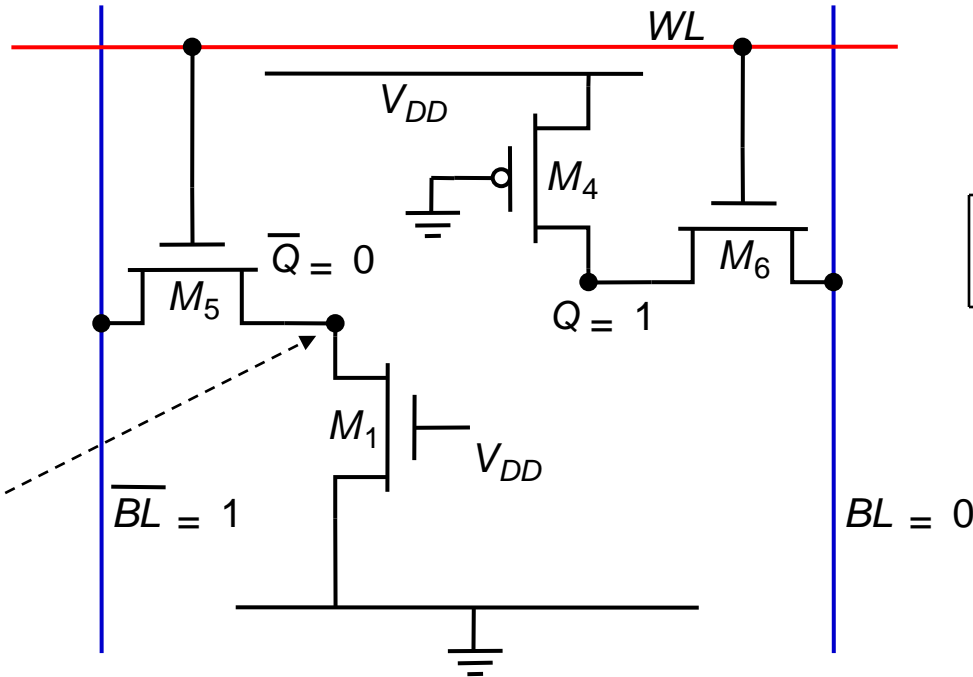

Reliable writing of the cell is ensured if we can pull node Q low enough—below the  $V_{th}$  of M1

$$k_{n, M6} \left( (V_{DD} - V_{Tn}) V_Q - \frac{V_Q^2}{2} \right) = k_{p, M4} \left( (V_{DD} - |V_{Tp}|) V_{DSATp} - \frac{V_{DSATp}^2}{2} \right)$$


(M6 in linear) (M4 in saturation)

$$V_Q = V_{DD} - V_{Tn} - \sqrt{(V_{DD} - V_{Tn})^2 - 2 \frac{\mu_p}{\mu_n} PR \left( (V_{DD} - |V_{Tp}|) V_{DSATp} - \frac{V_{DSATp}^2}{2} \right)}$$

**PR = pull-up ratio of cell = M4/M6**
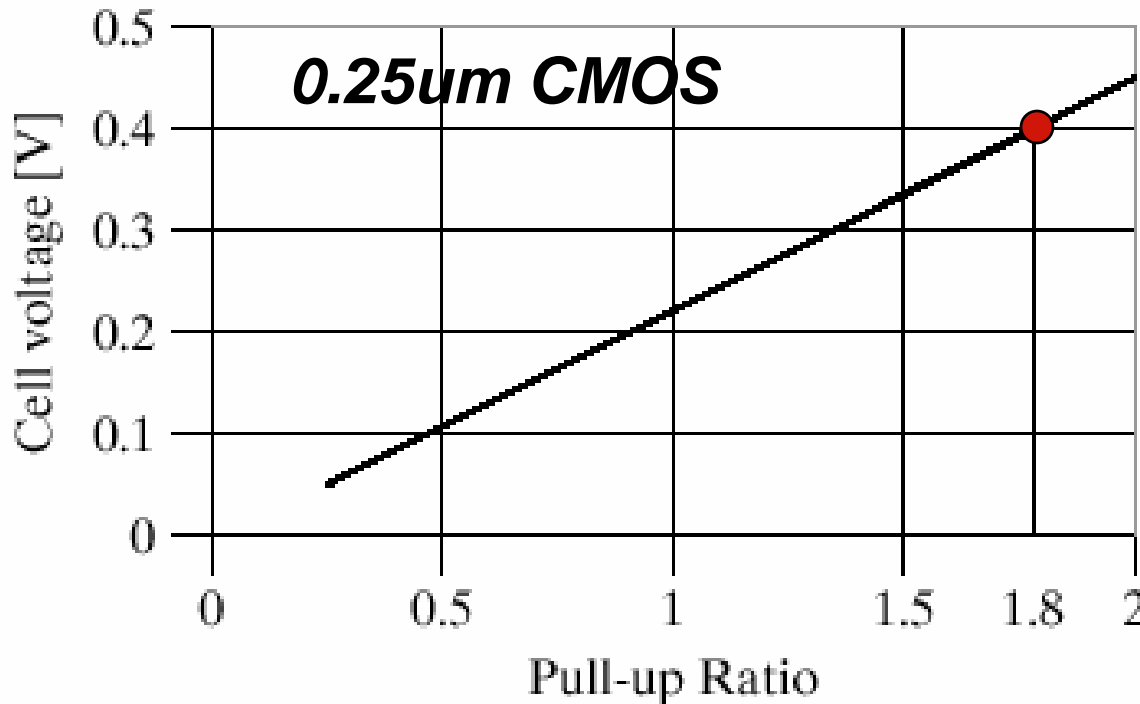
# CMOS SRAM Analysis (Write)

Dependence of  $V_Q$  on Pull-up Ratio.....lower PR gives lower  $V_Q$



$$PR = \frac{W_4/L_4}{W_6/L_6}$$


Should be low to keep  $V_Q$  low

PR between the PMOS (M4) pull-up and the NMOS (M6) Pass Transistor must be  $< 1.8$  to keep  $V_{tn} < 0.4$  V


# Performance of SRAM

- ❑ **Read operation** is more critical. It requires discharging of the **large bit line capacitance** through the stack of 2 transistors (M1-M5)
- ❑ **Write time** is dominated by the propagation delay of the **cross-coupled inverter pair**, since the drivers that set BL and  $\overline{BL}$  can be large
- ❑ **Sense amplifiers** used to **accelerate Read time**....as the difference between BL and  $\overline{BL}$  builds up, sense amplifier is activated, and it discharges one of the bit lines

# Sense Amp Operation

 


# 6T-SRAM — Layout

 

6T SRAM  
Takes  
significant  
area...the two  
PMOS need  
n-wells
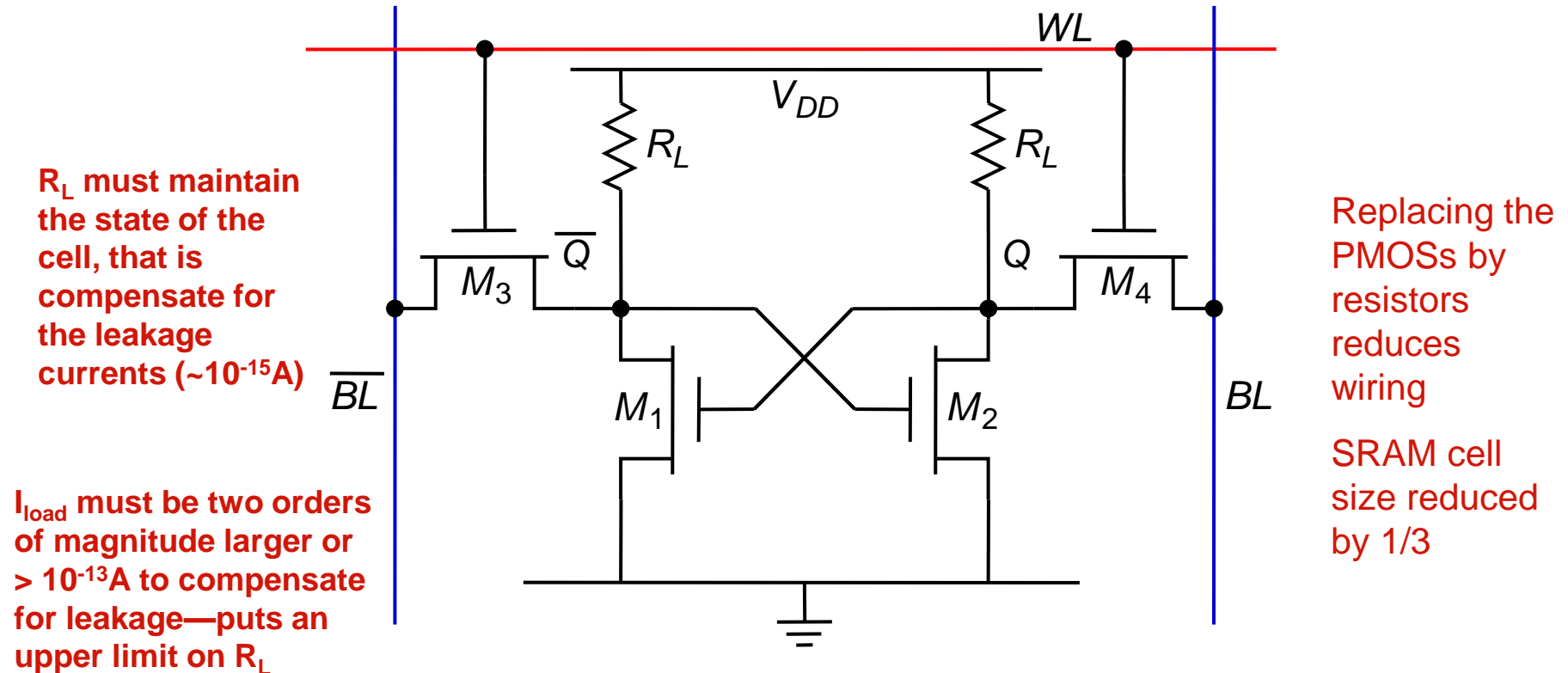
# Resistive-load (4T) SRAM Cell

Reduce area using resistive load inverters...simplifies writing



Static power dissipation -- Want  $R_L$  large (use undoped poly)  
Bit lines precharged to  $V_{DD}$  to address  $t_p$  problem

# SRAM Characteristics

**Table 12-2** Comparison of CMOS SRAM cells used in 1-Mbit memory (from [Takada91])

	Complementary CMOS	Resistive Load	TFT Cell
Number of transistors	6	4	4 (+2 TFT)
Cell size	58.2 $\mu\text{m}^2$ (0.7- $\mu\text{m}$ rule)	40.8 $\mu\text{m}^2$ (0.7- $\mu\text{m}$ rule)	41.1 $\mu\text{m}^2$ (0.8- $\mu\text{m}$ rule)
Standby current (per cell)	$10^{-15}$ A	$10^{-12}$ A	$10^{-13}$ A



Instead of PMOS devices, use parasitic devices on top of cell structure using thin-film transistors (TFTs)

Use high  $V_t$


**However, embedded SRAM cells---used in microprocessor caches, employ 6T cells.**


 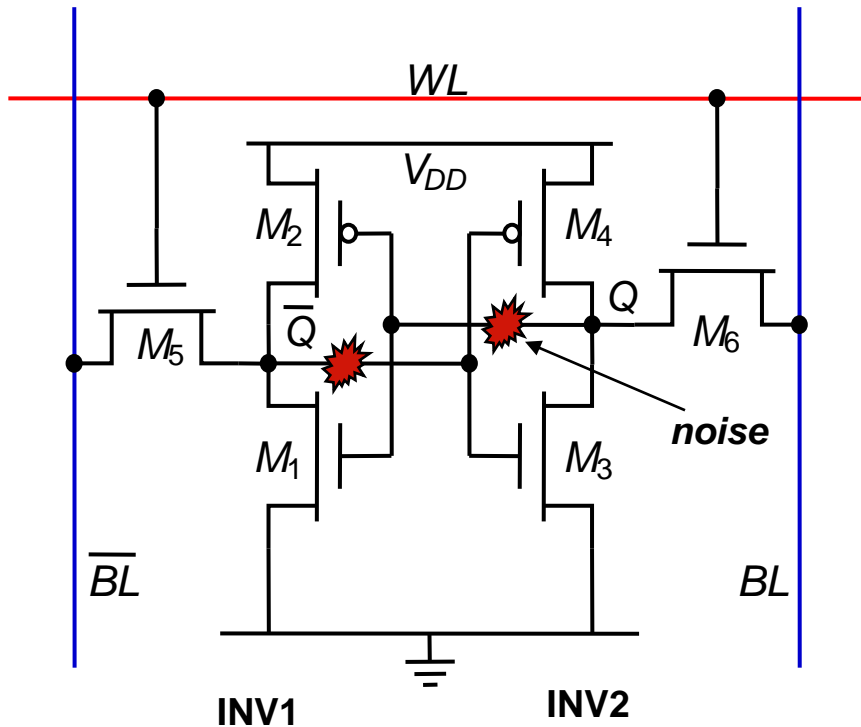
# 6-T CMOS SRAM Cell: Static Noise Margin



Butterfly Curve

 



The SNM (hold margin) can be estimated graphically by the **length of the side of the square** fitted between the VTCs and having the longest diagonal.

As noise increases at the two nodes above, the reverse VTC for INV1 moves upward, while the VTC for INV2 moves to the left (**worst case**)

Once they both move by the SNM value, the curves meet at only two points.....at A' and B'..... and any further noise flips the data.
 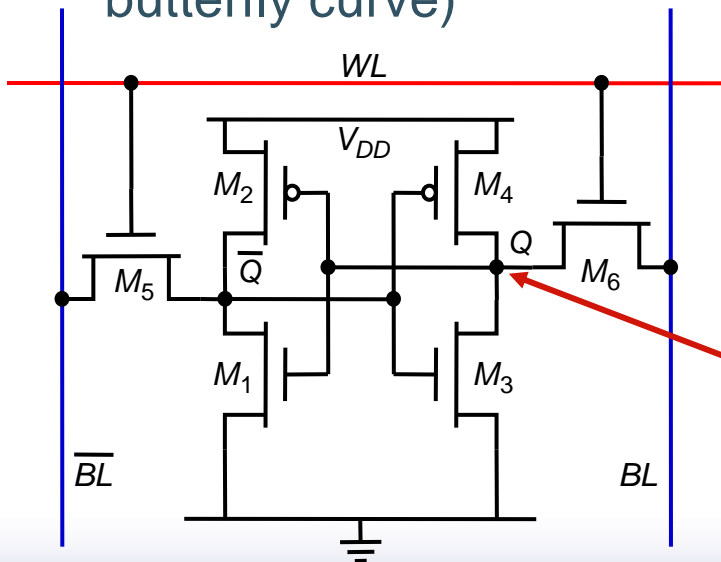
# Static Noise Margin (SNM)



- ❑ **Hold Margin:** How strongly the node storing '1' and the node storing '0' are coupled to  $V_{DD}$  and  $V_{SS}$  respectively.
- ❑ **Read Margin:** The difference between  $V_{TRIP}$  and  $V_{READ}$  (max. voltage at Q)
- ❑ **Write Margin:** The maximum voltage on a bit-line that allows writing to the cell, while the other bit-line is at  $V_{DD}$ . (not determined by the butterfly curve)


 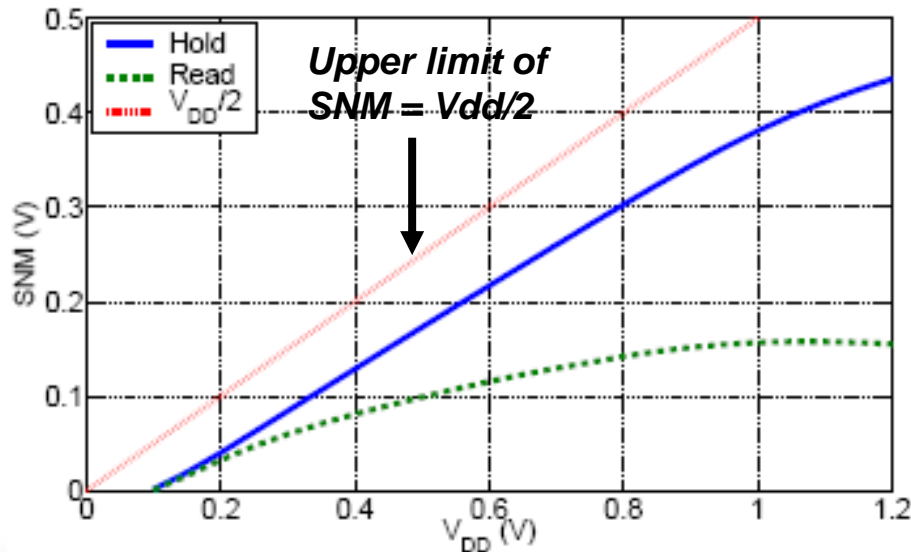
# SNM Dependencies

- Dependence on  $V_{DD}$  : SNM for a bitcell with ideal VTCs is still limited to  $V_{DD}/2$
- Dependence on sizing

*Here, Cell ratio = size of PD device over size of access device*





# 3-Transistor DRAM Cell (Early Days)

Periodic refresh operation consists of **read** followed by **write**

1 Kbit memory: Intel

Still used in some ASICs

 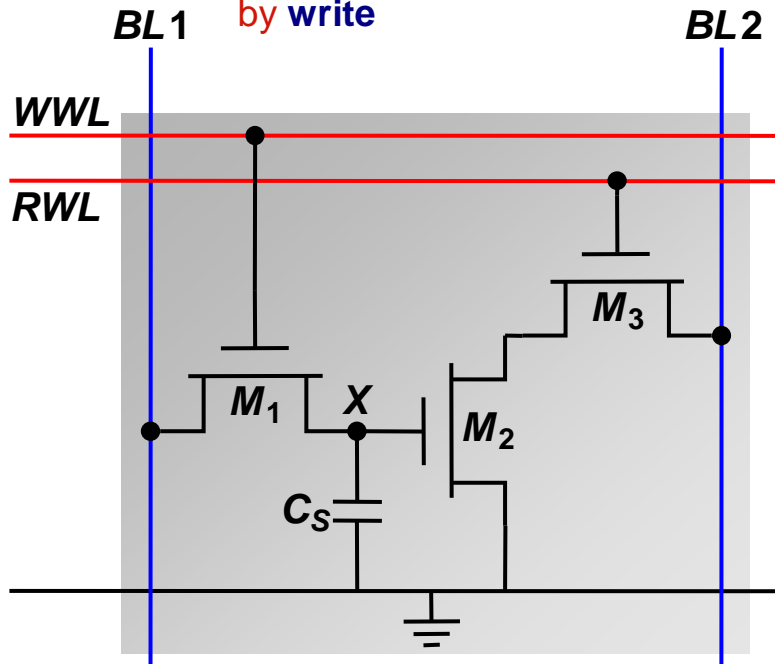Dynamic: since it involves charge storage on a capacitor



Cell is **written** by placing value on BL1 and asserting Write Word Line (WWL=1)

Data retained as charge stored on Cs once WWL=0



For **reading** the cell, RWL=1

M2 can be on or off depending on stored value

BL2 is either clamped to Vdd or is precharged to either Vdd or Vdd-Vt

M2-M3 pulls BL2 low when X=1, otherwise BL2 remains high (cell is inverting: senses the inverse value of the stored signal )

# 3T-DRAM — Layout

  

Unlike SRAM, no constraint on device sizes

Read operation is non-destructive



No special process steps needed

Value at node X =  $V_{WWL} - V_{tn}$

This reduces the current through M2 during read operation and increases read access time: can use a higher value of  $V_{WWL}$  to avoid this
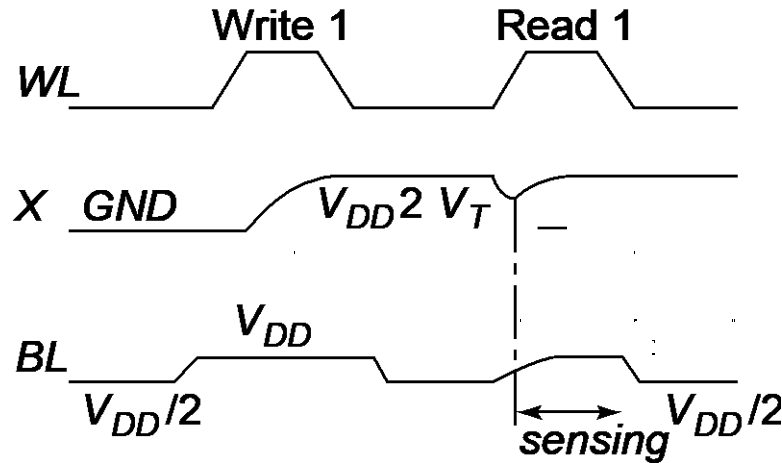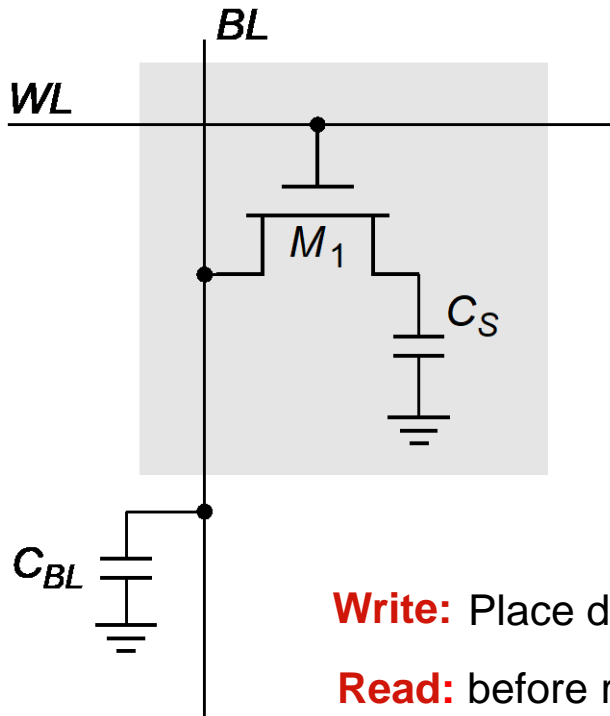
# 1-Transistor DRAM Cell

Most pervasive in commercial memory design



**Write:** Place data on BL and assert WL, depending on data value, Cs is 1 or 0

**Read:** before read, precharge BL to  $V_{PRE}$

After  $WL=1$ , charge redistribution takes place between bit line and storage capacitance resulting in a voltage change on BL

$$\Delta V = V_{BL} - V_{PRE} = (V_{BIT} - V_{PRE}) \frac{C_S}{C_S + C_{BL}}$$

← Charge transfer ratio (1-10%)


$V_{BIT}$  is initial voltage on  $C_S$ .  $V_{BL}$  is final voltage on BL after charge redistribution. Voltage swing is small since  $C_S \ll C_{BL}$ ; typically around 250 mV.

**Note:** From charge conservation,  $C_S V_{BIT} + C_{BL} V_{PRE} = (C_S + C_{BL}) V_{final}$ , and  $V_{final} (= V_{BL})$


# DRAM Cell Observations

- ❑ 1T DRAM requires a **sense amplifier** for each bit line, due to charge redistribution read-out.
- ❑ DRAM memory cells are **single ended** in contrast to SRAM cells.
- ❑ The **read-out** of the 1T DRAM cell is **destructive**; read and refresh operations are necessary for correct operation.
- ❑ Unlike 3T cell, **1T cell** requires presence of an **extra capacitance** that must be explicitly included in the design.
- ❑ When **writing a “1”** into a DRAM cell, a **threshold voltage is lost**. This charge loss can be circumvented by bootstrapping the word lines to a higher value than  $V_{DD}$

# 1-T DRAM Cell

 

**Cross-section**

 


**Layout**

**Uses Polysilicon-Diffusion Capacitance**


**Expensive in Area**




 
# *SEM of poly-diffusion capacitor 1T-DRAM*



# Advanced 1T DRAM Cells

 


**Trench Cell**

  


**Stacked-capacitor Cell**

# *Non-Volatile Memory*
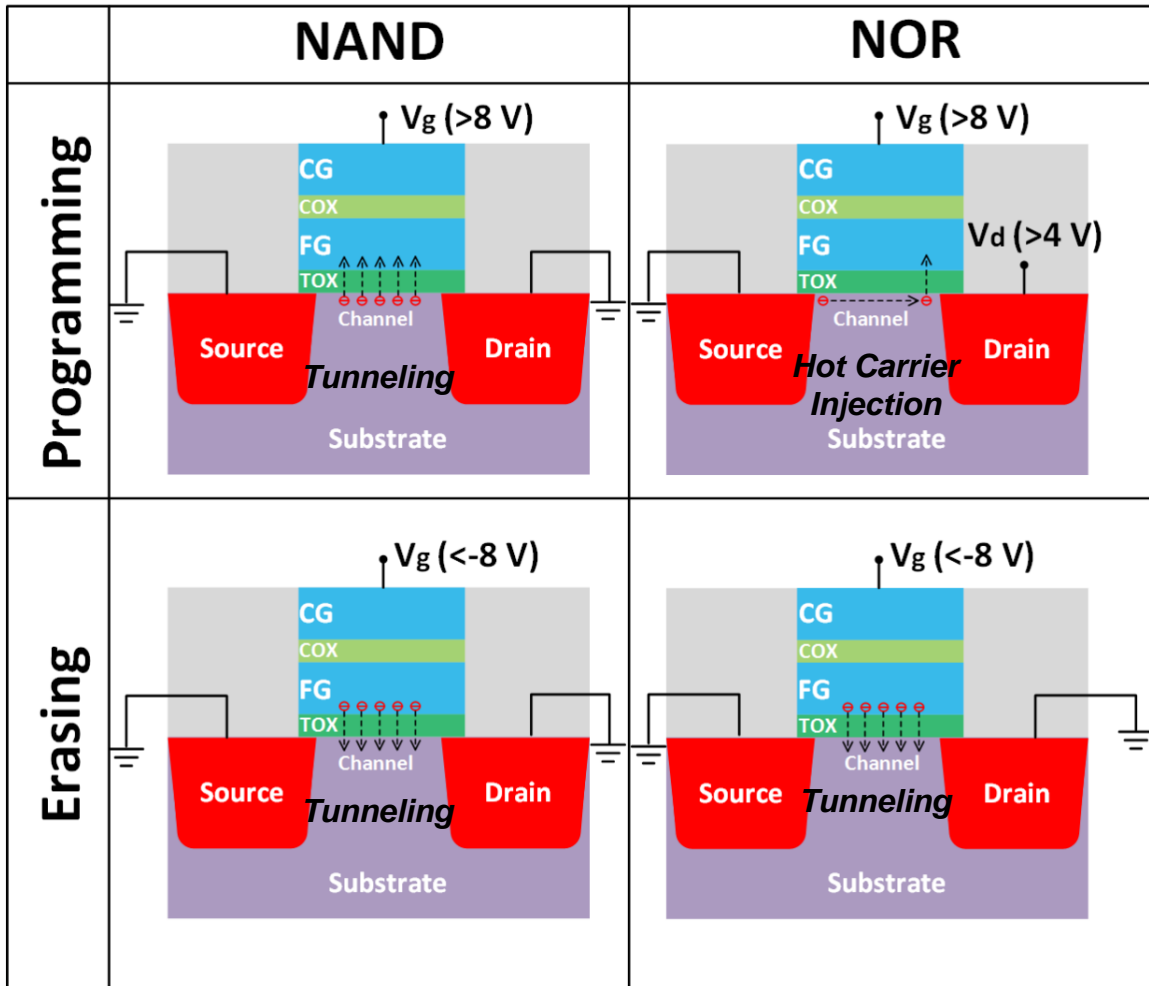
# Flash Memory (with Floating Gate (FG) Transistor)





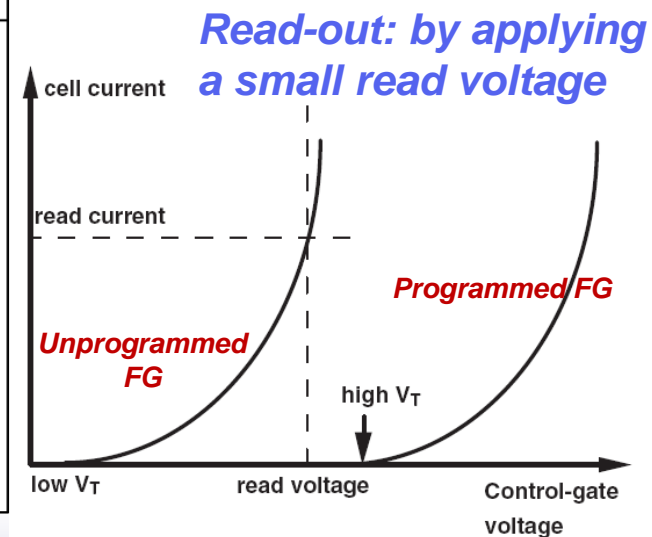*N-type device*  
*CG: control gate*  
*COX: control oxide*  
*FG: floating gate*  
*TOX: tunnel oxide*



# NAND vs. NOR circuit



## NOR-EEPROM

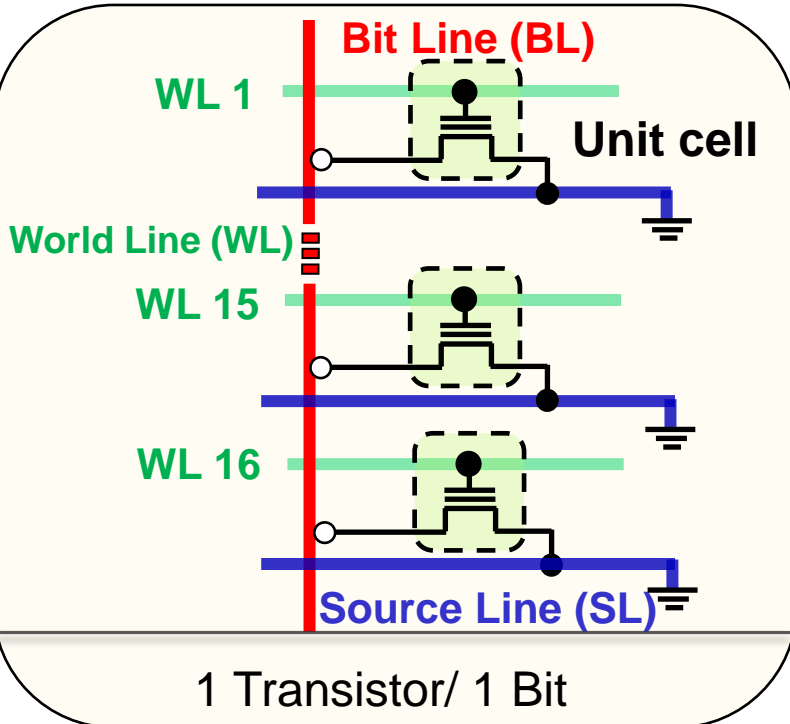 

*Devices can be  
Randomly accessed*

NOR: It's available for random access

## NAND-EEPROM

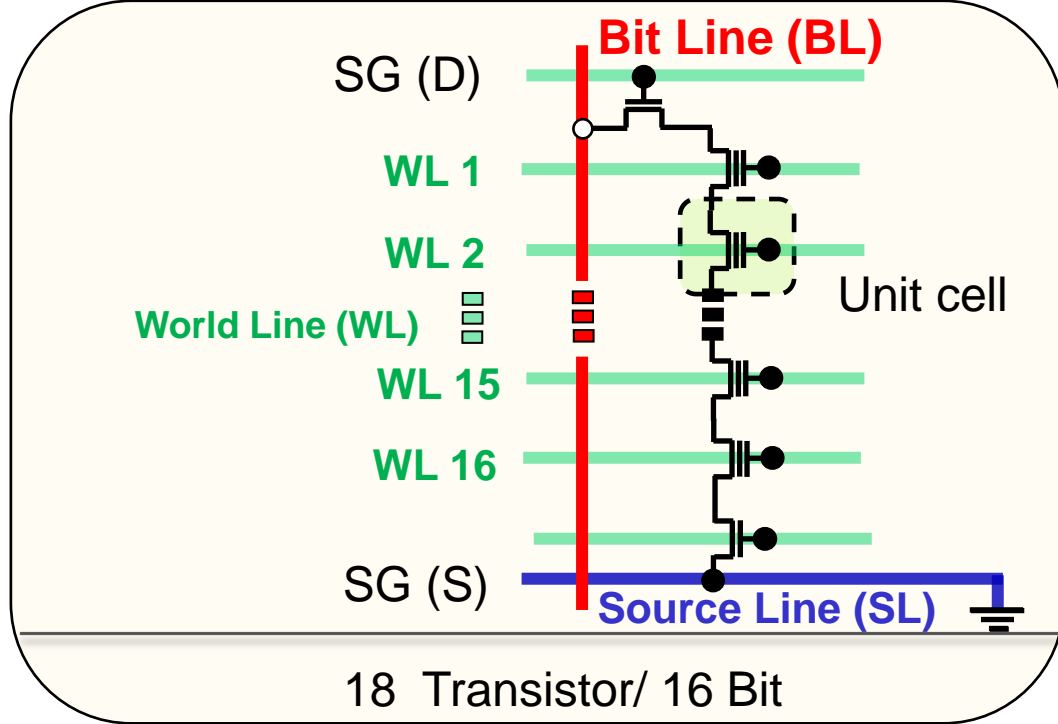 

*Both SG devices needed for read out*

NAND: It's allowed to access one bit only per readout operation



# NAND vs. NOR

## Merits of NAND

★ Tunneling rate > Hot carrier inj.

- ① High speed programming (★)
- ② High speed erasing
- ③ High capacity
- ④ Low cost per bit

## Demerits of NAND

- ① Slow random access
- ② Byte programming cannot be performed  
↑ (1 Byte= 8 bit)  
(Need of bit by bit programming/erasing process / pre cell)
- ③ Slow read operations  
(Serial access => sequential data readout)

- Applications -
- Suitable for Data Memory (Handy terminal, Voice recorder, DSC, Fax modem, etc)

## Merits of NOR

- ① High speed random access
- ② Byte programming

(Individual bit cell for programming/erasing process)


## Demerits of NOR

- ① Slow programming
- ② Slow speed erasing
- ③ Low capacity
- ④ High cost per bit

(NOR must be erased in large "chunks". Those chunks can often be subdivided and erased in smaller subunits resulting in a performance penalty)

- Applications -
- Suitable for replacement of EPROM
  - Suitable for control memory (BIOS, Cellular, HDD, etc)

# Scaling issues

 

- thin COX/TOX  $\rightarrow$  leakage current  $\rightarrow$  short retention time
- small cell-to-cell distance  $\rightarrow$   $V_{th}$  perturbation by adjacent cells

## *Promising solution: 2D materials....*

**Can 2D-Nanocrystals Extend the Lifetime of Floating-Gate Transistor Based Nonvolatile Memory?**

*Wei Cao, Jiahao Kang, Simone Bertolazzi, Andras Kis and Kaustav Banerjee*

*IEEE Transactions on Electron Devices, vol. 61, No. 10, pp.3456-3464, 2014.*

# 3-D ICs : Multiple Active Si Layers

K. Banerjee et al., Proceedings of the IEEE, 2001

- **Advantages**

- Reduce Interconnect Length by **Vertically Stacking Multiple Si Layers**
- Reduce **Chip Area**, **power dissipation** and **improve Chip Performance**
- **Heterogeneous integration** possible, e.g., memory, digital, analog, optical, etc. using different substrates (Si, III-V etc)

