
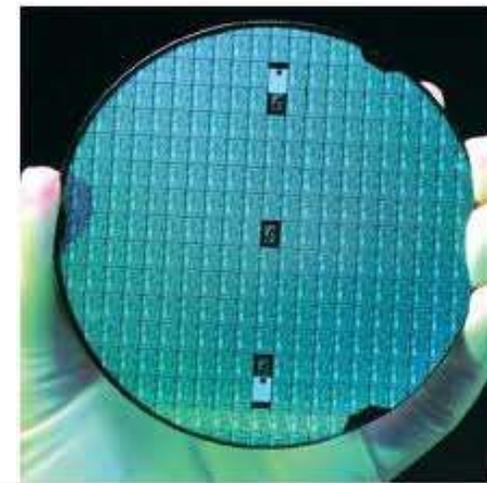
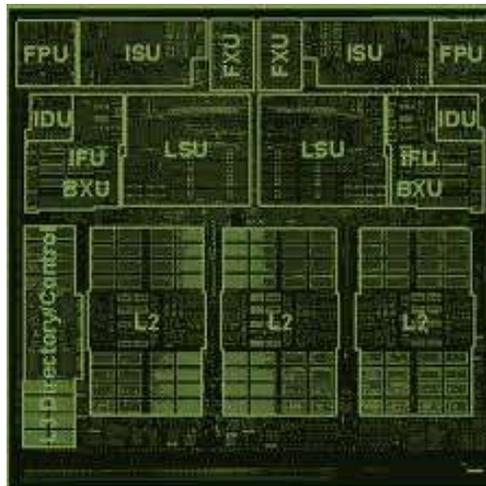


Structure of silicon crystal

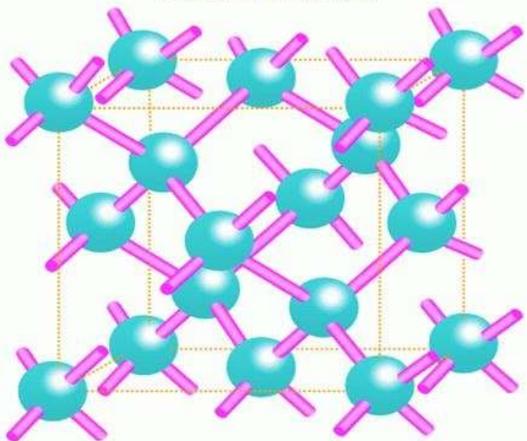


# *ECE 122A*

# *VLSI Principles*

## *Lecture 13*

Prof. Kaustav Banerjee  
Electrical and Computer Engineering  
University of California, Santa Barbara  
*E-mail: [kaustav@ece.ucsb.edu](mailto:kaustav@ece.ucsb.edu)*


# A Generic Digital Processor

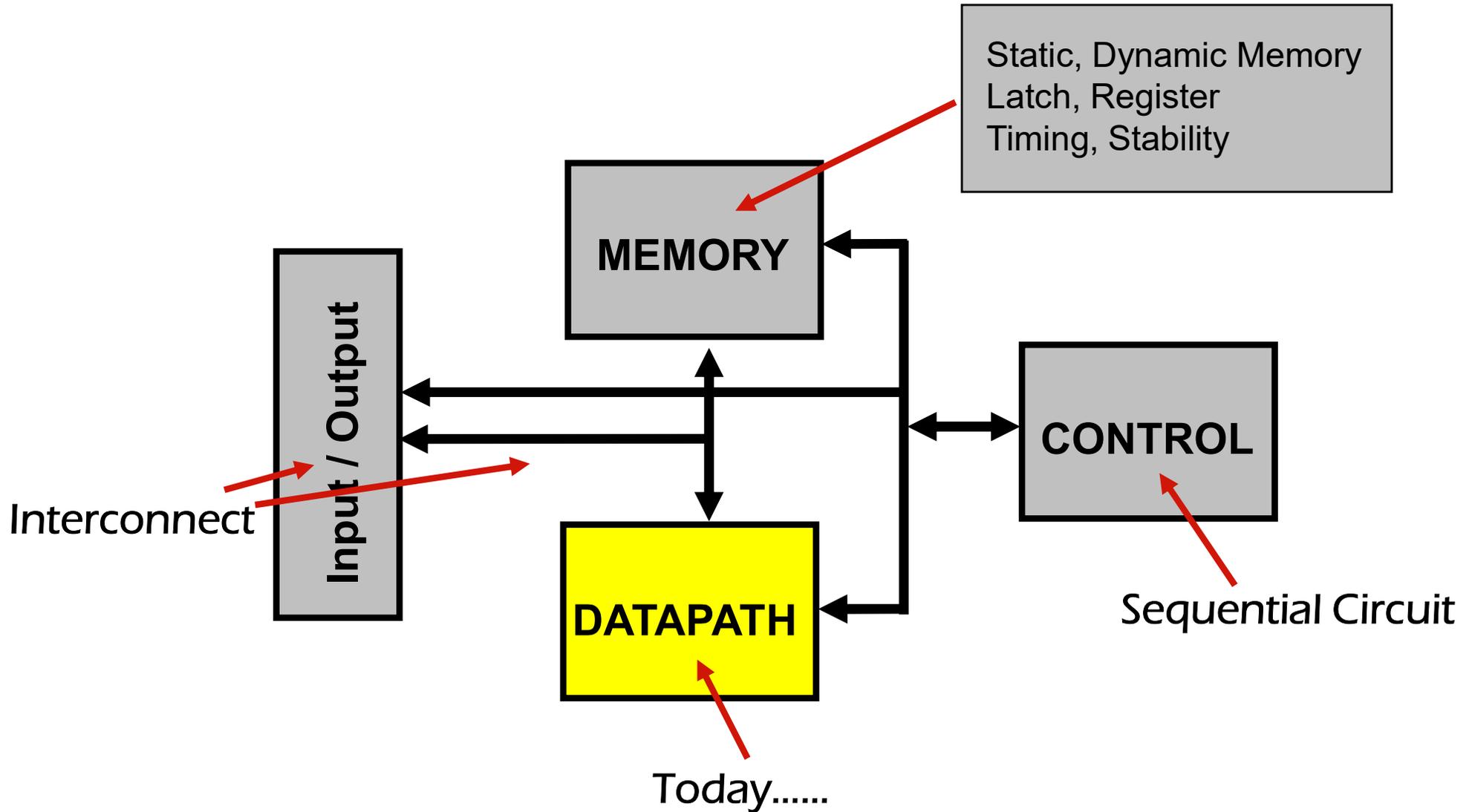

# ***DATAPATH***


- The core of a digital Processor
  - where all computations are performed
- Datapath consists
  - **Logic Blocks**
    - Combinational Logic Functions (AND, OR, XOR....)
  - **Arithmetic Blocks**
    - Addition
    - Multiplication
    - Comparison
    - Shift

# An Intel Microprocessor

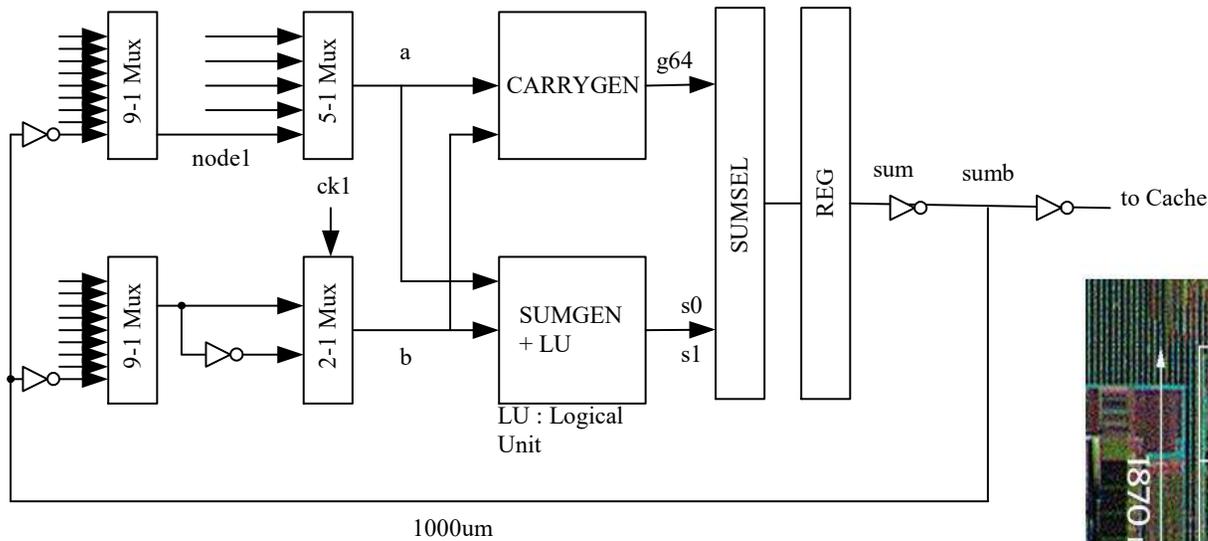

 
## Intel Itanium® Integer Datapath

Itanium has 6 integer execution units like this



Fetzer, Orton, ISSCC'02

# Bit-Sliced Design

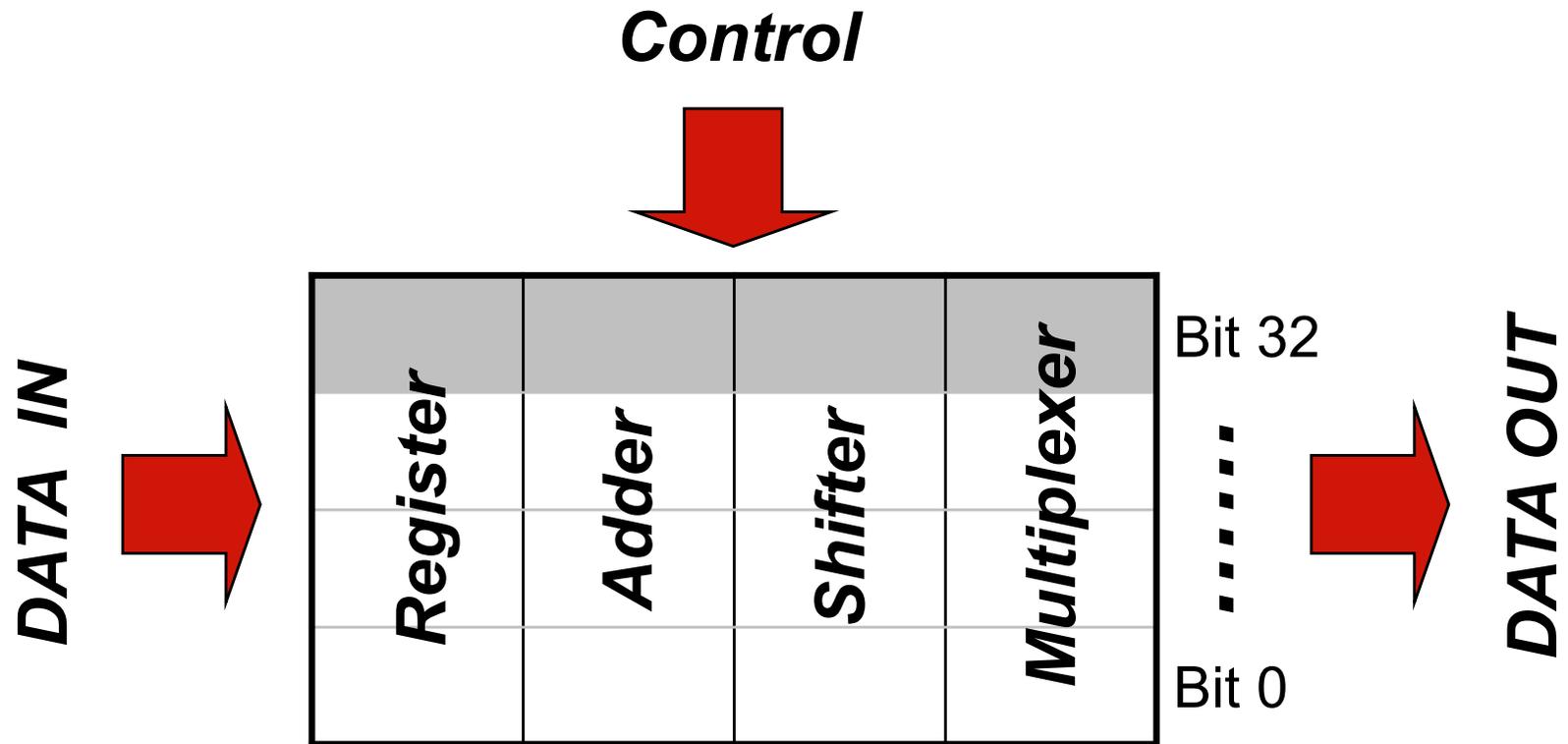

*Design a single bit datapath and repeat for all bits*

# Adders

## *Design an Adder*

- Fundamental Arithmetic Building Block
- Performance
  - Logic Level Optimization
    - Optimize Boolean Functions
    - Carry Lookahead
  - Circuit Level Optimization
    - Transistor Sizing
- Power Consumption

# Fundamental Logic of Adders

## □ Truth table of a full adder

- Sum:  $S = A \oplus B \oplus C_{in}$

- Carry out:

$$C_{out} = (A \cdot B) + (C_{in} \cdot (A \oplus B))$$

A	B	C	$C_{out}$	S
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

## □ PGK (independent of $C_{in}$ )

- Generate:  $G = A \cdot B$

- Propagate:  $P = A \oplus B$

- Kill:  $K = \sim A \cdot \sim B$

$$S = P \oplus C_{in}, C_{out} = G + C_{in} \cdot P$$

# Adder Overview

□ Different adders covered in the slides:

➤ **Single-bit adder**

❖ *Static*

- *Static CMOS*
- *Mirror design*
- *Transmission gate*

❖ *Dynamic*

- *Manchester chain*

➤ **Multi-bit adder**

❖ *Ripple-carry adder*





❖ *Carry bypass adder*

- *Linear carry select*
- *Square-root carry select*



❖ *Carry look-ahead*

# Half-Adder Implementations

Half-Adder

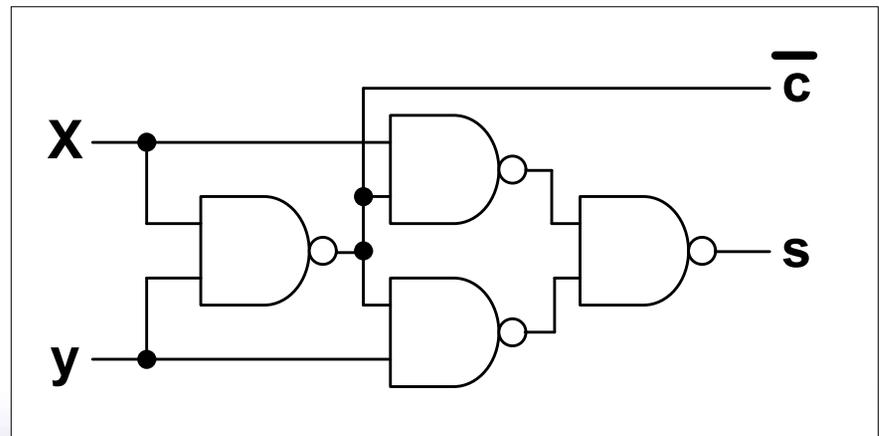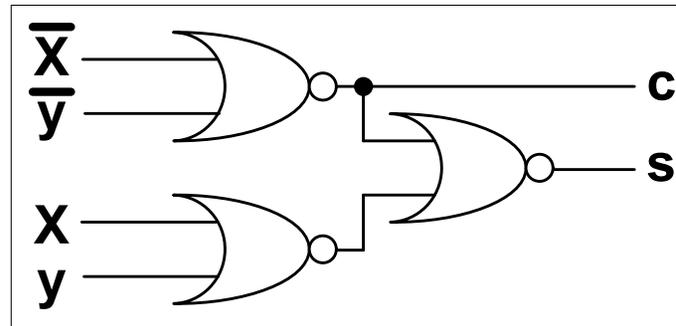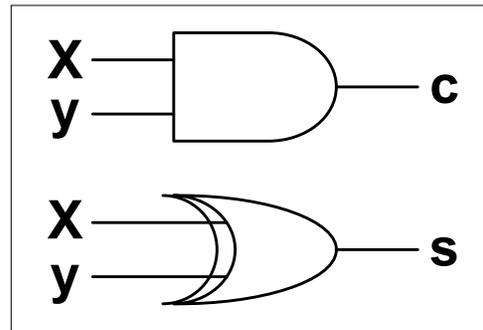 


# Full-Adder

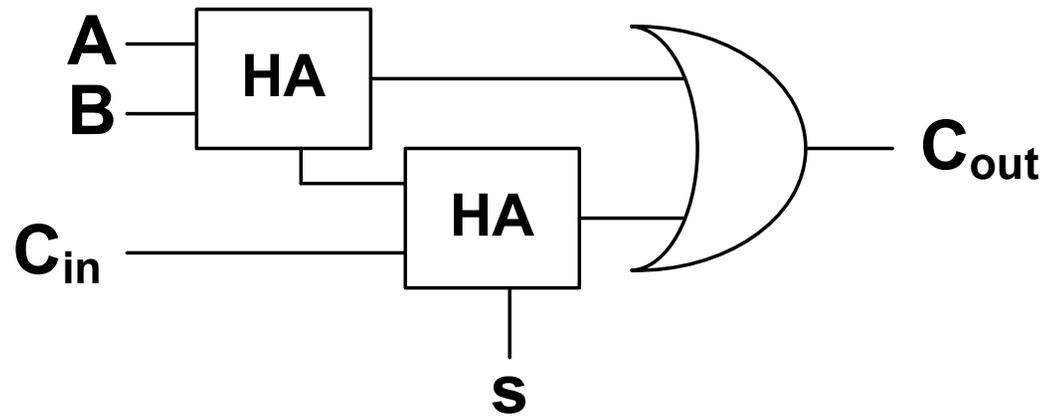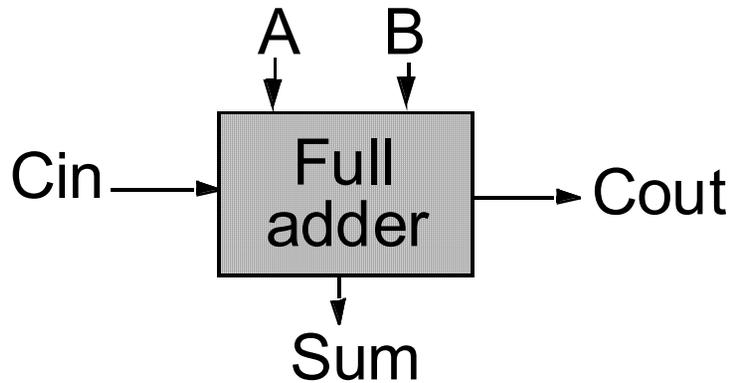

$$S = A \oplus B \oplus C_{in} = \overline{A}\overline{B}C_{in} + \overline{A}B\overline{C}_{in} + A\overline{B}\overline{C}_{in} + ABC_{in}$$


$$C_{out} = AB + BC_{in} + AC_{in}$$

# Complimentary Static CMOS Full Adder

 

28 Transistors

# The Ripple-Carry Adder

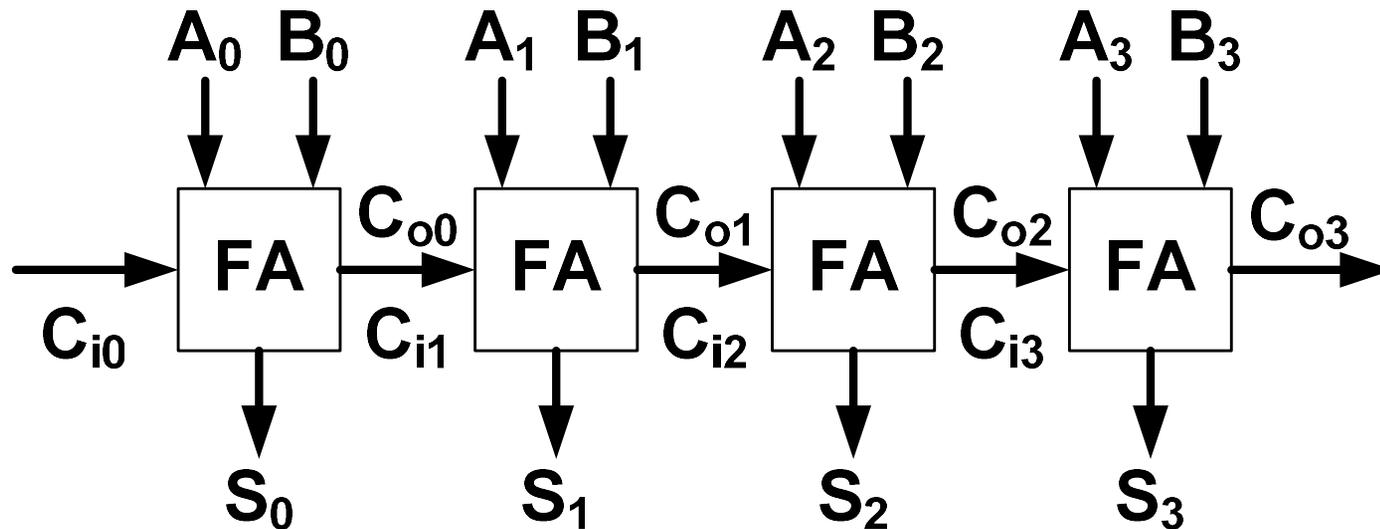


Worst case delay: linear with the number of bits  $t_d = O(N)$

$$t_{adder} \sim (N-1)t_{carry} + t_{sum}$$

- ❑ Propagation Delay is proportional to  $N$
- ❑  $t_{carry}$  dominates the propagation delay

# Inverting Property

 


$$\bar{S}(A, B, C_i) = S(\bar{A}, \bar{B}, \bar{C}_i)$$

$$\bar{C}_0(A, B, C_i) = C_0(\bar{A}, \bar{B}, \bar{C}_i)$$

**Inverting all inputs to FA results in inverted values for all outputs**
 
# Minimize Critical Path by Reducing Inverting Stages




**Exploit Inversion Property**

# Mirror Adder (1)

A	B	$C_i$	S	$C_o$	status
0	0	0	0	0	D
0	0	1	1	0	D
0	1	0	1	0	P
0	1	1	0	1	P
1	0	0	1	0	P
1	0	1	0	1	P
1	1	0	0	1	G
1	1	1	1	1	G

Truth Table for Full Adder

 


- ❑ Carry-inverting gate is eliminated
- ❑ PDN/PUN networks are not dual

# Mirror Adder (2)



A	B	$C_i$	S	$C_o$	status
0	0	0	0	0	D
0	0	1	1	0	D
0	1	0	1	0	P
0	1	1	0	1	P
1	0	0	1	0	P
1	0	1	0	1	P
1	1	0	0	1	G
1	1	1	1	1	G

Truth Table for Full Adder

 

# Mirror Adder Implementation


Stick Diagram

 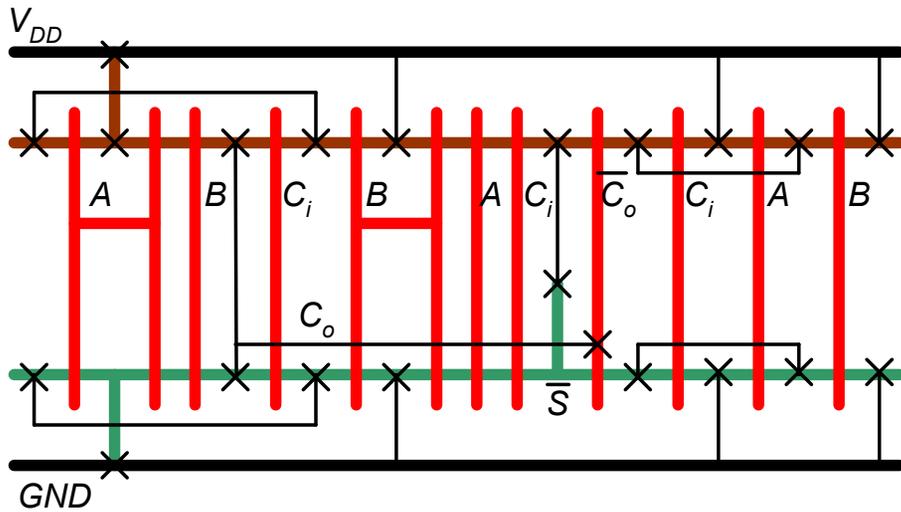

# Mirror Adder Summary

- ❑ **24** Transistors
- ❑ The NMOS and PMOS chains are completely **symmetrical**
- ❑ A maximum of **2 series transistors** in carry-generation circuitry
- ❑ The transistors connected to  $C_i$  should be closest to the output
- ❑ Carry-Stage transistors have to be optimized for speed
- ❑ Sum-Stage transistors can be optimized for area
- ❑ The most critical issue is to minimize the capacitance at  $C_o$
- ❑  $C_o$  is composed of **4 diffusion capacitances**, **2 internal gate capacitances**, and **6 gate capacitances** in the connecting adder cell


# Transmission Gate Full Adder

 

***This implementation has similar sum and carry output delay***


# Carry-Bypass Adder

## Carry-Skip Adder

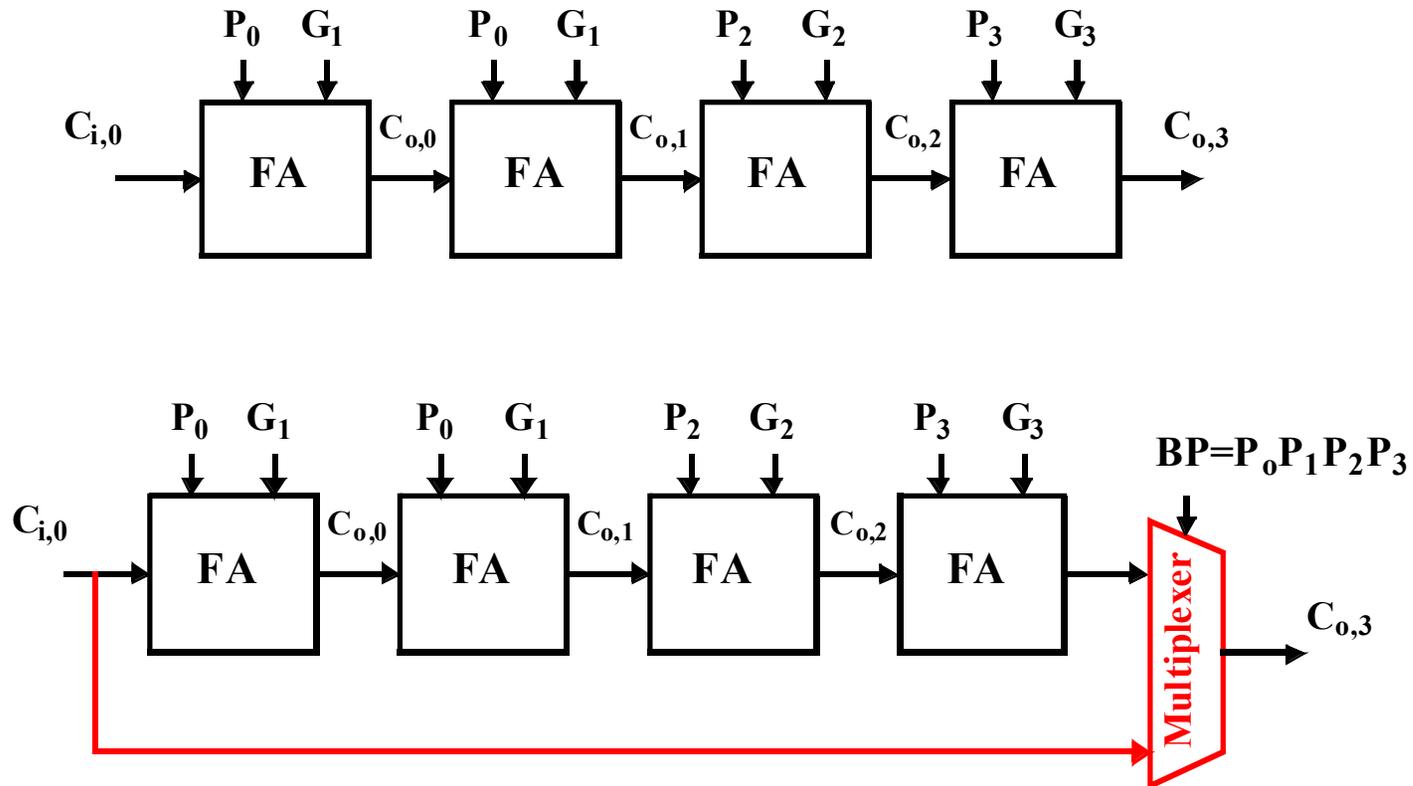

Idea: If ( $P_0$  and  $P_1$  and  $P_2$  and  $P_3 = 1$ ) then  $C_{o,3} = C_0$ , else “kill” or “generate”.

# 16-bit Carry-Bypass Adder

 


**$N=16$     $M=4$**

$$t_{adder} = t_{setup} + Mt_{carry} + (N/M-1)t_{bypass} + (M-1)t_{carry} + t_{sum}$$

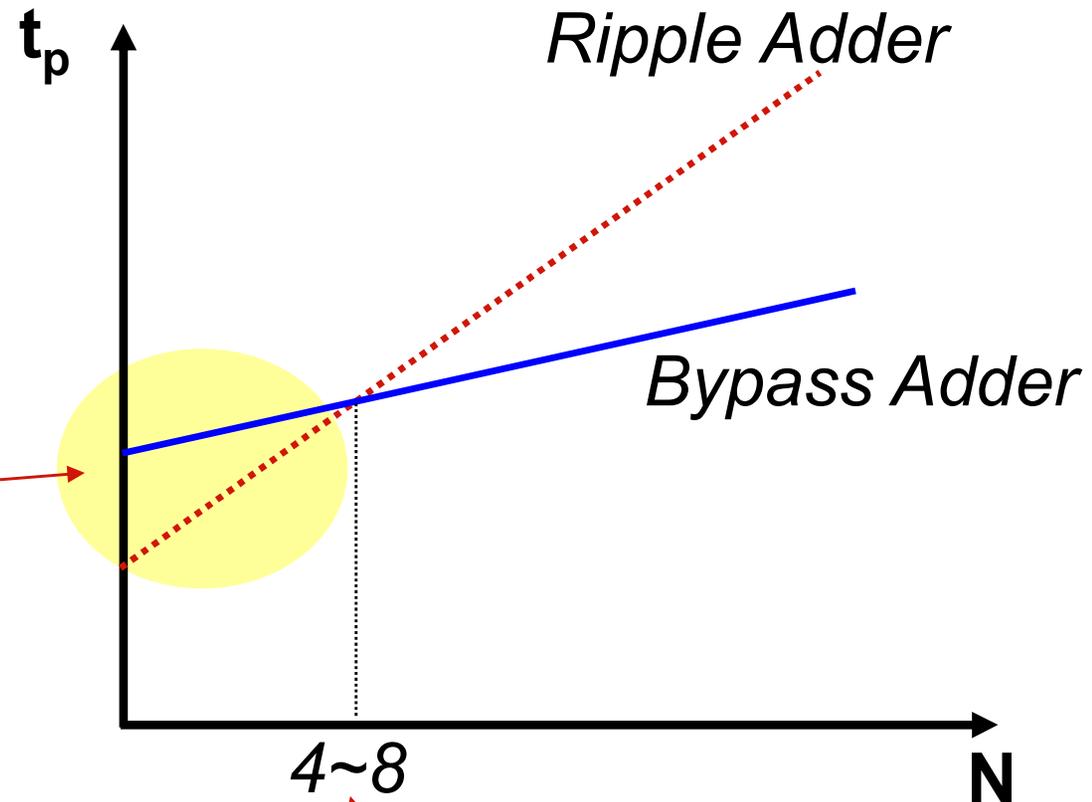
# Carry Ripple versus Carry Bypass

For smaller N, bypass adder is not preferred due to the overhead of bypass multiplexer




Depends on technology

# Linear Carry-Select Adder

 

**~ 30 % Hardware overhead**


# 16-bit Linear Carry-Select Adder

 

$$N=16 \quad M=4$$

$$t_{adder} = t_{setup} + Mt_{carry} + (N/M)t_{mux} + t_{sum}$$

# Adder Delays - Comparison

 


# Look-Ahead - Basic Idea

Expanding Lookahead equations:

$$C_{0,k} = G_k + P_k C_{0,k-1}$$
 
$$C_{0,k} = G_k + P_k (G_{k-1} + P_{k-1} C_{0,k-2})$$



All the way:

$$C_{0,k} = G_k + P_k (G_{k-1} + P_{k-1} (\dots + P_1 (G_0 + P_0 C_{i,0}))))))$$

# Carry Determination


$$C_{o,0} = G_0 + P_0 C_{i,0}$$

$$C_{o,1} = G_1 + P_1 C_{o,0} = G_1 + P_1 (G_0 + P_0 C_{i,0}) = G_1 + P_1 G_0 + P_1 P_0 C_{i,0}$$

$$C_{o,2} = G_2 + P_2 G_1 + P_2 P_1 G_0 + P_2 P_1 P_0 C_{i,0}$$

$$C_{o,3} = G_3 + P_3 G_2 + P_3 P_2 G_1 + P_3 P_2 P_1 G_0 + P_3 P_2 P_1 P_0 C_{i,0}$$

# 4-bit Look-Ahead

 

**Large stack**



**Poor Performance**

# Multipliers


## The Binary Multiplication

				1	0	1	0	1	0		Multiplicand
x				1	0	1	1				Multiplier
<hr/>											
				1	0	1	0	1	0		} Partial products
				1	0	1	0	1	0		
				0	0	0	0	0	0		
				0	0	0	0	0	0		
+	1	0	1	0	1	0					
<hr/>											
	1	1	1	0	0	1	1	1	0		Result


# *Reduce Partial Products*

- Partial products can be reduced by multiplier transformation (Booth's Recording)
- Reduce number of partial products is equivalent to reducing the number of additions

# 4X4 Bit-Array Multiplier

 


# Critical Path

 

For  $MXN$  Bit-Array Multiplier

$$t_{\text{multiplier}} = [ (M-1) + (N-2) ] t_{\text{carry}} + (N-1) t_{\text{sum}} + t_{\text{and}}$$

# Carry-Save Multiplier

 


Carry is saved for the next adder stage

Vector Merging Adder


$$t_{multiplier} = (N-1) t_{carry} + t_{and} + t_{merge}$$

# The Barrel Shifter

Area Dominated by Control Wiring

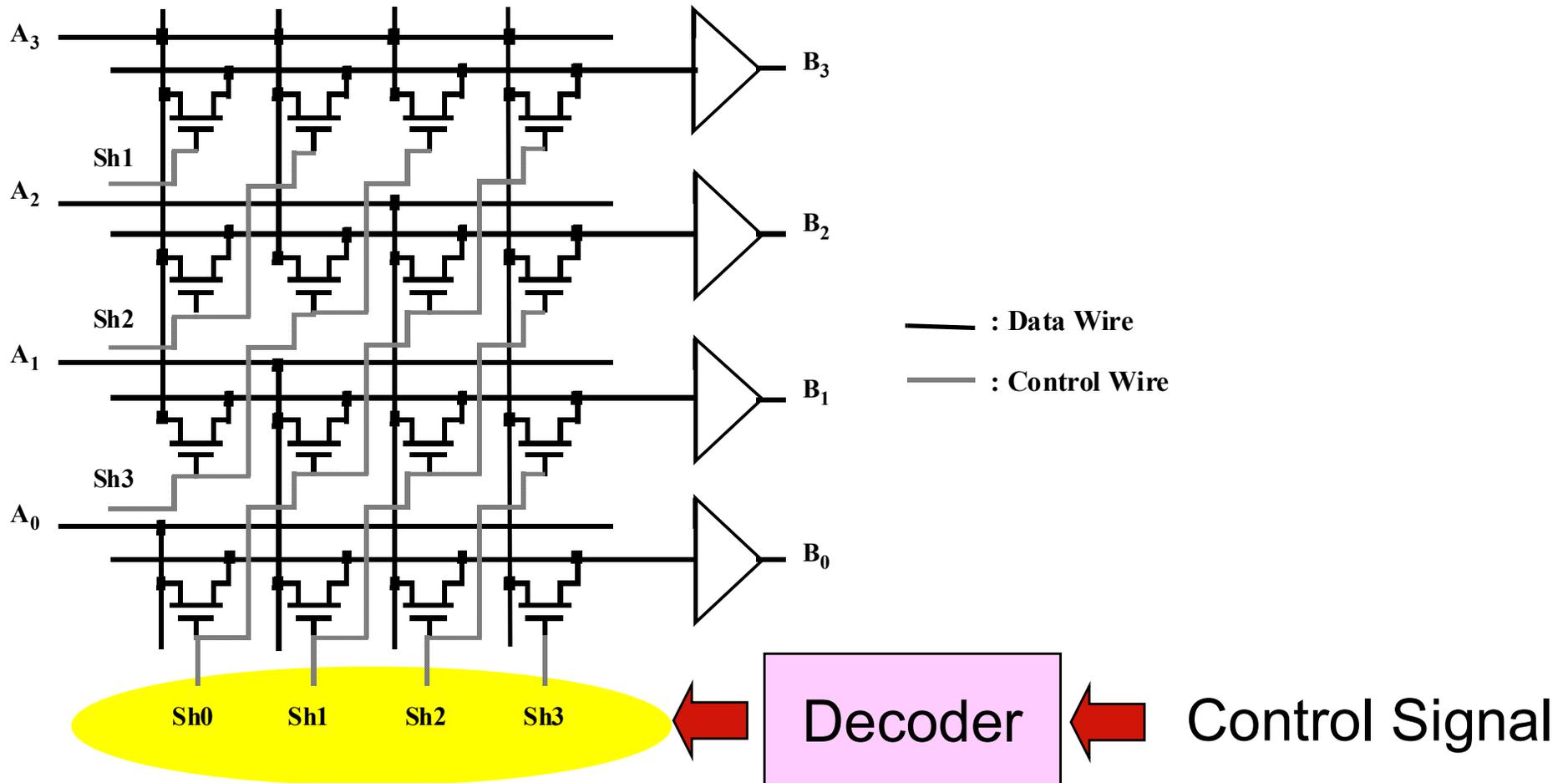


# 4x4 barrel shifter

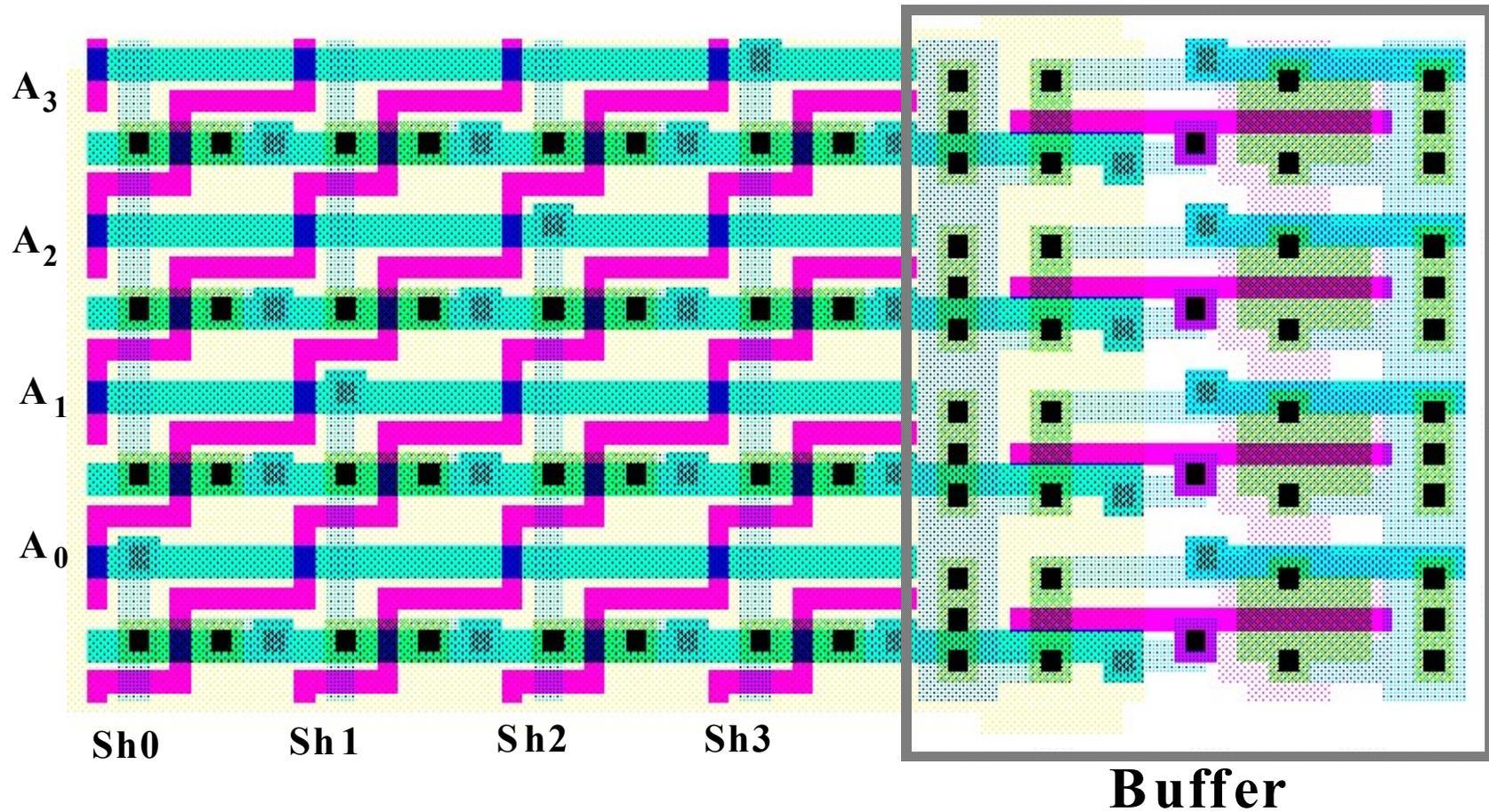

$$\text{Width}_{\text{barrel}} \sim 2 p_m M$$

# Logarithmic Shifter

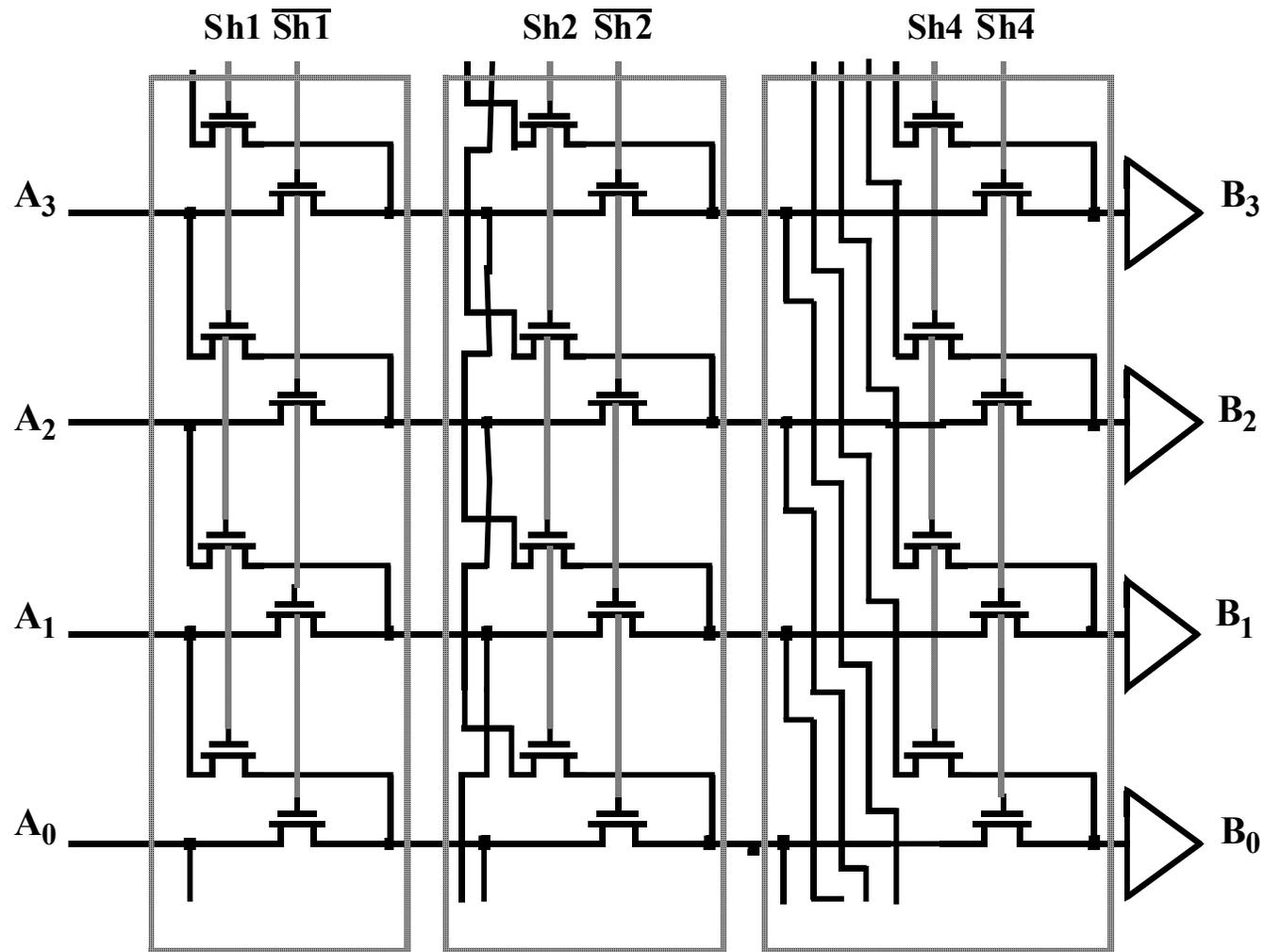

# 0-7 bit Logarithmic Shifter

