
 
 


Structure of silicon crystal

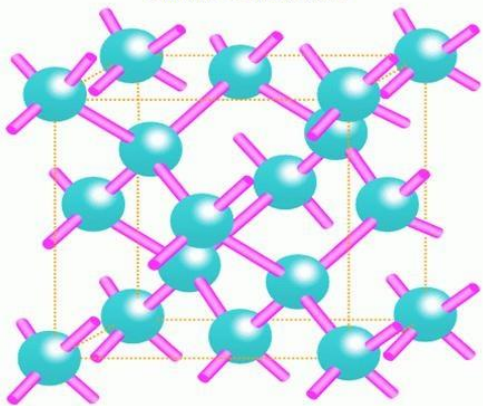

# *ECE 122A*

# *VLSI Principles*

## *Lecture 3*

Prof. Kaustav Banerjee  
Electrical and Computer Engineering  
University of California, Santa Barbara  
*E-mail: [kaustav@ece.ucsb.edu](mailto:kaustav@ece.ucsb.edu)*

# *MOS voltage levels*

## □ **NMOS summary**

- Transfers logic '0' completely (good for discharging a node)
- Does not transfer logic '1' completely (bad for charging a node)


## □ **PMOS summary**

- Transfers logic '1' completely
- Does not transfer logic '0' completely

## □ **Result:**

- **NMOS used for pull-down, PMOS for pull-up**

# Switch Behavior of NMOS and PMOS

 

To establish a path between “a” and “b”, both g1 **AND** g2 must be ON


To establish a path between “a” and “b”, at least g1 **OR** g2 must be ON

**FIG 1.14** Connection and behavior of series and parallel transistors

# 2-input NAND Gate

**Table 1.2** NAND gate truth table

A	B	pull-down network	pull-up network	Y
0	0	OFF	ON	1
0	1	OFF	ON	1
1	0	OFF	ON	1
1	1	ON	OFF	0

 


*2 NMOS transistors must be in series....*

*2 PMOS transistors must be in parallel....*
 
# CMOS NAND Implementation

Recall De Morgan's Law.....

$$Y = \overline{A \cdot B} = \overline{A} + \overline{B}$$



(a)




(b)

**FIG 1.11** 2-input NAND gate schematic (a) and symbol (b)  $Y = \overline{A \cdot B}$

Also, 2-input NOR:  $Y = \overline{A + B} = \overline{A} \cdot \overline{B}$

# CMOS 3-input NAND Implementation

 


**$Y=0$ , when  $A=B=C=1$**

Hence, A, B, C are in series for the NMOS (pull-down network)

**$Y=1$ , when A or B or C=0**

Hence, A, B, C are in parallel for the PMOS (pull-up network)

**FIG 1.12** 3-input NAND gate schematic  
 $Y = \overline{A \cdot B \cdot C}$

 

**FIG 1.22** Various implementations of a CMOS 4-input AND gate

# 2-input NOR Gate

$$2\text{-input NOR: } Y = \overline{A + B} = \overline{A} \cdot \overline{B}$$


Table 1.4		NOR gate truth table	
<i>A</i>	<i>B</i>	<i>Y</i>	
0	0	1	
0	1	0	
1	0	0	
1	1	0	

**2 PMOS must be in series.....**

**2 NMOS must be in parallel....**




# CMOS NOR Implementation

 

(a)




(b)

 


**FIG 1.15** 2-input NOR gate schematic (a) and symbol (b)  $Y = \overline{A + B}$

# CMOS 3-input NOR Implementation

 

**FIG 1.16** 3-input NOR gate schematic  
 $Y = \overline{A + B + C}$

# Combinational Logic

 

	pull-up OFF	pull-up ON
pull-down OFF	Z	1
pull-down ON	0	crowbarred (X)

**Output state X should always be avoided: static power**

**Output state Z indicates a high-impedance state. If a gate's output state = Z, that gate has no influence on the rest of the circuit**

 
**Z-state is used in tri-state logic circuits and is of relevance in certain gates such as multiplexers**

**FIG 1.13** General logic gate using pull-up and pull-down networks

# Compound Gates





$$Y = \overline{A.B + C.D}$$

 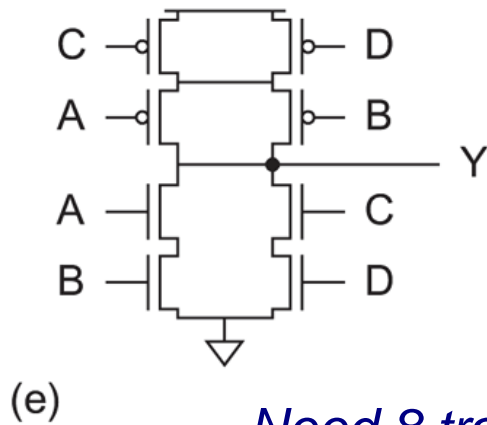  *Needs 20 transistors....*




**FIG 1.23** Inefficient discrete gate implementation of AOI22 indicating transistor counts

# Compound Gates $Y = \overline{A.B + C.D}$




# Compound Gates

 

**FIG 1.18** CMOS compound gate for function  $Y = \overline{(A + B + C)} \cdot D$


# Pass Transistors

 

**FIG 1.19** Pass transistor strong and degraded outputs

# Transmission Gates: Pass Transistors in Parallel

Both 0 and 1 passed strongly


 


*Double Rail Logic: both the control input and its complement is required*

**FIG 1.20** Transmission gate



# Tristate Buffer

  

**FIG 1.24** Tristate buffer symbol


# Tristate Buffer

**Table 1.5** Truth table for tristate

$EN / \overline{EN}$	$A$	$Y$
0/1	0	Z
0/1	1	Z
1/0	0	0
1/0	1	1

*Note: Z indicates a 'high-impedance' third state....*

# Transmission Gate as Tristate Buffer

 


**Non-restoring:** *input-signal will slowly degrade over a number of stages.... since Y is not connected to either Vdd or Gnd*

**FIG 1.25**

Transmission gate

# Tristate Buffer as Inverter

**Restoring:** O/P (Y) is directly connected to **Vdd** or **GND**

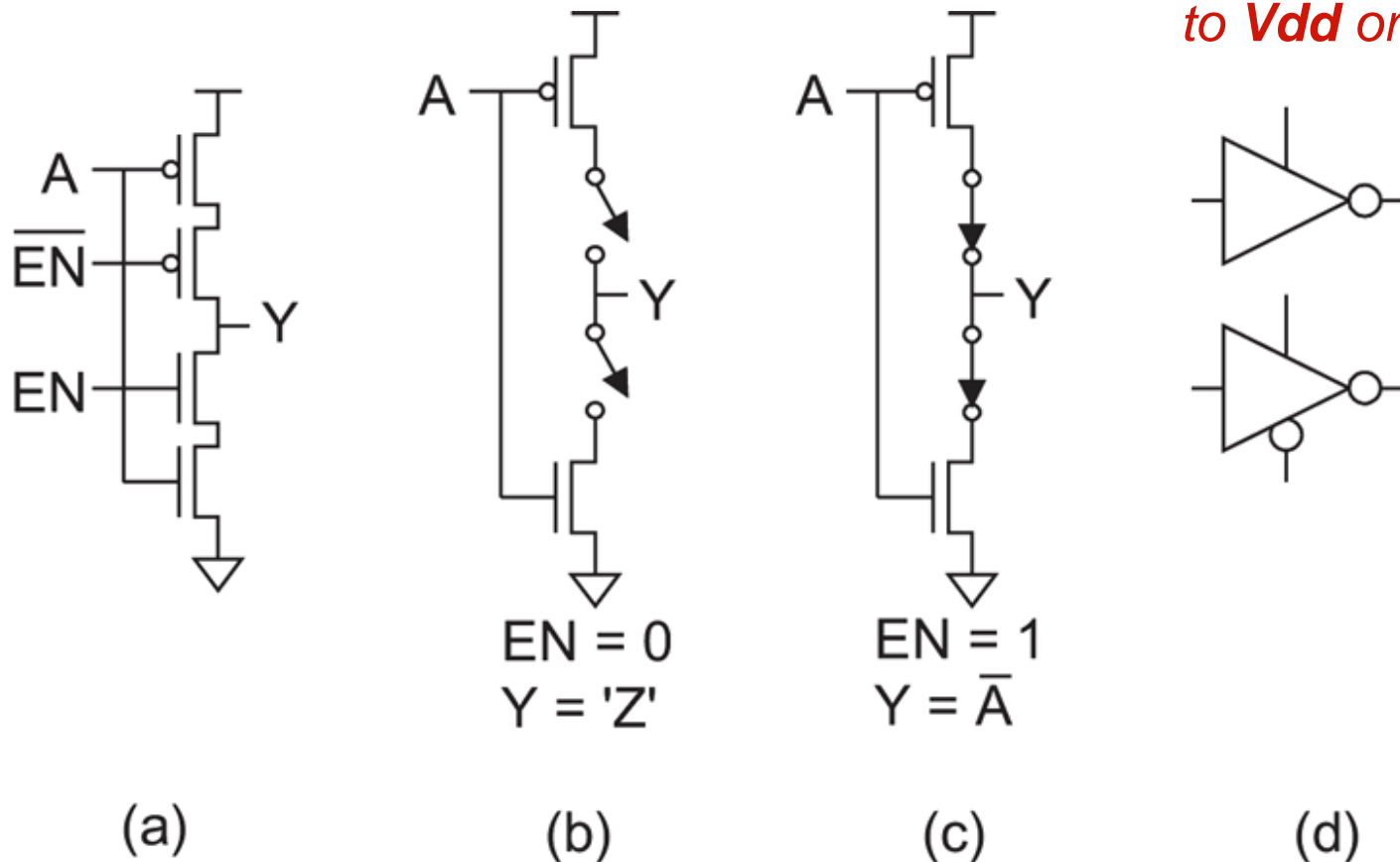


**FIG 1.26** Tristate inverter

# Multiplexer (MUX)

Connects **one** of  $n$  inputs to the **output**....


Used as data selectors...encoders

## 2:1 MUX

 

$$Y = As + Bs'$$

## 4:1 MUX

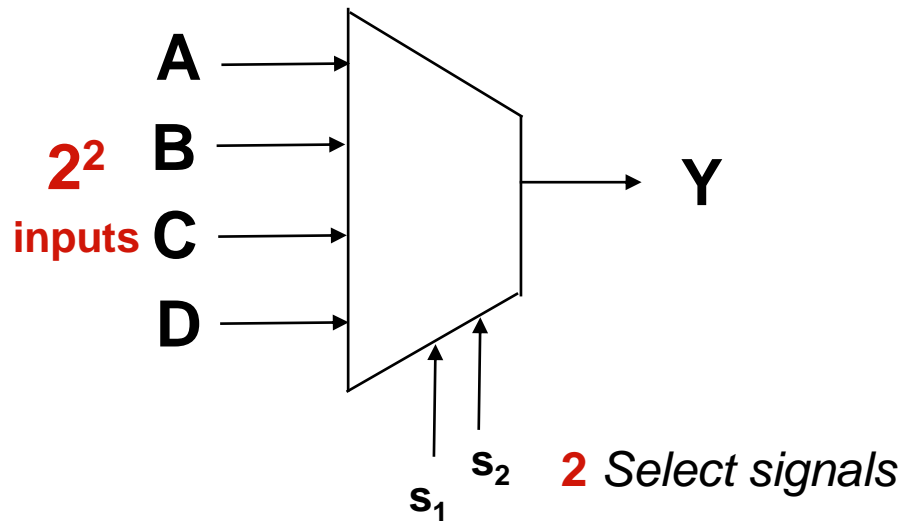

$$Y = As_1s_2 + Bs_1s_2' + Cs_1's_2 + Ds_1's_2'$$

In general,  $2^n$  inputs will have  $n$  select signals

$$Y = \sum_{k=0}^{2^n - 1} m_k I_k$$

$m_k$  is a minterm of the  $n$  control variables and  $I_k$  is the corresponding data input

# 2:1 Multiplexer (MUX)


**Table 1.6** Multiplexer truth table

$s / \bar{s}$	$D1$	$D0$	$Y$
0/1	X	0	0
0/1	X	1	1
1/0	0	X	0
1/0	1	X	1

$$Y = D1.S + D0.\bar{S} \text{ (when } s = 0, D1=X, \text{ when } \bar{s}=0, D0=X)$$

Note: X indicates a **don't care** condition

# Non-restoring MUX

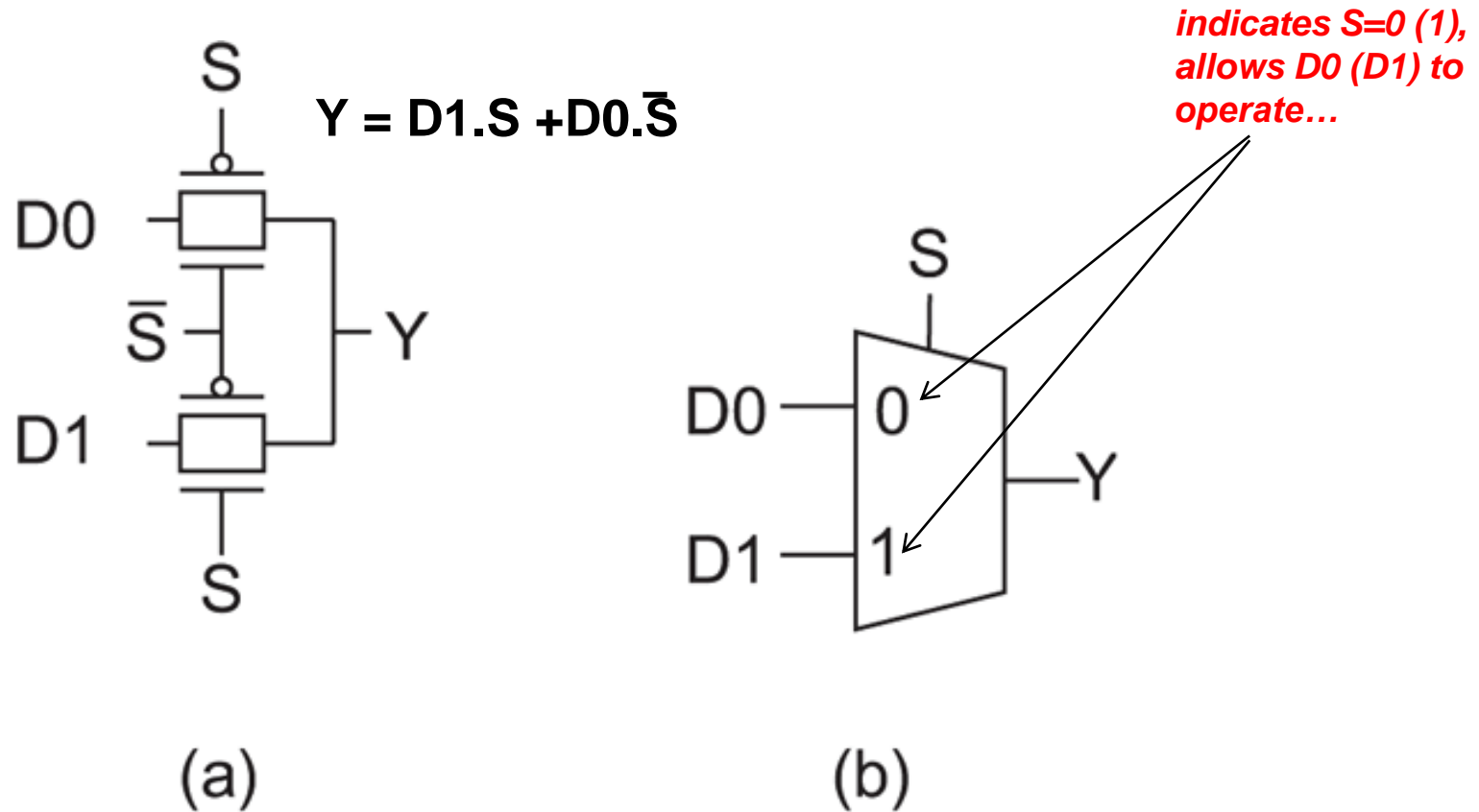

**FIG 1.27** Transmission gate multiplexer


# Inverting and Restoring MUX

$$S/\bar{S} = 0/1$$

$$D0 = 0: Y = 1 = \bar{D0}$$

$$D0 = 1: Y = 0 = \bar{D0}$$


$$\bar{Y} = D1.S + D0.\bar{S}$$

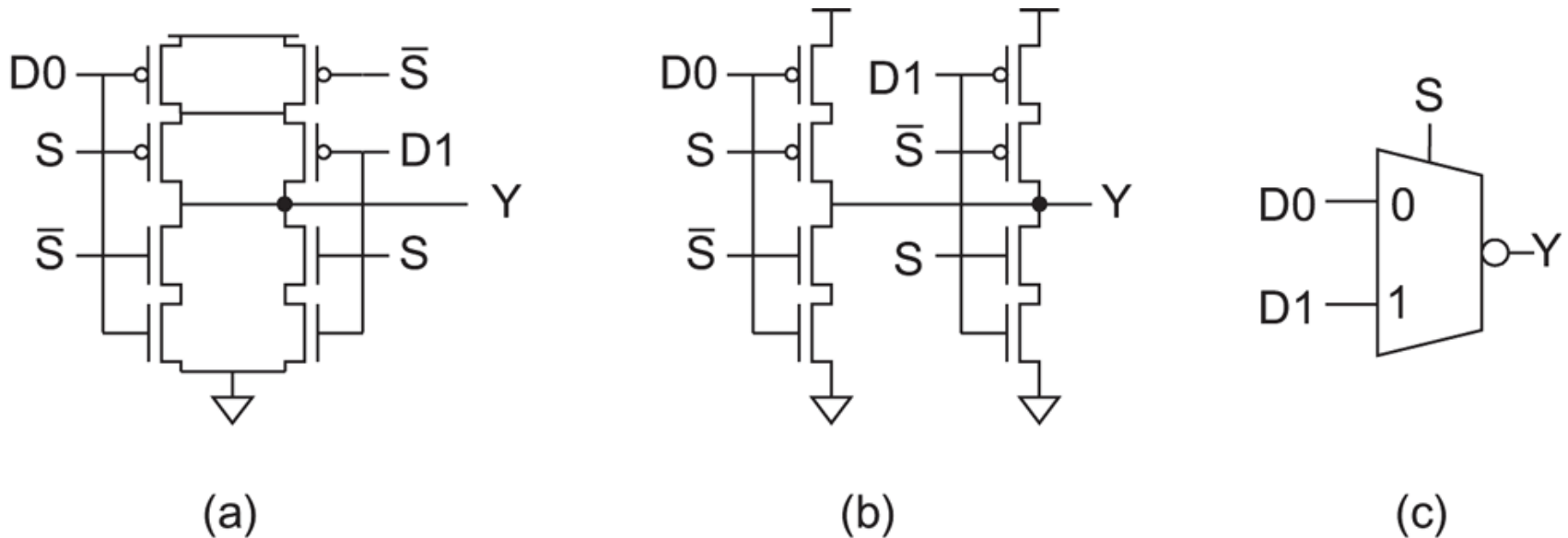


**FIG 1.28** Inverting multiplexer



# A 4:1 MUX

 

(a) Using three 2:1 MUXs

 


(b)

**FIG 1.29** 4:1 multiplexer

# Static CMOS Summary


- ❑ In **static** circuits at every point in time (except when switching) the output is connected to either GND or  $V_{DD}$  via a low resistance path.
  - fan-in of  $n$  (or  $n$ -inputs) requires  $2n$  ( $n$  N-type +  $n$  P-type) devices
- ❑ **Non-ratioed logic**: gates operate independent of PMOS or NMOS sizes (since no conflict between pull-up and pull-down networks)
- ❑ **No path** ever exists between **Vdd** and **GND**: **low static power**
- ❑ Fully-restored logic: (NMOS passes “0” only and PMOS passes “1” only)
- ❑ Gates must be **INVERTING**:  $Y = \bar{X}$ , so that  $X=1$  (NMOS pull-down network is “ON”) for  $Y=0$  (node is fully discharged)

# Latches (level sensitive device)

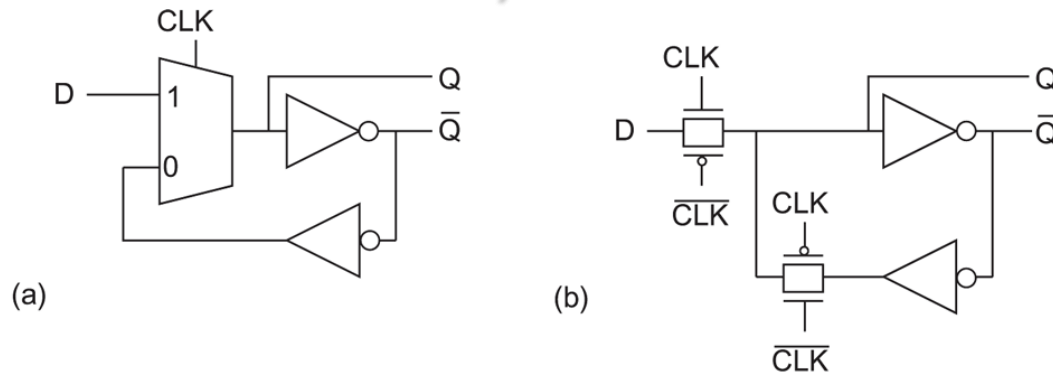


*CLK=1: D to Q*

*CLK=0: Holds state of Q*

 

**As long as CLK remains high: D to Q**

 

**FIG 1.30** CMOS positive-level-sensitive D latch

# Flip-Flops

(edge-triggered device)

Combines two latches:

One +ve sensitive (**slave**) and one -ve sensitive latch (**master**)

Edge Triggered FF or Master-Slave FF

$CLK=0$ :  $D$  to  $QM$

$$\overline{QM} = \overline{D}$$

Slave holds previous value of  $Q$

$CLK=1$ : master can't sample input and holds value of  $D$

Slave opens and  $QM=(D) = Q$


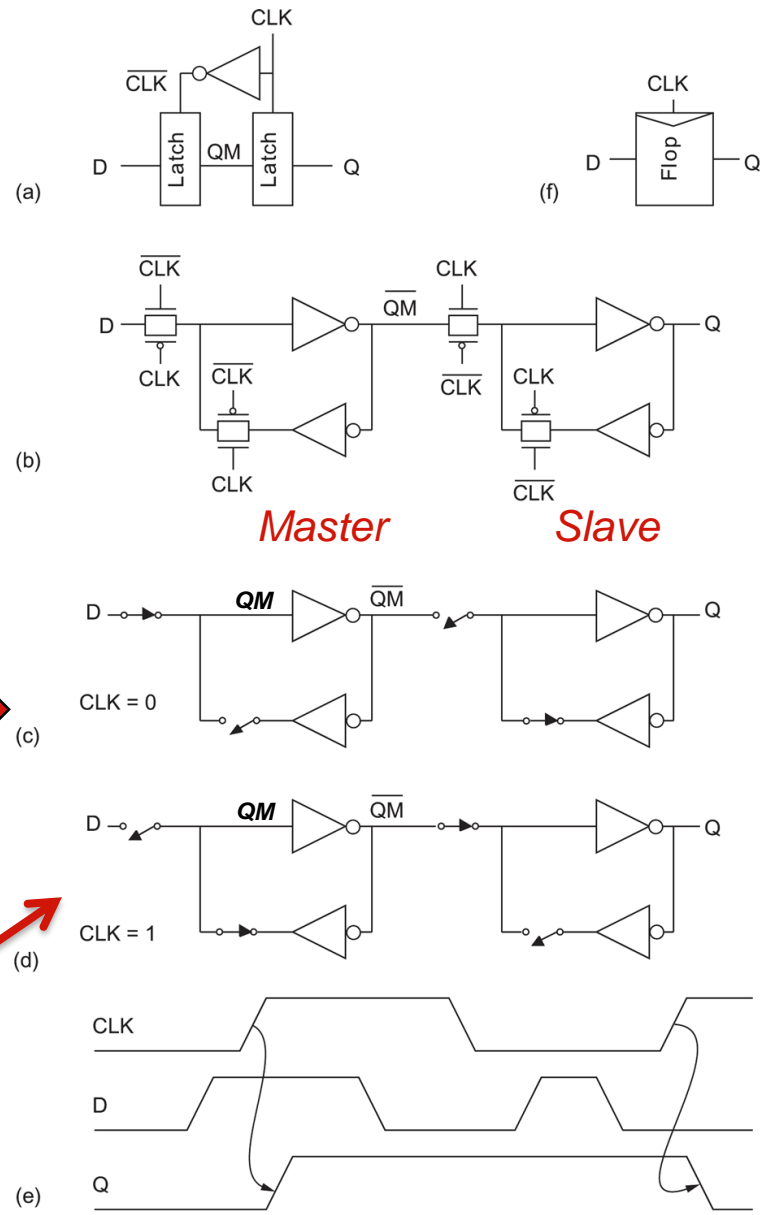
 


FIG 1.31 CMOS positive-edge-triggered D flip-flop

# Timing Definitions

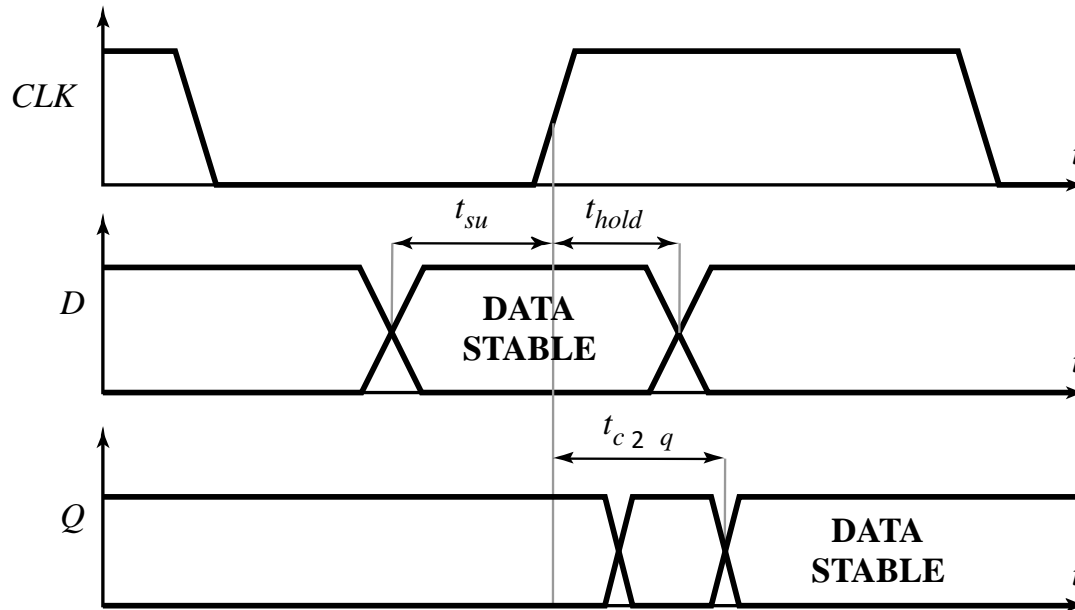

$t_{su}$  = **setup time** = time for which the data inputs (D) must be valid before the CLK edge

$t_{hold}$  = **hold time** = time for which data input must remain valid after the CLK edge

$t_{c2q}$  = **worst case** propagation time through the Register (w.r.t the CLK edge)