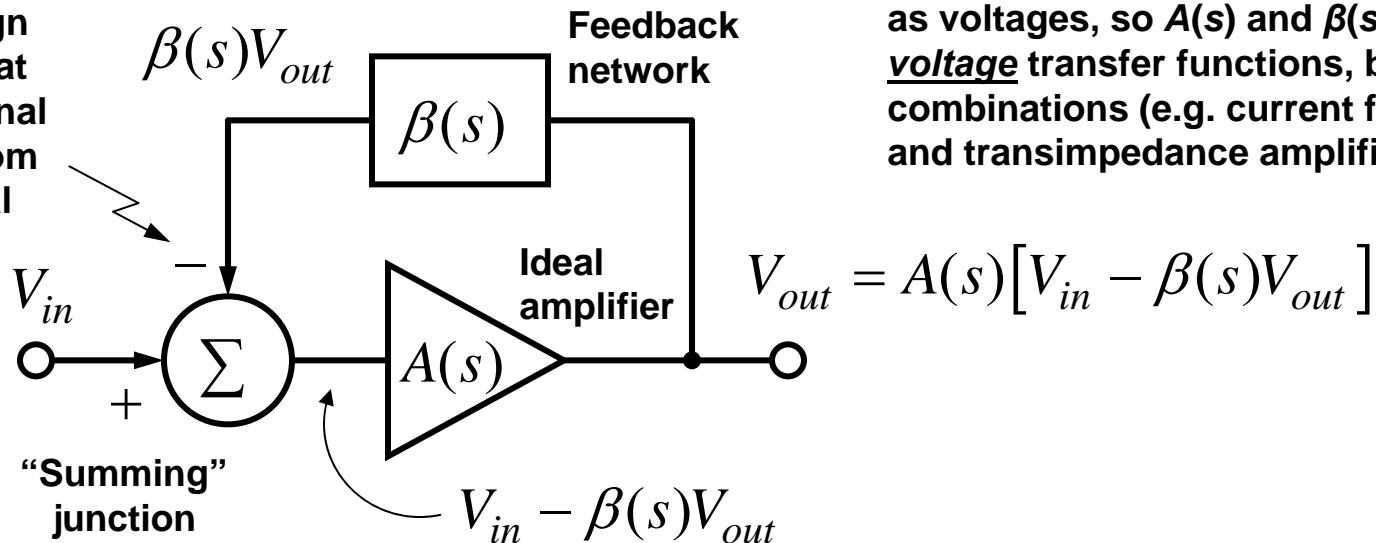


# Basic Feedback Concepts

Consider an ideal gain stage with negative feedback

Negative sign indicates that feedback signal subtracts from input signal



Here we are representing the signals as voltages, so  $A(s)$  and  $\beta(s)$  are voltage transfer functions, but other combinations (e.g. current feedback and transimpedance amplifiers)

$A(s)$  is the “open-loop gain”. It is the gain of the amplifier by itself, with no external feedback path

The gain of the system with feedback is given by:


$$\frac{V_{in}}{V_{out}} = \frac{A(s)}{1 + \beta(s)A(s)}$$

When the amplifier gain is very large, 
$$\frac{V_{in}}{V_{out}} = \frac{A(s)}{1 + \beta(s)A(s)} \Rightarrow \frac{1}{\beta(s)}$$

Thus the gain of the system is determined by the feedback components.


In transistor amplifiers, feedback allows us to stabilize the gain with respect to parameter variations

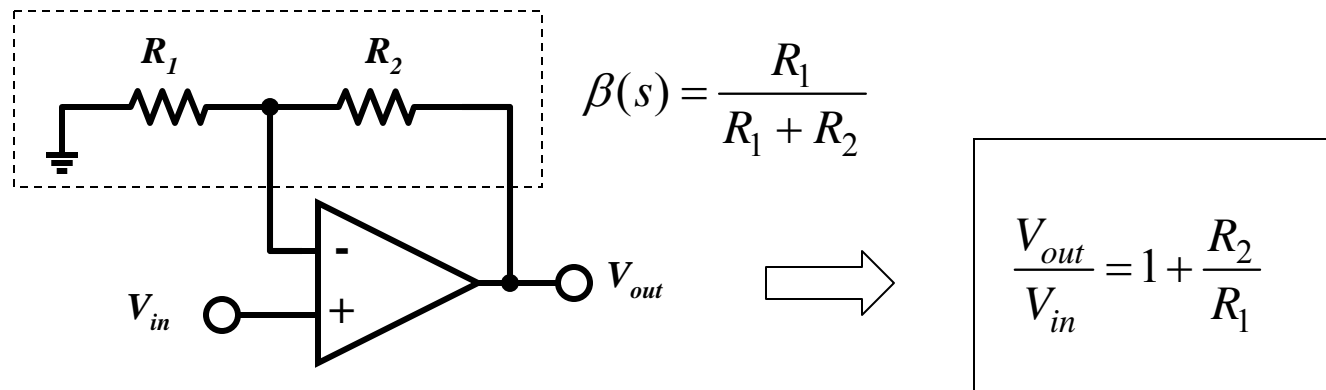In op-amp circuits, most gain stages do not depend on the actual op-amp gain as long as the op-amp has a large gain and high input impedance)




# Basic Op-Amp Gain Stages

### Inverting Amplifier

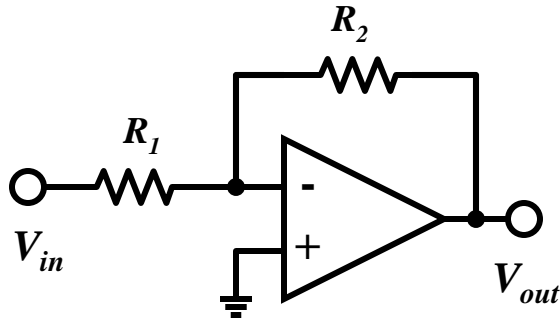

### Non-Inverting Amplifier

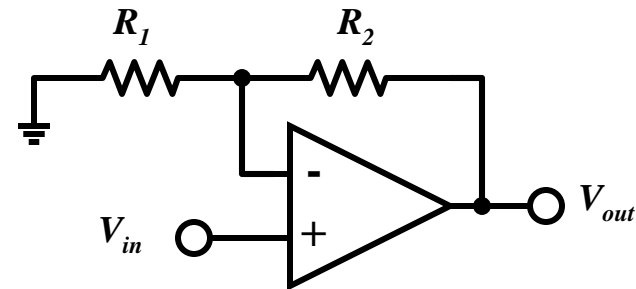

Replacing the op-amps by the simple equivalent circuit (dependent source) gives:

$$\frac{V_{out}}{V_{in}} = \frac{-\frac{R_2}{R_1}}{1 + \frac{1}{A_v} \left( 1 + \frac{R_2}{R_1} \right)}$$

For large gain  $A_v \rightarrow \infty$

$$\frac{V_{out}}{V_{in}} \Rightarrow -\frac{R_2}{R_1}$$


$$\frac{V_{out}}{V_{in}} = \frac{A_v}{1 + \frac{A_v}{1 + \frac{R_2}{R_1}}}$$

$$\frac{V_{out}}{V_{in}} \Rightarrow 1 + \frac{R_2}{R_1}$$
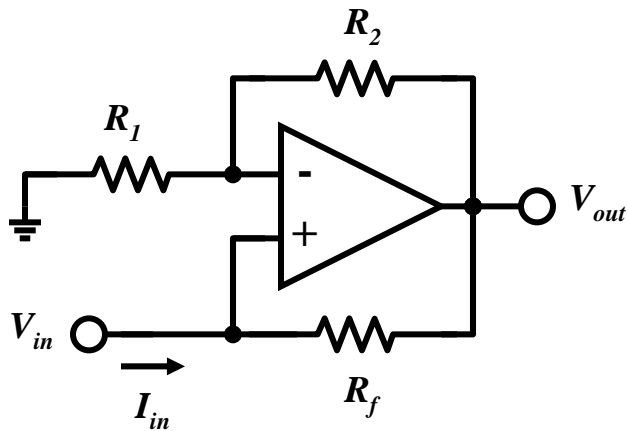
# Negative Resistance Circuit

Positive feedback is often associated with potential instabilities and usually avoided for that reason. But it can be exploited. This is an interesting example:

Use positive feedback to create a “negative resistor”:



$$\frac{V_{in}}{I_{in}} = \frac{A_v R_f}{1 - \frac{A_v}{1 + R_1 / R_2}} \Rightarrow -R_f \left( 1 + \frac{R_1}{R_2} \right)$$

A negative resistance means that the input current flows out of the terminal, thus the circuit can supply energy to an external circuit.

Negative resistance circuits are often used in oscillators