

ECE 2B – Winter 2006

HW #5 – Due March 9<sup>th</sup> by 3:30pm

(1) Do the following problems in Chapter 4:  
4.32, 4.34

(2) Do the following problems in Chapter 5:  
5.3, 5.6, 5.9, 5.12, 5.14

(3) Find  $V_{CE}$ ,  $I_B$ , and  $I_C$  for the following circuit:

