

# Introduction to Agilent ADS circuit simulation tools

- Introduction
- DC Simulation
- Transient Simulation
- How do you calculate power dissipation in ADS?
- Parameter Sweeps
- Defining subnetworks in ADS
- Interconnect modeling

## ***Introduction***

ADS provides a vast array of simulation modes and models. For design of high speed digital circuits, the most useful simulation tools will be DC and transient analysis. Whether to use ADS or HSPICE is a matter of individual preference. Since ADS is oriented toward microwave applications, you will find that it contains a much larger library of transmission line and passive component models that include nonidealities of these components. When dealing with high speed interconnections, this might provide the incentive to learn to use ADS even if you are already an experienced HSPICE user. On the other hand, ADS has yet to handle transistor model libraries in a convenient manner. It is much simpler to switch between process corners in HSPICE using the library commands.

The easiest way to learn ADS is through example files. ADS project files are stored in a compressed format with a .zap file extension.

1. Download the *ece225\_ex1.zip* file from the course website and locate it in your user directory with write permission. This may require renaming the file since Internet Explorer likes to add a .zip extension to these files. Rename the file by removing the .zip.

2. Open up ADS from the START menu.


*Start > Programs > Advanced Design System 2002 > Advanced Design System*

There are two ways to begin using ADS.

The first is to import an existing compressed project file. (Simulations are saved in a “project” directory.) Choose: File > Uncompress. Browse to find and select the correct file. When the file is uncompressed, a schematic display panel and a data display panel will open. Simulations are performed from the schematic and outputs read on the data display.

The second method is to open up a new project. You must choose a name for the project directory. If the project has already been created, then open it up with the Open icon and selecting the project name.

### Open existing project

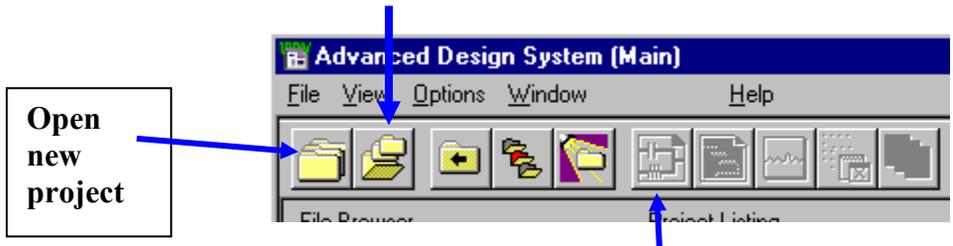


If the schematic window doesn't open automatically, open the window with this button.
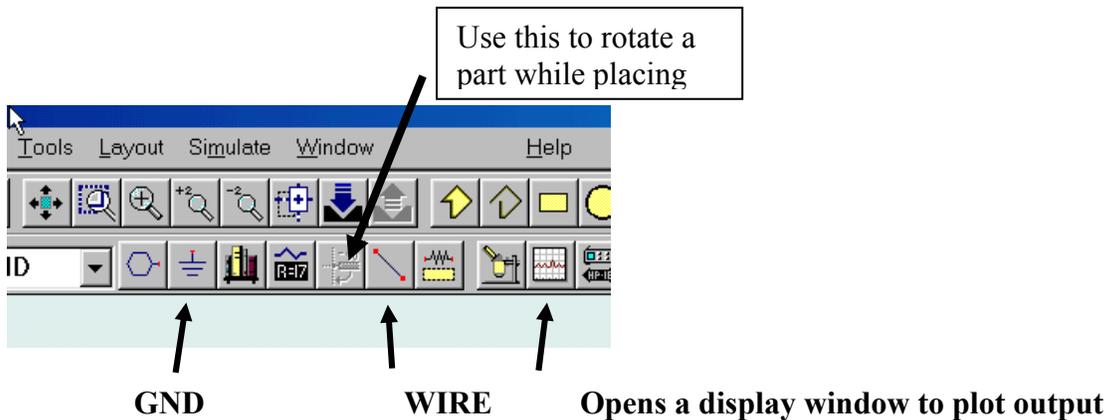
### DC simulation.

Open the CMOS inverter schematic (*inverter\_vtc*). Notice that the simulation type is set through a controller icon. These are found in the pulldown menu on the toolbar at the upper left of the window. In this example, a DC sweep of the input voltage is enabled as shown below.



Schematics can be constructed by placing components and interconnecting them with wires. Use the drop down menu and associated palette at the left side of the schematic panel to select components.



All variables, swept or fixed, must be identified and initialized first with a VAR icon block.

The toolbar shows the VAR icon circled in blue. Below it, three variable blocks are defined:


VAR	VAR	VAR
VAR1	VAR3	VAR2
VIN=0	lambda=1.2e-7	WN=3*lambda
VDD=2.5	ADP=WP*5*lambda	WP=6*lambda
Vstep=VDD/100	ADN=WN*5*lambda	LN=2*lambda
	PDN=WN+8*lambda	LP=2*lambda
	PDP=WP+8*lambda	

Output variables are defined by labeling circuit nodes. (Insert > Wire/Pin label) You can also add current probes wherever needed to measure current.

The **Probe Components** palette shows **I.Probe** and **OscTest** icons. The circuit diagram includes the following components and annotations:


- MOSFET\_PMOS** MOSFET2: Model=MODpmos25, Length=LP, Width=WP
- MOSFET\_NMOS** MOSFET1: Model=MODnmos25, Length=LN, Width=WN
- BSIM3\_Model** MODnmos25
- Vout**: label the output node (circled in blue)
- VDD**: nodes can be connected with wires or by labels.
- I\_Probe** and **I\_Probe1**: current probes connected to the VDD node (circled in blue)
- V\_DC** SRC1: Vdc=VDD
- V\_DC** SRC2: Vdc=VIN

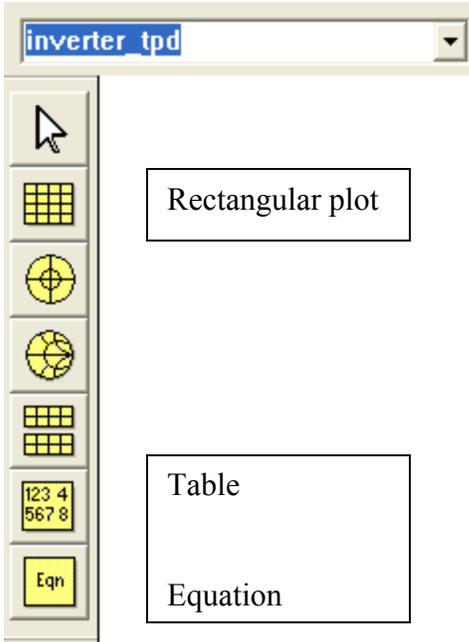
Run the simulation (F7) then view the data display. Any node voltage can be plotted or read in a table. The palette on the left side of the data display provides several options.



Use pulldown menu to choose correct dataset

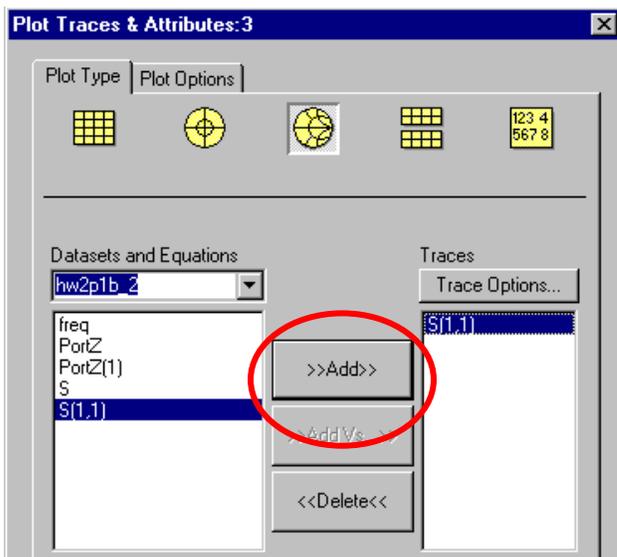Plot Traces & Attributes opens up with a menu that you can use to select the desired variable, in this case,  $S(1,1)$ . Highlight the variable by clicking on it and click on Add.



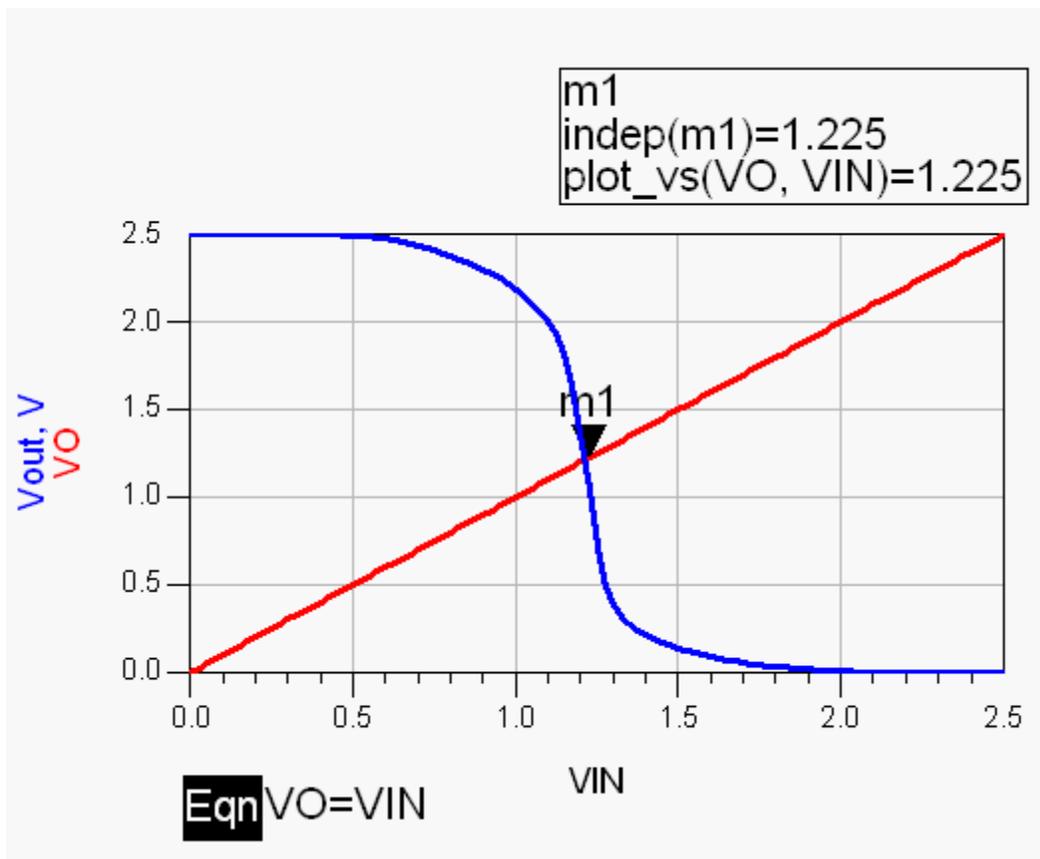


Markers can be placed on the plot to measure voltages more precisely. Equations can be defined as needed. In the example above, the equation  $VO = VIN$  is used to plot the red line that defines the inverter threshold.
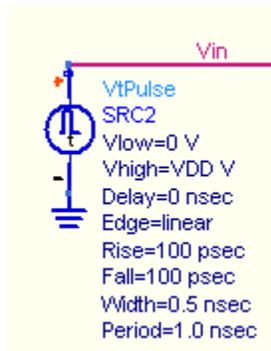
### ***Transient Analysis***


You can use the transient analysis simulation mode to predict propagation delays. Find the Simulation – Transient menu and select the transient controller. Then specify the simulation time and the maximum time step size.



A pulse source can be used for driving the inverter inputs. Choose appropriate voltages and rise/fall times. Refer to inverter\_tpd for an example.



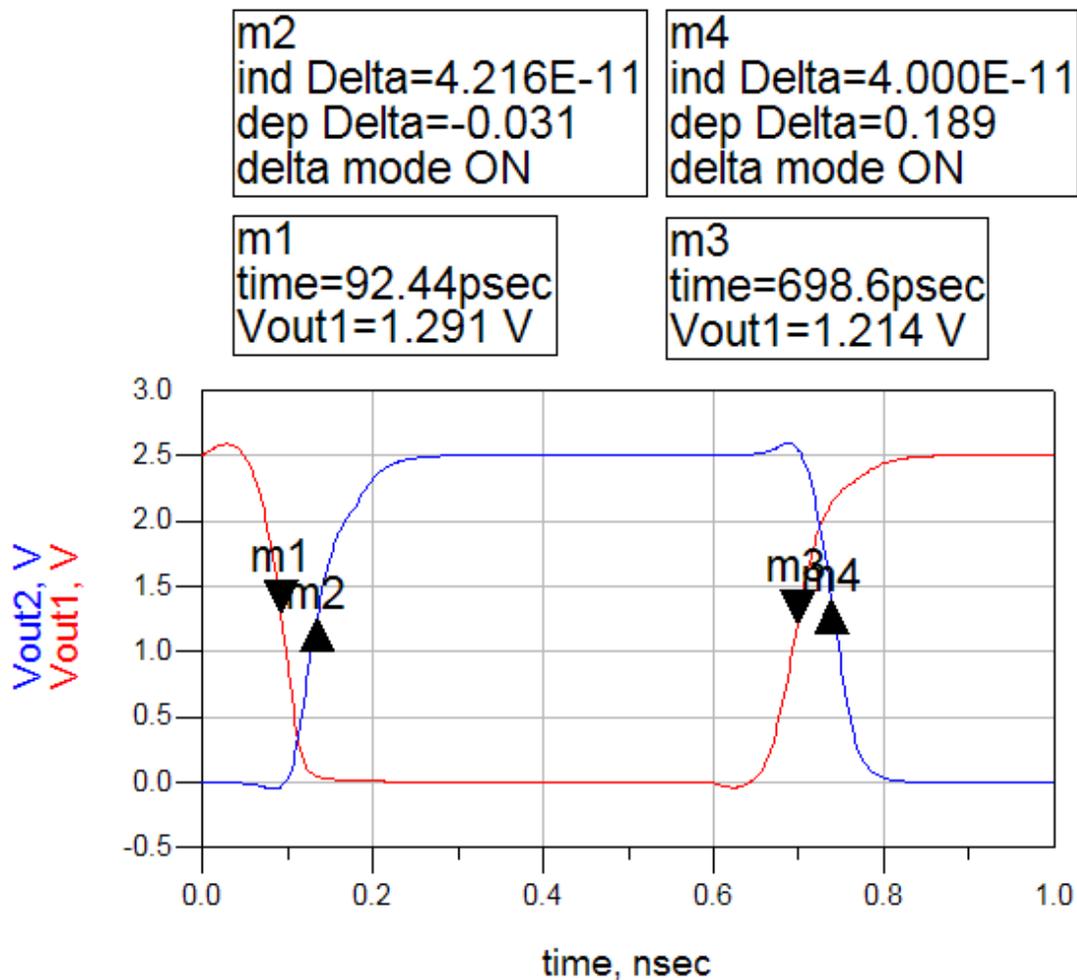The input and output of the inverter under test is shown below. Markers can be used to measure  $t_{PHL}$  and  $t_{PLH}$ . Using the delta marker function we find  $t_{PLH} = 42$  ps and  $t_{PHL} = 40$  ps



### ***How do you calculate power dissipation using ADS?***

You can include a current probe in the path to measure current. (its in the probe components palette: I\_probe. Note that the output from the probe contains a suffix .i

For example, the current value measured by a current probe with an instance I\_DD is called I\_DD.i)


A measurement equation can be written that includes calculation of the instantaneous power and the average power.

$$P\_inst = VDD * I\_DD.i$$
$$P\_avg = \text{mean}(p\_inst)$$

Note that the simulation should include an integral number of cycles in order to calculate the power accurately. Of course if you are averaging over lots of cycles, a small truncation error won't matter much.


You would look for the output of the measurement equation P\_inst or P\_avg in the data display as just another variable. If you do calculations with the Eqn in the data display, then you locate that output in another data set called equations. This is found when you are setting up a plot or table by the pulldown menu under datasets and equations.

<b>Eqn</b> p_inst=VDD*I_DD.i	P_avg
<b>Eqn</b> P_avg=mean(p_inst)	3.648E-5

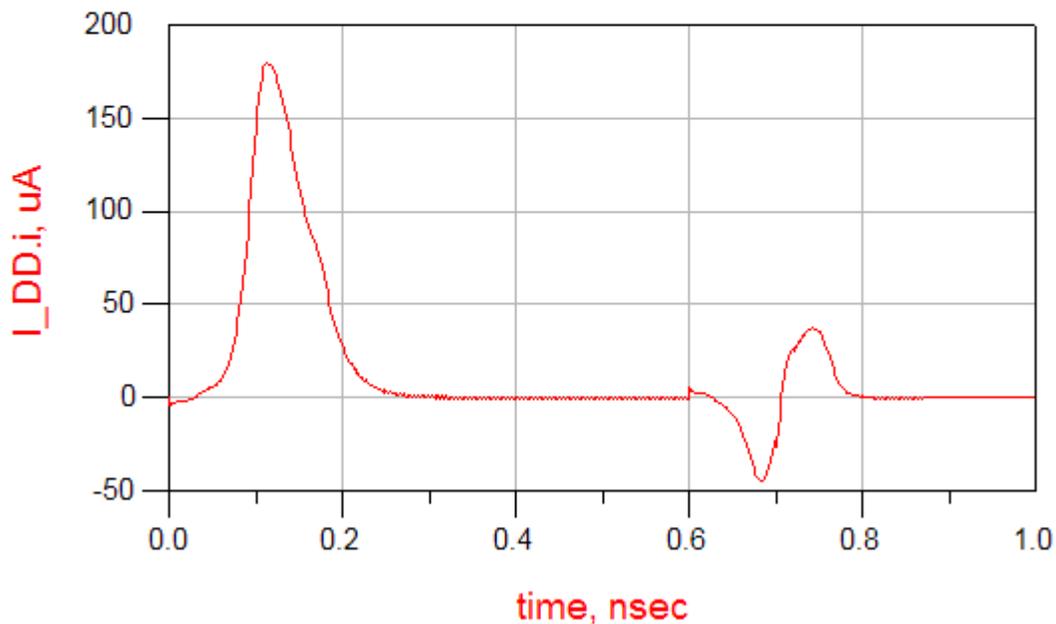
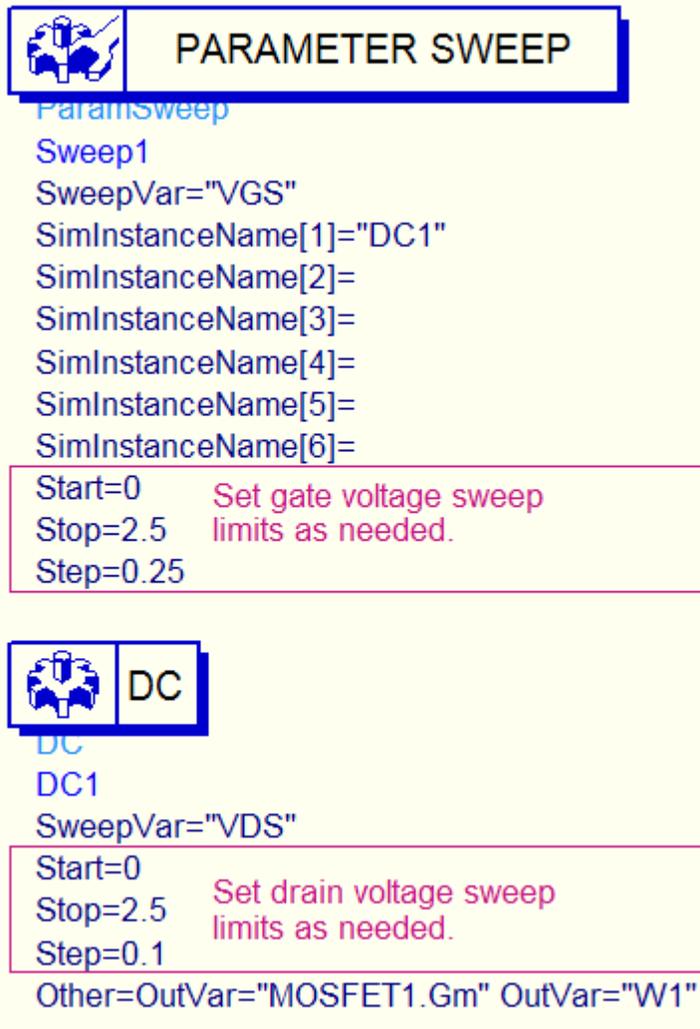
## Parameter Sweeps

Parameter sweeps perform a very useful function in simulations. It allow the systematic variation of one or more parameters to find optimum parameter values or to investigate trends in performance or simply to sweep out I – V characteristics of an active device. The latter is illustrated in the ECE225\_S03 project by the NMOS and PMOS curve tracer schematics. The parameter sweep controller can be found in the palette that displays for every simulation mode in ADS. In the example below, the DC controller sweeps VDS from 0 to 2.5V first with VGS = 0. VGS is then incremented by 0.25V and VDS is swept again. This continues until VGS = 2.5V at which point the simulation is complete.



The image shows a screenshot of the ADS software interface for configuring a parameter sweep. It is divided into two numbered steps:

**2.** **PARAMETER SWEEP**  
Paramsweep  
Sweep1  
SweepVar="VGS"  
SimInstanceName[1]="DC1"  
SimInstanceName[2]=  
SimInstanceName[3]=  
SimInstanceName[4]=  
SimInstanceName[5]=  
SimInstanceName[6]=

Start=0      Set gate voltage sweep limits as needed.  
Stop=2.5  
Step=0.25


**3.** **DC**  
DC  
DC1  
SweepVar="VDS"

Start=0      Set drain voltage sweep limits as needed.  
Stop=2.5  
Step=0.1  
Other=OutVar="MOSFET1.Gm" OutVar="W1"

A curve tracer-like display is plotted in the data display panel:

# NMOS\_curve\_tracer

## ID, Gm measurement display

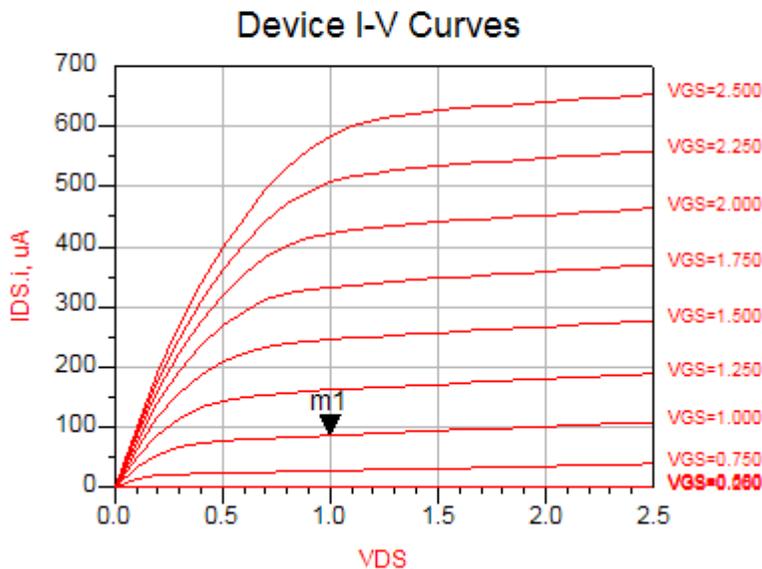


### Defining a Subnetwork in ADS:

Subnetworks allow you to take advantage of the hierarchy possible in ADS. You can save circuits or portions of circuits that you plan to reuse as subnetworks which can then be accessed in the Component Library.

Here are the steps:

Begin from your schematic of the circuit that you want to represent as a subnetwork.

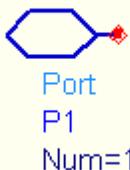1. Insert and label Port connectors from the tool bar. In the example of the inverter subnetwork, Port1 is connected to the input and Port2 to the output.



Complete the construction of your schematic for the subnetwork. Note that you will need to include transistor models into the subnetwork if your circuit requires transistors. Name and save the subnetwork.

2. . Create Subnetwork symbol:

*View > Create/Edit Schematic Symbol*


The Symbol Generator panel opens up. Click on the *Auto Generate Tab*  
Unfortunately, there are not logic symbols in the symbol library. Select a dual symbol and Order pins by location.

To return to the schematic, choose *View > Create/Edit Schematic Symbol (again)*  
Save the file

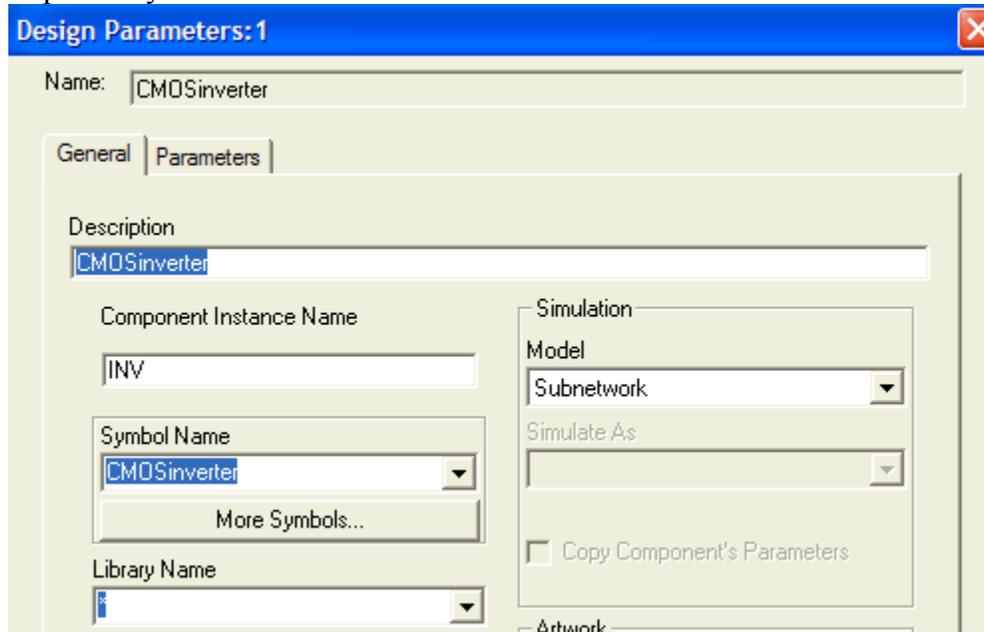
3. Name the circuit and set the design parameters

*File > Design Parameters*

General tab. The component name will be shown, CMOSInverter in this example. Name the component instance. For example: INV When the component is included in a schematic, each instance will be numbered sequentially.




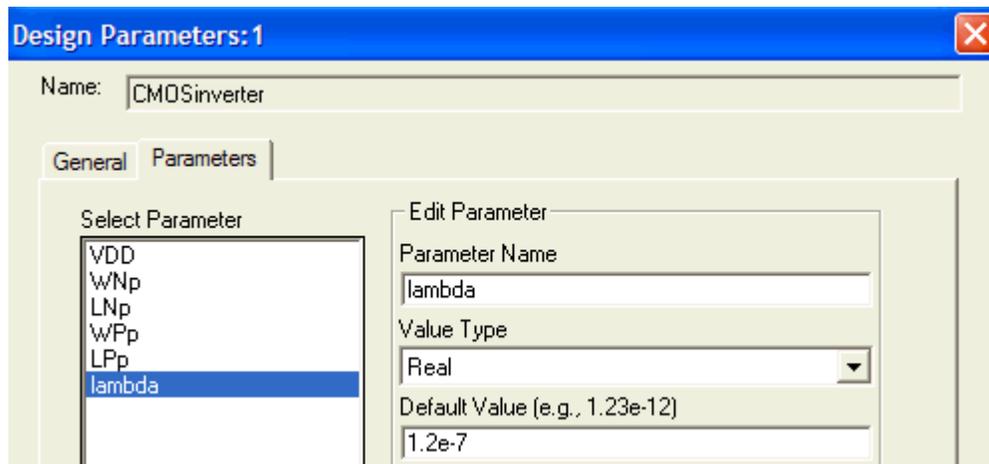5. If you want to allow adjustable parameters from outside the subnetwork, use the Parameters menu tab. This is useful when you want to sweep some parameter that is inside the subnetwork. In this example, 6 parameters are declared to be adjustable. Their values are given a default, but can be specified again outside the model in the schematic where it is being used.




6. Save the subnetwork again.

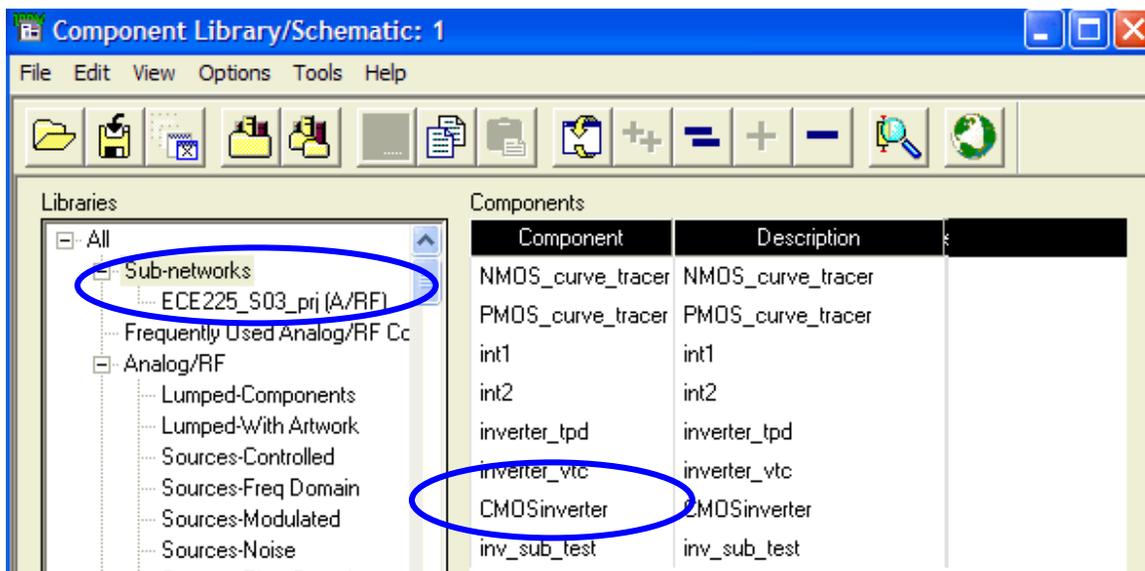
7. To insert your inverter into the schematic, use the component library icon (the bookshelf icon) on the tool bar to open the library. Select your project, then the component you wish to insert. You can then point and click into the schematic.



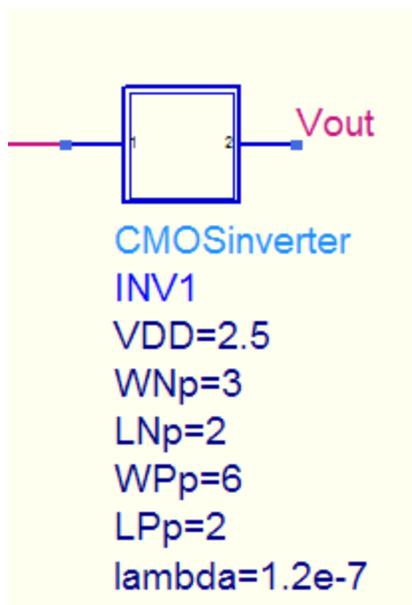The symbol appears like this in the schematic:



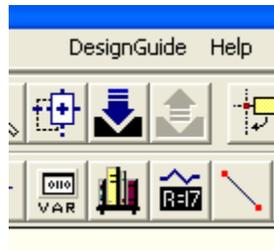7. You can push into the subnetwork to view or modify it with the down arrow icon on the toolbar.




## Interconnect models

The multilayer substrate model (T-lines – Multilayer) calculates the RLGC relationships between conductors in a multiple metal process. This is a lossy transmission line model that also considers skin effect losses. Using this with the single or coupled lines allows the simulation of interconnect delays and power or ground inductance effects on circuit performance. Refer to the int2 schematic in the ECE225\_S03 ADS example file project.

Interconnect metal conductivity and thickness and dielectric constant and thickness must be known and provided as inputs to the MLSUBSTRATE<sub>x</sub> model specification (where x = number of metal layers + 1). In the example below from Rabaey, Chandrakasan, and Nikolic<sup>1</sup>, a cross section of a 5 layer metal process is shown along with a table describing conductor thicknesses. Using the conductor thickness as a scale, one can estimate the dielectric thicknesses. It is assumed that the first dielectric layer is SiO<sub>2</sub> while subsequent ones may have a reduced dielectric constant of about 3 (perhaps polyimide).

LAYER	PITCH	THICK	A.R.
Isolation	0.67	0.40	-
Polysilicon	0.64	0.25	-
Metal 1	0.64	0.48	1.5
Metal 2	0.93	0.90	1.9
Metal 3	0.93	0.90	1.9
Metal 4	1.60	1.33	1.7
Metal 5	2.56	1.90	1.5
	μm	μm	

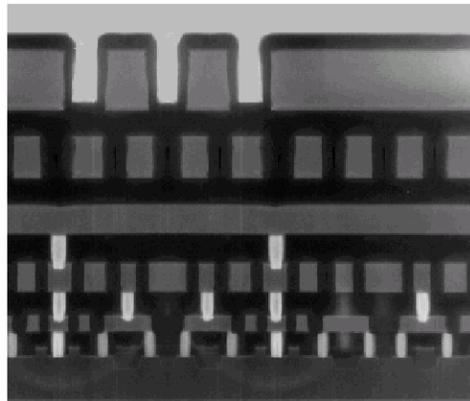


### Layer pitch, thickness and aspect ratio

The model parameters assign the highest layer number to the bottom layer. In this example, Metal 1 is assigned as a ground plane for signal conductors on Metals 2 and 3. M4 is assigned as another ground distribution plane and M5 is power. Note that it is possible to route longer interconnects on M4 or M5 if needed using a coplanar strip transmission line topology.

---
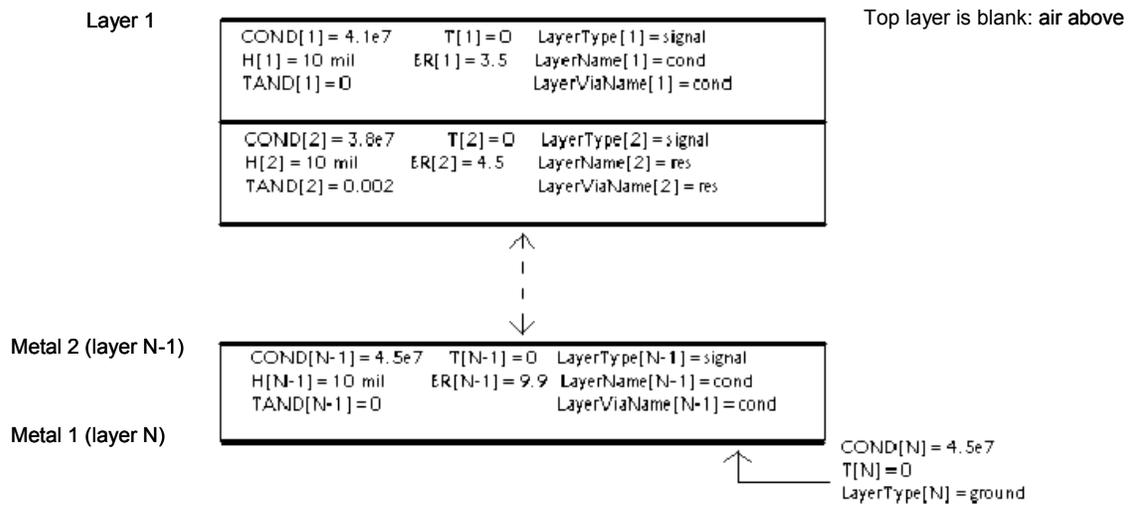
<sup>1</sup> J. Rabaey, A. Chandrakasan, B. Nikolic, Digital Integrated Circuits: A Design Perspective, Second Ed., Prentice-Hall/Pearson, 2003.



5 metal layer interconnect

```

MLSUBSTRATE6
Subst2
Er[1]=5           Er[4]=3           LayerType[4]=signal
H[1]=5 um        H[4]=2 um        LayerType[5]=signal
TanD[1]=0         TanD[4]=0        LayerType[6]=ground
T[1]=0 um        T[4]=0.9 um
Cond[1]=1         Cond[4]=3.8e7
Er[2]=3.9         Er[5]=3.9
H[2]=2.2 um      H[5]=1 um
TanD[2]=0         TanD[5]=0
T[2]=1.9 um      T[5]=0.9 um
Cond[2]=3.8e7    Cond[5]=3.8e7
Er[3]=3           T[6]=0.5 um
H[3]=2 um        Cond[6]=3.8e7
TanD[3]=0         LayerType[1]=blank
T[3]=1.3 um      LayerType[2]=power
Cond[3]=3.8e7    LayerType[3]=ground
  
```

MLnCTL\_C (T-lines – Multilayer) is used to represent single or coupled lines. The parameter n represents the number of lines. Constant width and spacing is assumed and all conductors must be on the same metal layer.

MLnCTL\_V allows for variable widths, spacings, and conductors can be on different layers.